


# Module 9C: The Voltage Comparator

## (Application: PWM Control via a Reference Voltage)

### Laboratory Outline

A voltage comparator considers two voltage waveforms, A and B, and outputs a binary (two-valued) voltage waveform indicating which is larger (a high voltage for  $V_{out}$  states that A is larger and a low voltage that B is larger, see Figure 1). In this module, we will study the application of the voltage comparator for PWM control via a reference voltage.

In the ECE110 laboratory exercise (Lab 8), you will have learned how to control the duty cycle of a PWM signal using a variable resistor in the feedback portion of an oscillator. This method is somewhat restrictive. Many sensors provide only access to the voltage output of a voltage divider circuit or, like an infrared receiver, a transistor-based voltage proportional (or *inversely-proportional*) to the received infrared intensity. These types of active sensors will require a different electronic mechanism to produce a sensor-controlled PWM signal than that used in Lab 8. A basic method of implementing PWM control via a reference voltage is made possible by comparing a triangular waveform to a slowing-varying reference voltage from the sensor.

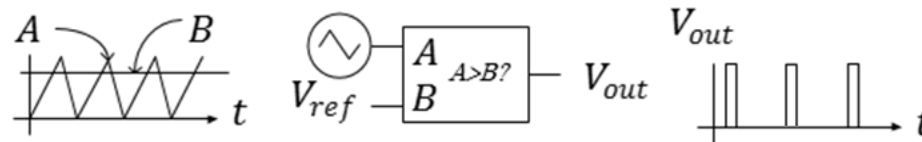

**Figure 1:** A block diagram demonstrating how a triangular waveform might be transformed into a PWM signal controlled by a reference voltage. When the reference voltage,  $V_{ref}$ , rises, the duty cycle of the PWM signal decreases.


### Prerequisites

- Laboratory Exercise #5, the construction of a simple oscillator circuit.
- *Explore More!* Module: The Voltage-Follower Buffer.
- (recommended prerequisite) Laboratory Exercise #8, the construction of an oscillator with a selectable duty cycle.

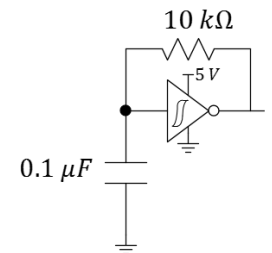
### Parts Needed

- The completed oscillator circuit (Lab#5)
- (1) LM358 Op Amps and (1) LM311 Voltage Comparator (2 per IC) (optionally, (2) LM358 Operational Amplifier)
- Trimpot 10 k $\Omega$  with knob (may be substituted with another trimpot...value is non-critical)

Notes: ***Inversely-proportional*** means that as one signal gets larger, the other gets proportionally smaller.



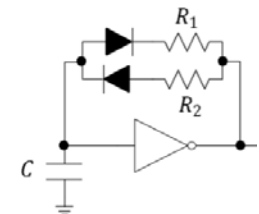Recall: Relaxation oscillator circuit from Lab 5.





Recall: A method to use (variable) resistance to control PWM duty cycle from Lab 8.

## At Home: Construction


- ✓ Create a triangular waveform generator by following the procedures for the **Explore More! Module: The Voltage-Follower Buffer**. That module may be submitted to your TA for separate module credit. When finished with that module, continue with the procedure here.

**Question 1:** Use the datasheet to add the schematic symbols for power and ground to the pinout below of the LM358 or LM311 used in the comparator circuit. We will use a 5- or 6-volt supply and ground the negative supply pin. What is the range of acceptable supply voltages?

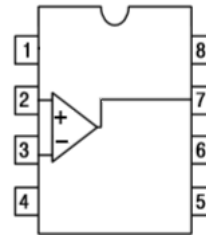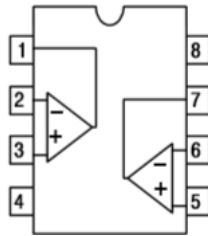


**Question 2:** On the physical pinout diagram above, add the circuit-schematic symbols of the components used to construct the circuit buffer of Figure 2.

Notes:

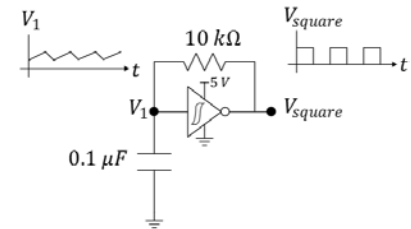


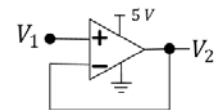The simple oscillator circuit waveforms from Lab 5.



A voltage follower used for “signal conditioning” from the *Explore More! Module: The Voltage-Follower Buffer*.


- ✓ Construct the voltage comparator circuit as shown in the figure below. The trimpot ( $10\text{ k}\Omega$ ) is not part of the voltage comparator, but is rather used to provide a controllable reference voltage. It may be substituted with another trimpot.

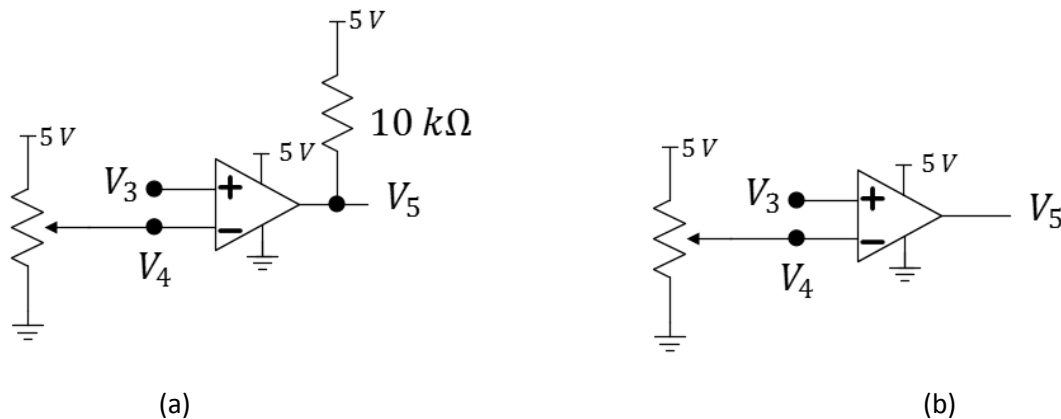

**Figure 2:** Configuration of a comparator test circuit based on (a) the LM311 comparator or (b) the LM358 op amp.

**Notes:** For the LM311-based circuit, the output pin is an “open collector” that should be biased towards  $V_{CC}$  using a so-called *pullup resistor* (shown in the figure to be  $10\text{ k}\Omega$ ). While the LM358 is readily available from your kit, the LM311 comparator chip offers faster response time and a larger output voltage range, the latter of which may be beneficial in this application. **NOTE:** If using the LM358, you may need to buffer the output using two consecutive Schmitt-trigger inverters (like in Lab #8).

- ✓ Construct the PWM circuit as shown in the figure below, where the node voltage  $V_4$  will control the duty cycle of  $V_5$ .

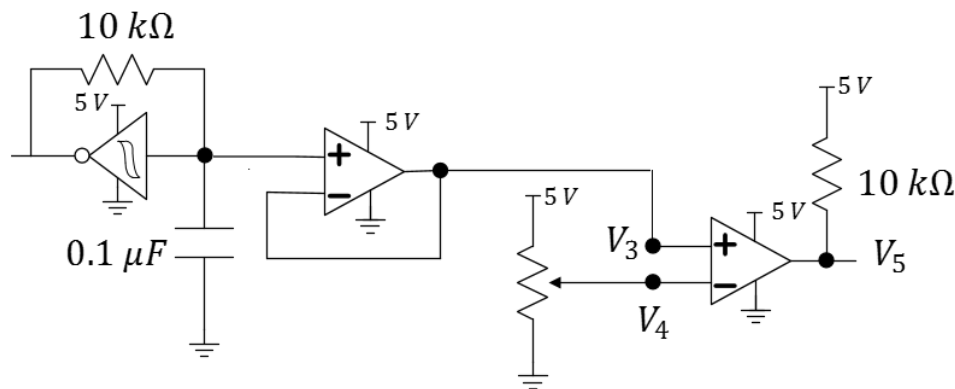

**Figure 3:** The final PWM circuit controlled by a reference voltage (assuming the LM311 was used).

## In the Laboratory: Analysis

With the circuit completed as in Figure 3, adjust the voltage output of the potentiometer-based voltage divider while simultaneously monitoring the three waveforms  $V_3$ ,  $V_4$ , and  $V_5$  on the oscilloscope.

**Question 3:** Describe what you see as the potentiometer (trimpot) is adjusted. Be sure to note the range of  $V_4$  that results in changes to the duty cycle of  $V_5$ . Think how  $V_3$  appears different than the representation of Figure 4.



**Figure 4:** Comparison of the inputs and output of a voltage comparator circuit used for PWM control.

**Question 4:** Produce a graph including all three plots for a duty-cycle near 30% and attach it to this report.

## Back at Home: Drawing Conclusions

You should have noticed that this implementation of the triangular waveform is not ideal. Our triangular waveform is a scaled and offset version of that plotted in Figure 4. The triangular waveform of Figure 4 goes from 0 V to nearly the full supply voltage of 5 V.

**Question 5:** Discuss why the  $V_3$  waveform of Figure 4 would be a better triangular waveform than ours when the reference voltage varies from 0 to 5 V.

## Learning Objectives

- To properly bias a voltage comparator based on either an LM358 Op Amp or a LM311 Voltage Comparator chip.
- To create a PWM waveform that is controlled by a reference voltage using the voltage comparator circuit.
- To gain experience in using the oscilloscope to assess a circuit while making and recording time-varying voltage waveforms.

## Learn More!

In **Explore More!: The Amplifier**, we will learn to convert the triangular waveform of the relaxation oscillator into a full-range waveform similar to that in Figure 4. In **Explore More!: PWM Control via an Active Sensor**, we will amend this method using the circuital tools learned in other lab modules to make the sensor-controlled PWM signal more **robust**.

Note: **Robust** is a term often used very loosely in engineering. It most often refers to a system that is insensitive to deviations in parameters or outside forces.