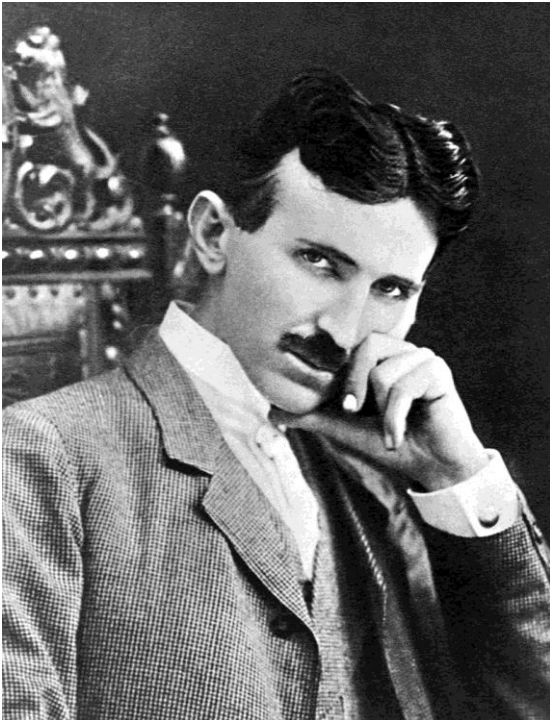


Lecture 9: AC and Time-average Power


- AC and DC
- Time-average Power
- Root-Means-Square (RMS) Voltage




Alternating vs. Direct Current




Nikola Tesla

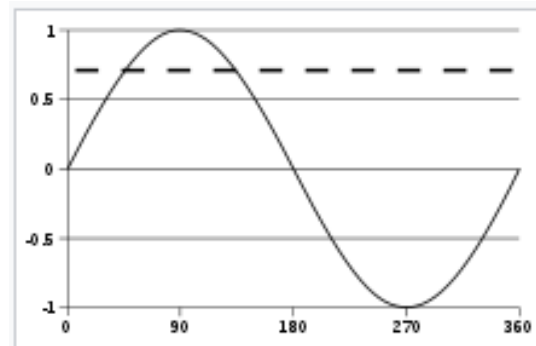

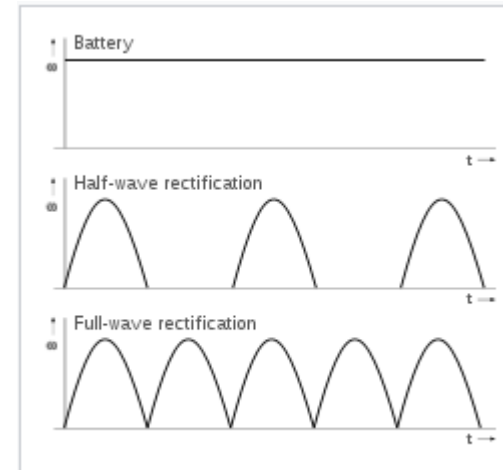A sine wave, over one cycle (360°).
The dashed line represents the **root mean square (RMS)** value at about 0.707



Types of direct current

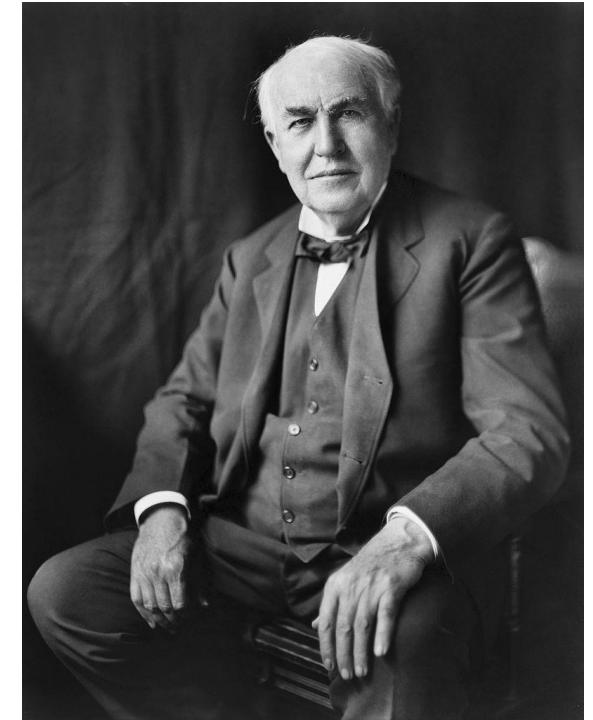

Thomas A. Edison

Explore More!...

Search for "Current War." An interesting read!


Power

For time-varying signals, power is a time-varying signal.

$$p(t) = i(t)v(t)$$

The **time-average power** is often of interest. Time average is computed by the equation
 
$$P_{avg} = \frac{\int_{-\infty}^{\infty} p(t) dt}{\int_{-\infty}^{\infty} dt}$$





Power Calculation: periodic

$$P_{avg} = \frac{\int_{-\infty}^{\infty} p(t) dt}{\int_{-\infty}^{\infty} dt}$$

If $v(t)$ and $i(t)$ are periodic, then $p(t)$ is periodic with period T

$$P_{avg} = \frac{\int_T p(t) dt}{T}$$

= area under $p(t)$ divided by T

= Energy in one period divided by T



Power Calculation: DC

If $v(t)$ and $i(t)$ are constant (DC), then $p(t)$ is constant

$$P_{avg} \equiv P = IV$$




Power Calculation: Noise

For non-periodic signals (e.g. constant white noise)

$$P_{avg} \approx \frac{\int_T p(t) dt}{T}$$

Where T is a sufficiently-long observation time

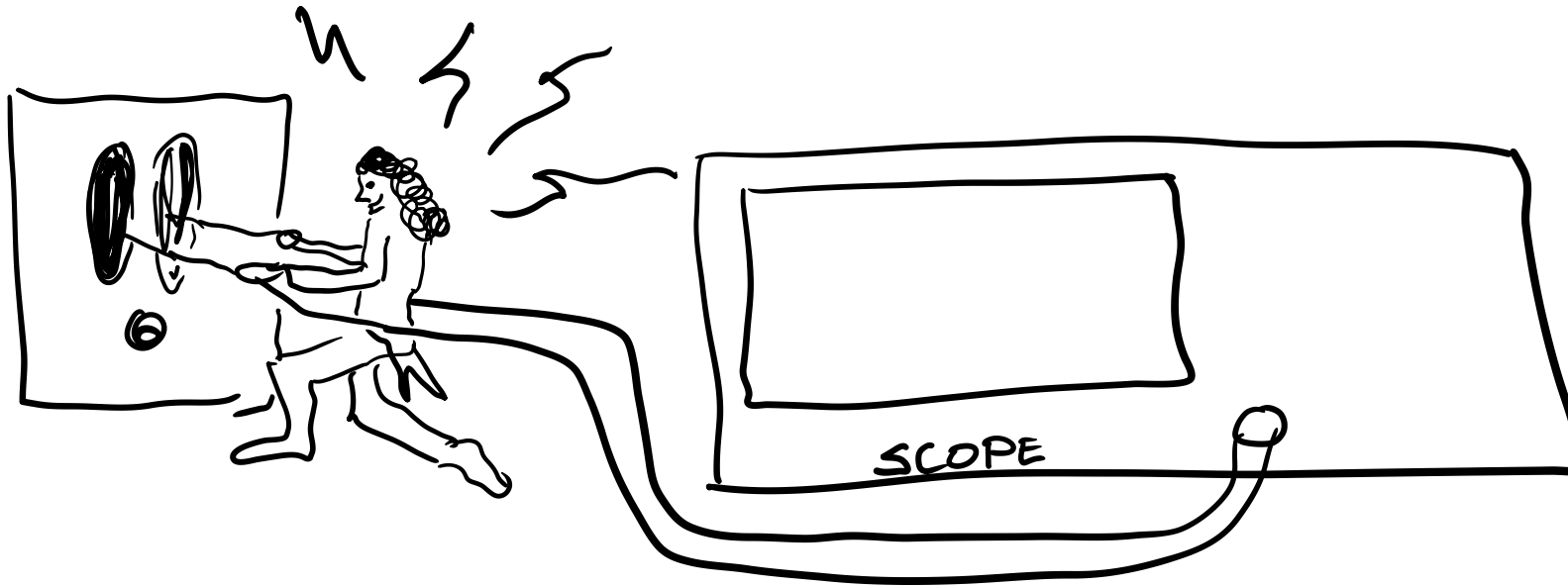Voltage from the wall plug is *sinusoidal*



Q: What is the peak instantaneous power absorbed by a 250Ω light bulb powered by the MAINS?

- A. 1 W
- B. 10 W
- C. 100 W
- D. 1 kW
- E. 10 kW

In History...

In the 1880's and 1890's, **Nikola Tesla** played a large role in improving DC motors, developing AC motors and generators, and developing many high-frequency/high-voltage experiments including many in the area of remote control and wireless telephony. **Marconi's** 1901 cross-Atlantic wireless transmission likely infringed upon a few of Tesla's nearly 300 patents.

We want Time Average Power, so What's This Stuff About RMS??

$$\begin{aligned} P_{avg} &= \frac{\int_{-\infty}^{\infty} p(t) dt}{\int_{-\infty}^{\infty} dt} \\ &= \frac{\int_{-\infty}^{\infty} v(t)i(t) dt}{\int_{-\infty}^{\infty} dt} \\ &= \frac{\int_{-\infty}^{\infty} \frac{v^2(t)}{R} dt}{\int_{-\infty}^{\infty} dt} \quad (\text{for a resistor}) \\ &= \frac{1}{R} \frac{\int_{-\infty}^{\infty} v^2(t) dt}{\int_{-\infty}^{\infty} dt} \\ &= \frac{1}{R} \text{avg}\{v^2(t)\} \end{aligned}$$

Define $V_{rms} \stackrel{\text{def}}{=} \sqrt{\frac{\int_{-\infty}^{\infty} v^2(t) dt}{\int_{-\infty}^{\infty} dt}}$ so that $P_{avg} = \frac{V_{rms}^2}{R}$
(for a resistor)

Important Comment: RMS voltage helps us find time-averaged power. We don't want RMS power...what does that even mean??

Important Comment #2: for things that are not resistors, we may need to look at $p(t)$ directly as V_{rms} doesn't tell the whole story.

Important Comment #3: You can use both V_{rms} , I_{rms} , and something called a power factor in more-advanced circuit courses. **Eg. ECE342**



Root-Mean-Square averages

RMS is meaningful when interested in power production/dissipation in AC.

$$V_{RMS} = \sqrt{\text{Average}[v^2(t)]}$$


1. Sketch $v^2(t)$
2. Compute $\text{Average}[v^2(t)]$
3. Take $\sqrt{\quad}$ of the value found in part 2.

Calculating P_{avg} and V_{rms}

$$y(t) = A \cos\left(\frac{2\pi}{T}t\right)$$

$A = \text{Amplitude}$
 $T = \text{period}$

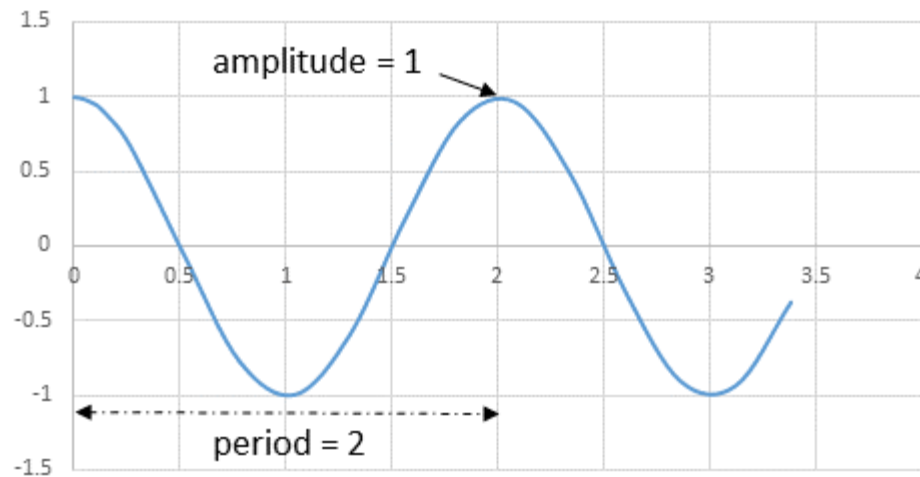Trig identity: $\cos(\alpha) \cos(\beta) = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$





USA “Mains voltage”

Q: What is the average power absorbed by a 250Ω light bulb if $A = 170\text{V}$?


In Practice: Time-varying signals

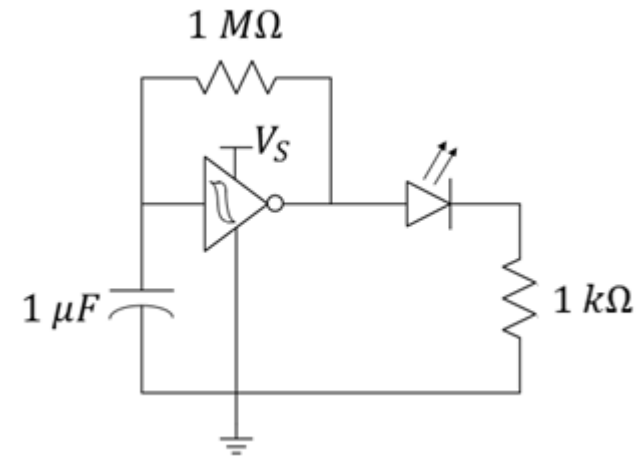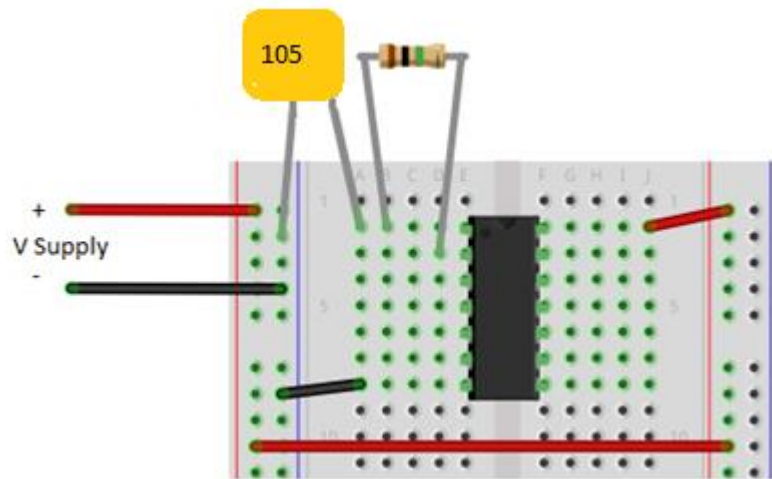In lab, we use the output of the inverter to change the input in a feedback loop. A “high” output drives the input high and a low input drives the input low. The inverter’s function causes “oscillation” to occur and the LED to flash. Note how the capacitor allows for changing input voltage.



Calculating P_{avg} and V_{rms}

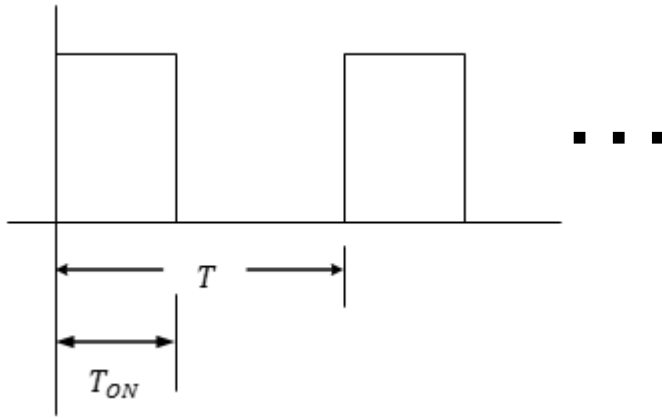Duty Cycle Definition: $\frac{T_{ON}}{T}$



Q: What happens to power and V_{rms} when T_{ON} is halved while T is unchanged?



L9 Learning Objectives

- a. Compute the time-average power from $p(t)$ plots
- b. Explain the meaning of V_{rms} and its relationship to P_{avg}
- c. Compute the rms-voltage from $v(t)$ plots