


Lecture 21: The BJT Voltage Amplifier

- Relating V_{out} to V_{in}
- Node notation for V_{CC}
- Voltage transfer function
- AC signal amplification




An interesting question

Self-excitation phenomenon?

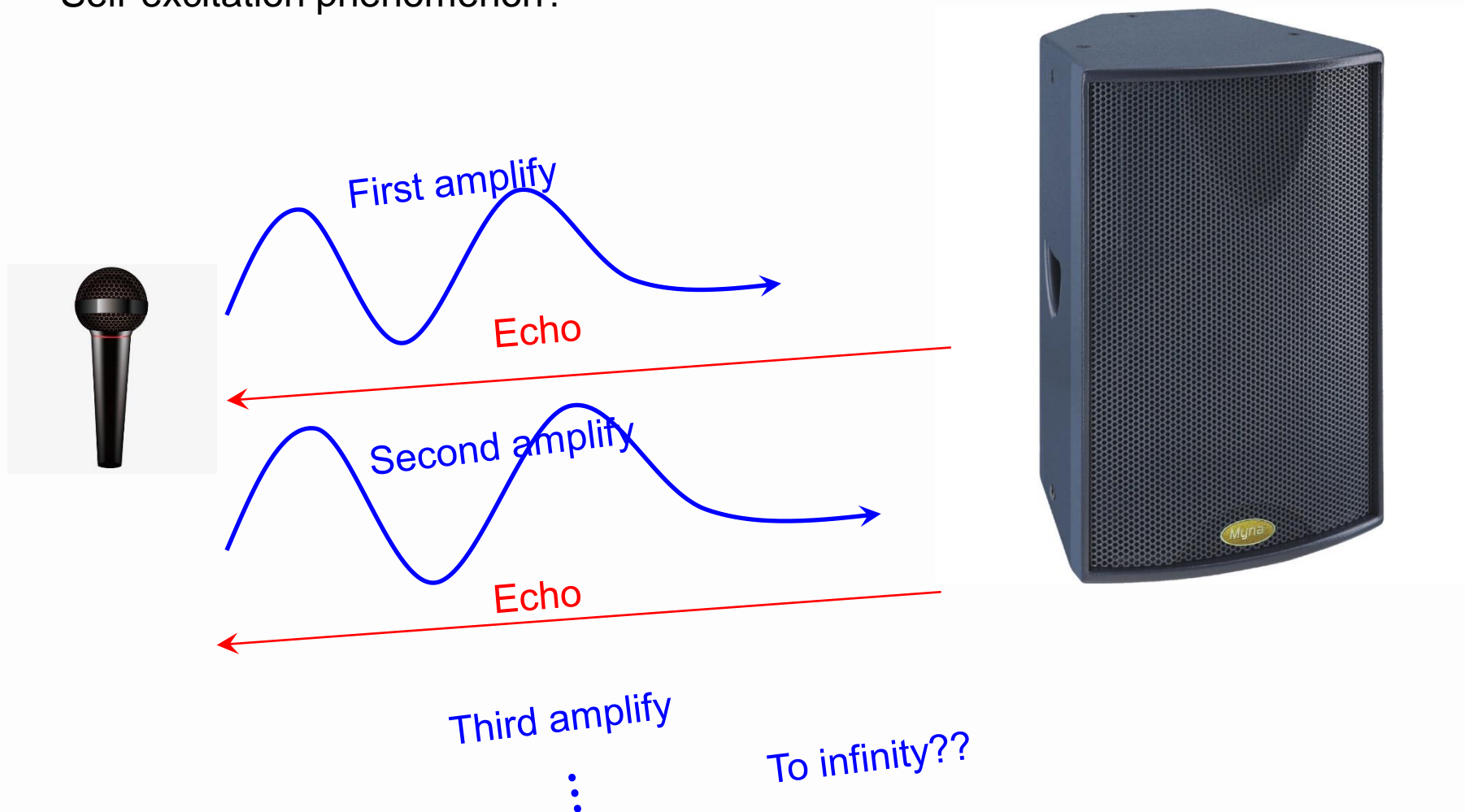

Notice

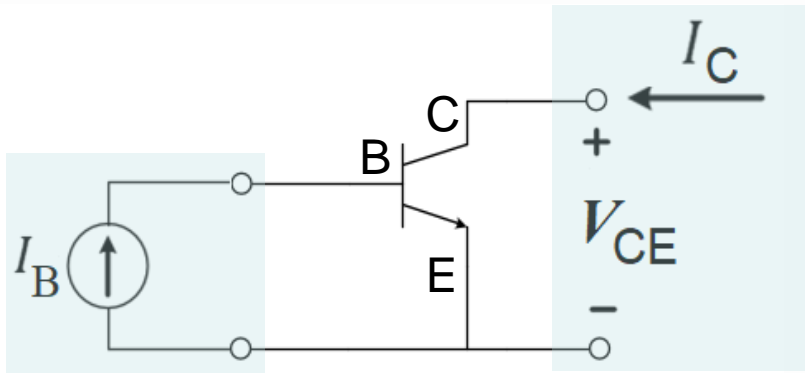

1. Cut-off regime

When $V_{BE} < V_{on}$, thus $I_C \approx 0$

2. Active regime

When $V_{BE} \geq V_{on}$, thus $I_C = \beta I_B$

$V_{CE} > V_{CE,sat}$

3. Saturation regime


When $V_{BE} \geq V_{on}$, and $V_{CE} = V_{CE,sat}$

$I_C = I_{C,sat}$

Calculating V_{out} from V_{in} (revisited)

BJT Datasheet:

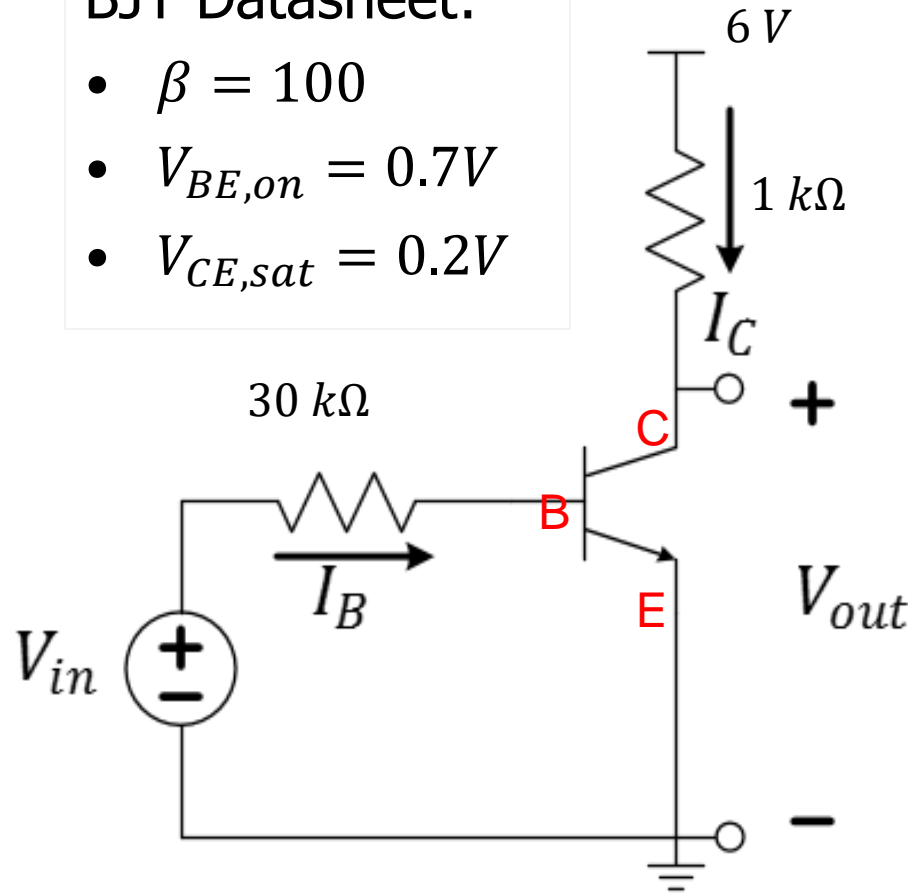- $\beta = 100$
- $V_{BE,on} = 0.7V$
- $V_{CE,sat} = 0.2V$




L21Q1: What is $v_{out} = V_{CE}$ for $V_{IN} = 0.3, 1, 2.5,$ and 3.5 Volts?

CHECK THE $I_{C,sat}$ FIRST

BJT Datasheet:

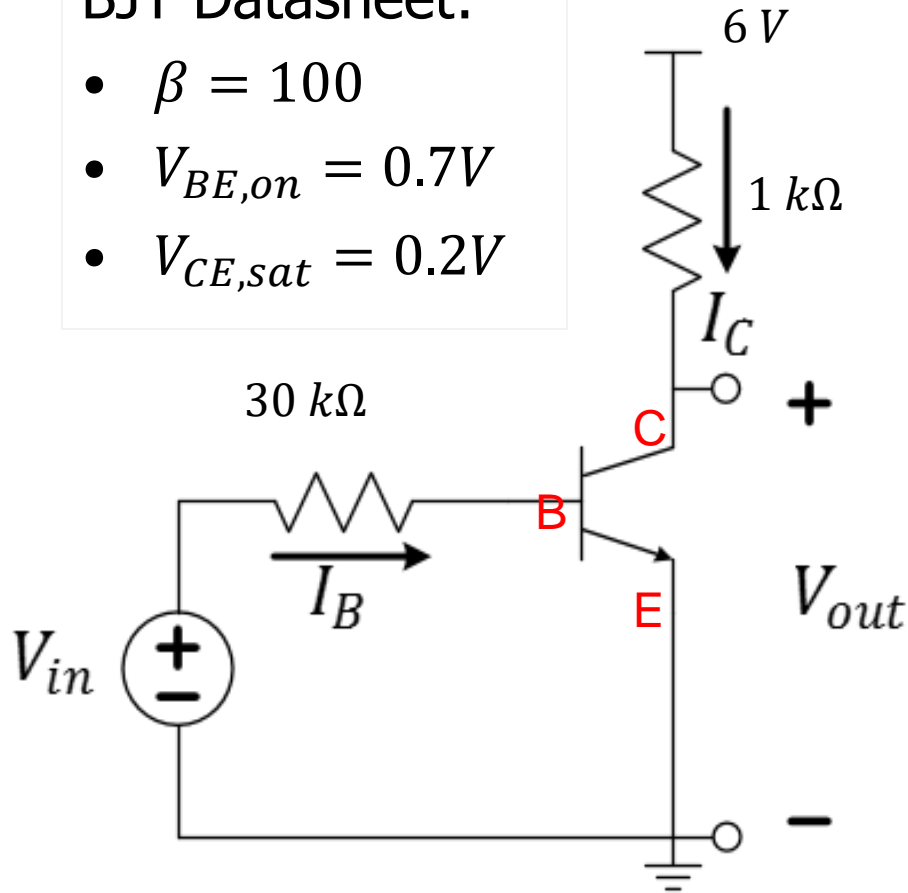- $\beta = 100$
- $V_{BE,on} = 0.7V$
- $V_{CE,sat} = 0.2V$



$$I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C}$$

$$= \frac{6 - 0.2}{1k} = 5.8mA$$

$$I_{B,sat} = \frac{I_{C,sat}}{\beta} = 58\mu A$$


I_B at onset of saturation

L21Q1: What is $v_{out} = V_{CE}$ for $V_{IN} = 0.3, 1, 2.5,$ and 3.5 Volts?

Calculating V_{out} from V_{in} (revisited)

BJT Datasheet:

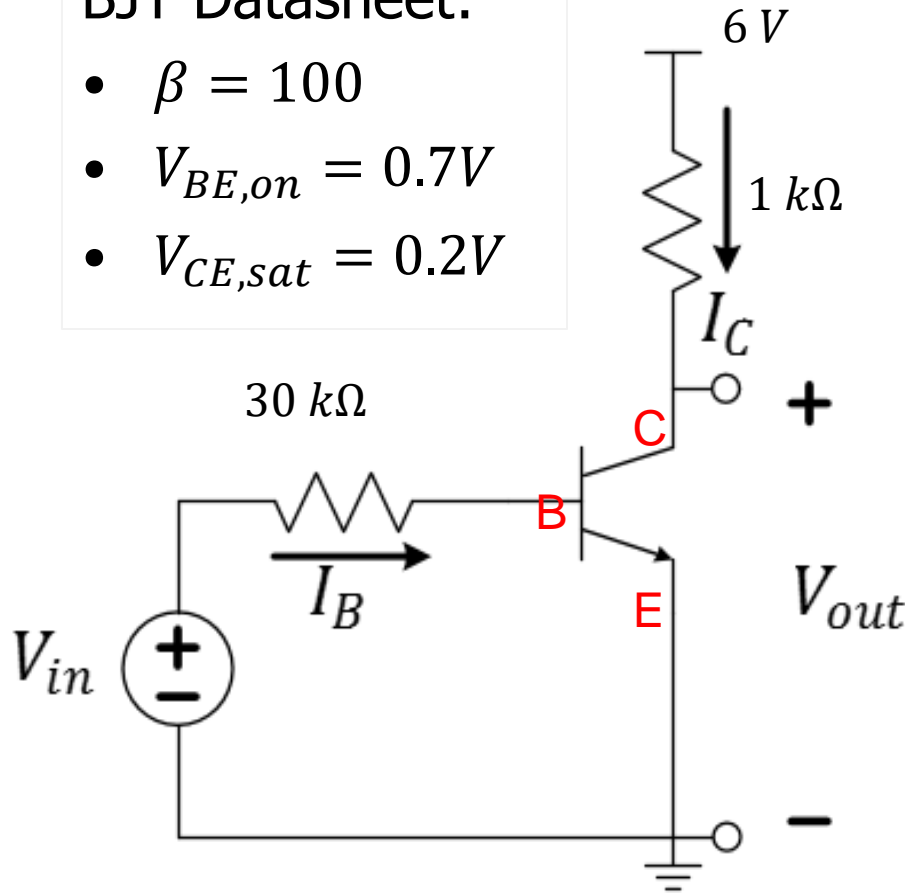- $\beta = 100$
- $V_{BE,on} = 0.7V$
- $V_{CE,sat} = 0.2V$



$$V_{in} = 0.3V$$

$$I_B = 0A$$

$$I_C = 0A$$


$$V_{out} = 6V$$

L21Q1: What is $v_{out} = V_{CE}$ for $V_{IN} = 0.3, 1, 2.5,$ and 3.5 Volts?

Calculating V_{out} from V_{in} (revisited)

BJT Datasheet:

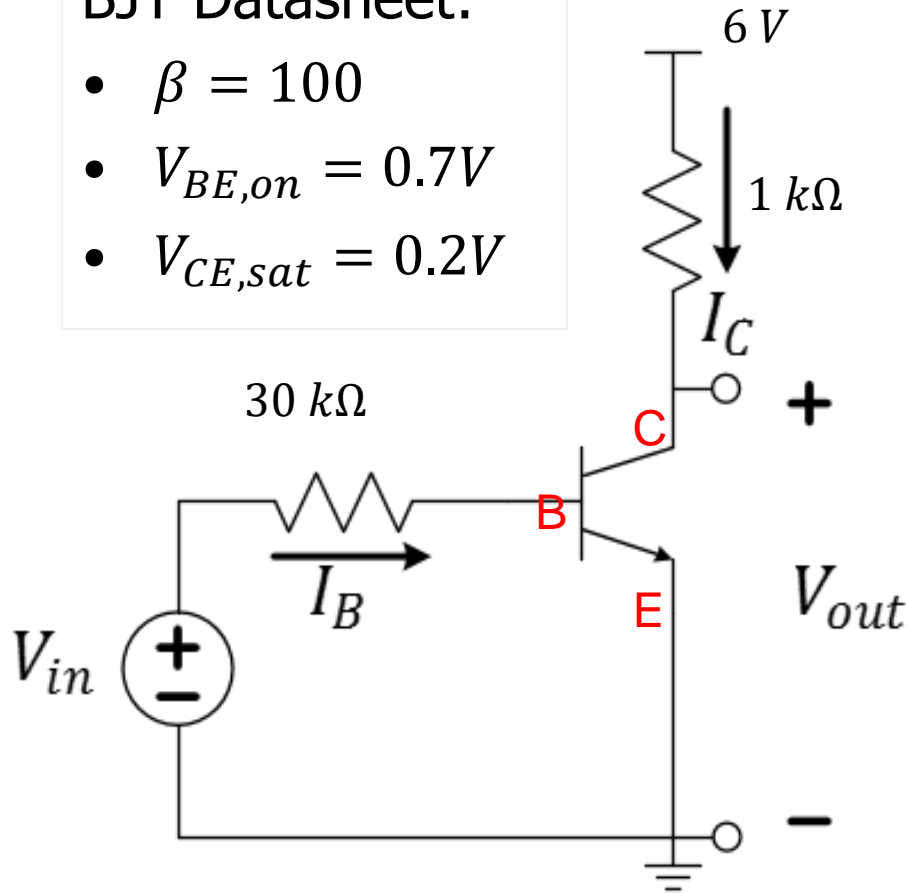- $\beta = 100$
- $V_{BE,on} = 0.7V$
- $V_{CE,sat} = 0.2V$



$$V_{in} = 1V$$

$$I_B = \frac{1 - 0.7}{30k} = 10\mu A$$

$$I_C = \beta I_B = 1mA \quad I_C < I_{C,sat}$$


$$V_{out} = 6 - (1k)(1m) = 5V$$

L21Q1: What is $v_{out} = V_{CE}$ for $V_{IN} = 0.3, 1, 2.5,$ and 3.5 Volts?

Calculating V_{out} from V_{in} (revisited)

BJT Datasheet:

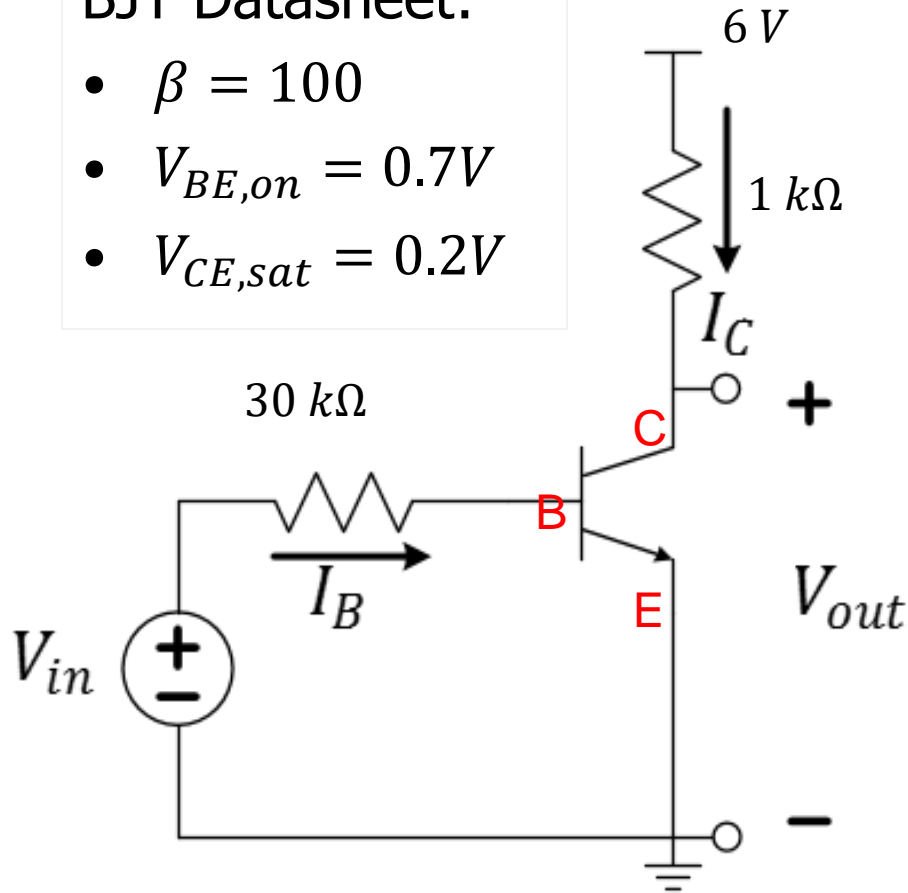- $\beta = 100$
- $V_{BE,on} = 0.7V$
- $V_{CE,sat} = 0.2V$



$$V_{in} = 2.5V$$

$$I_B = \frac{2.5 - 0.7}{30k} = 60\mu A$$

$$I_C = \beta I_B = 6mA > I_{C,sat}$$


$$V_{out} = V_{C,sat} = 0.2V$$

L21Q1: What is $v_{out} = V_{CE}$ for $V_{IN} = 0.3, 1, 2.5$, and 3.5 Volts?

Calculating V_{out} from V_{in} (revisited)

BJT Datasheet:

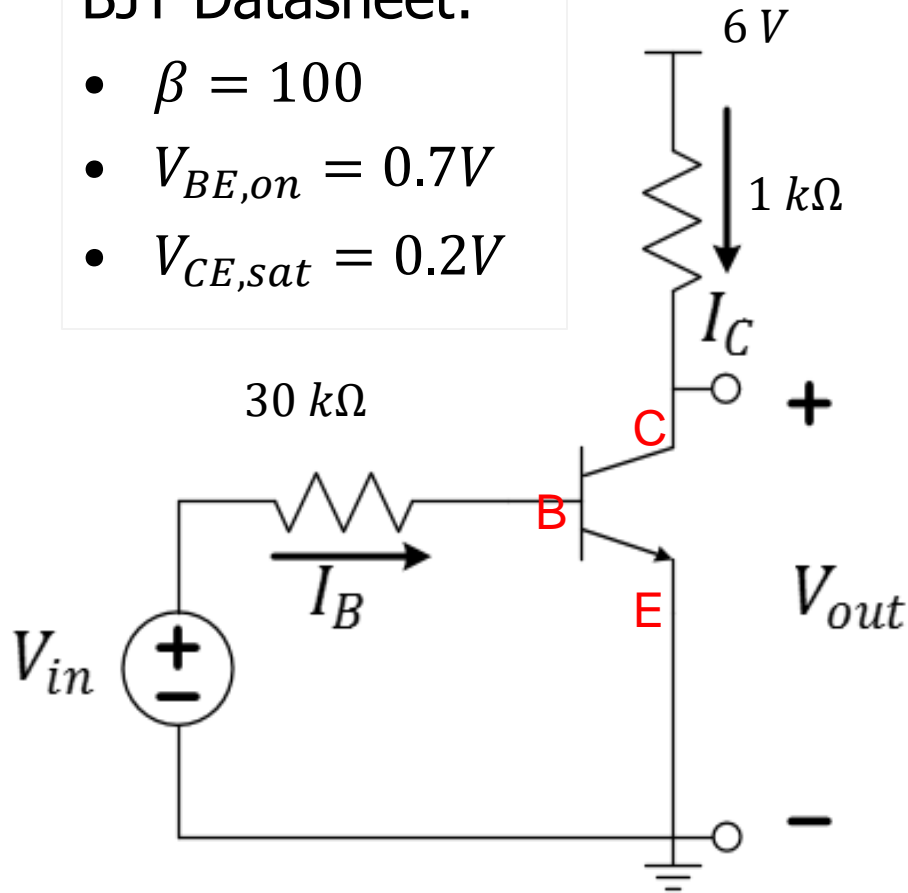- $\beta = 100$
- $V_{BE,on} = 0.7V$
- $V_{CE,sat} = 0.2V$



$$V_{in} = 3.5V$$


$$I_B = \frac{3.5 - 0.7}{30k} = 93\mu A$$

$$I_C = \beta I_B = 9.3mA > I_{C,sat}$$

$$V_{out} = V_{C,sat} = 0.2V$$

L21Q1: What is $v_{out} = V_{CE}$ for $V_{IN} = 0.3, 1, 2.5$, and 3.5 Volts?

Review of BJT operating regimes

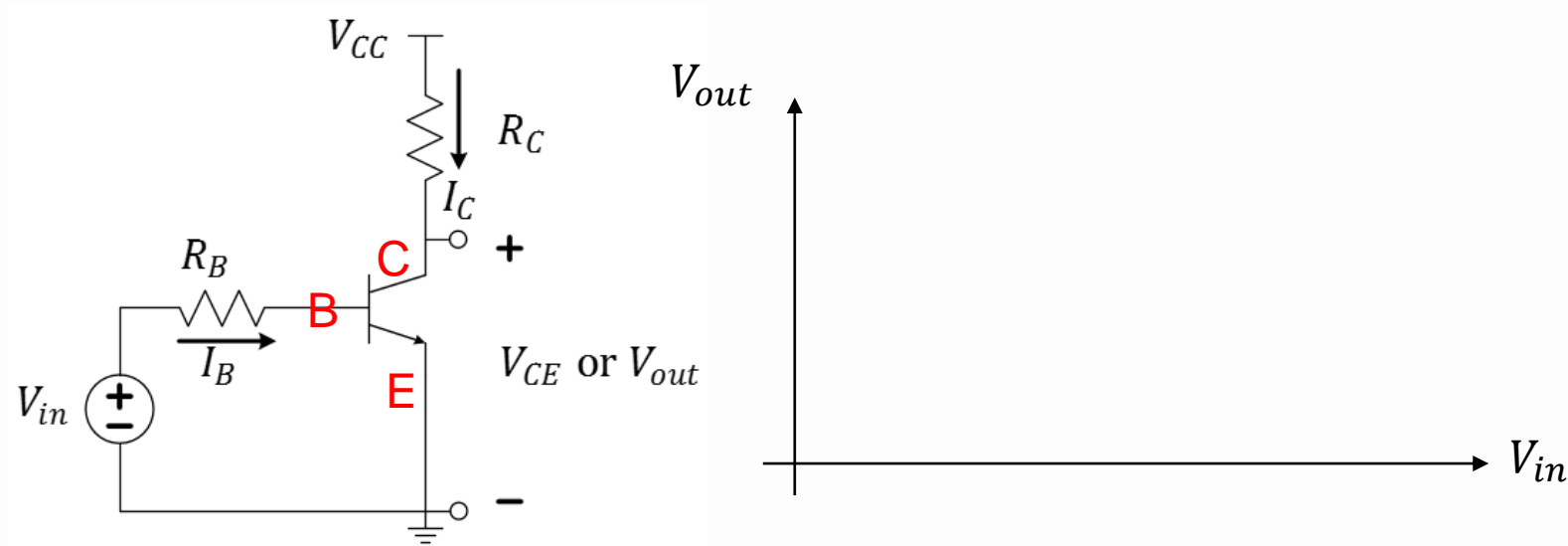

$$A. \quad V_{in} = \frac{V_{CC} - V_{CE,sat}}{R_C}$$

$$B. \quad V_{in} = V_{CC} + V_{BEon}$$

$$C. \quad V_{in} = V_{CE,sat} + I_B R_B$$



$$D. \quad V_{in} = V_{CC} - I_C R_C + I_B R_B$$

$$E. \quad V_{in} = V_{BEon} + \frac{R_B}{\beta R_C} (V_{CC} - V_{CE,sat})$$

Regime	V_{in}	I_B	I_C	V_C

L21Q2: What is the formula for minimum V_{IN} which causes saturation?

Review of BJT operating regimes

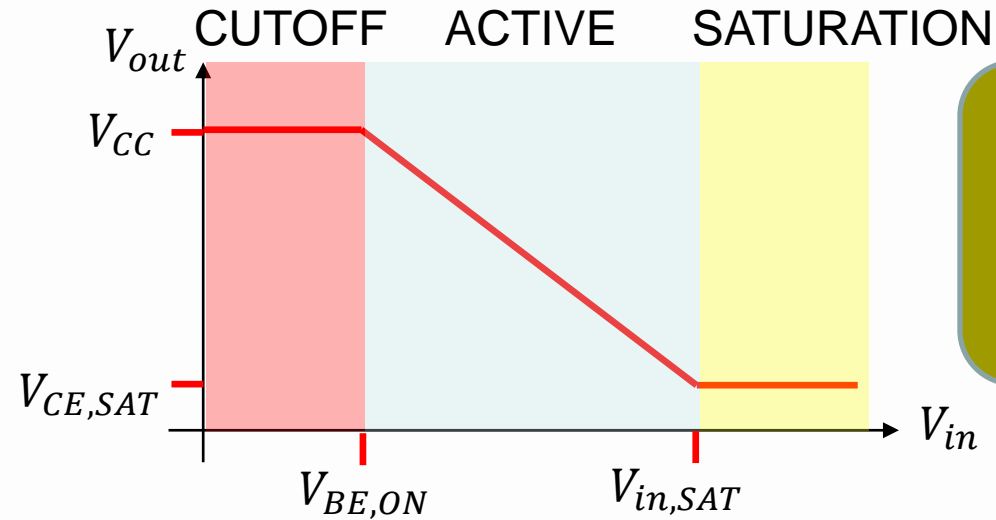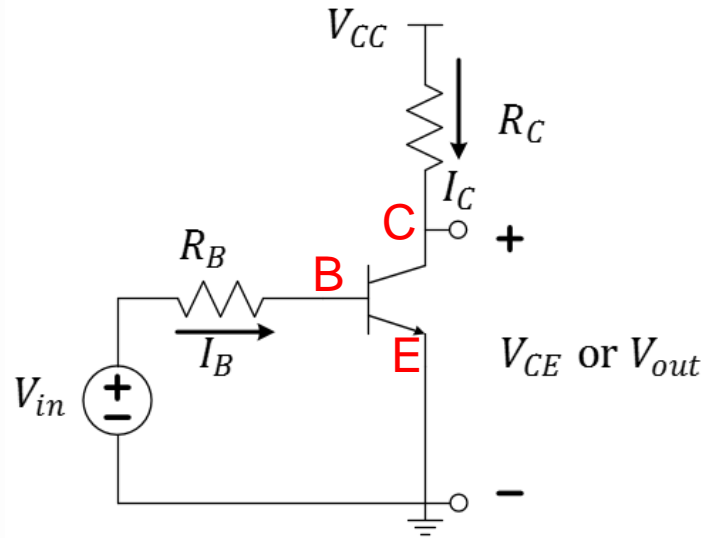

In active regime


$$V_{in} \uparrow \Rightarrow I_B \uparrow$$

$$\Rightarrow I_C \uparrow \Rightarrow V_{out} \downarrow$$

Regime	V_{in}	I_B	I_C	V_{CE}
CUTOFF	$V_{in} < V_{BE,ON}$	0	0	V_{CC}
ACTIVE	$V_{BE,ON} \leq V_{in} \leq V_{in,SAT}$	$(V_{in} - V_{BE,ON})/R_B$	$I_C = \beta I_B$	$V_{CC} - R_C I_C$
SATURATION	$V_{in} > V_{in,SAT}$	$(V_{in} - V_{BE,ON})/R_B$	$I_{CE,SAT}$	$V_{CE,SAT}$

What's the value of $V_{in,sat}$?

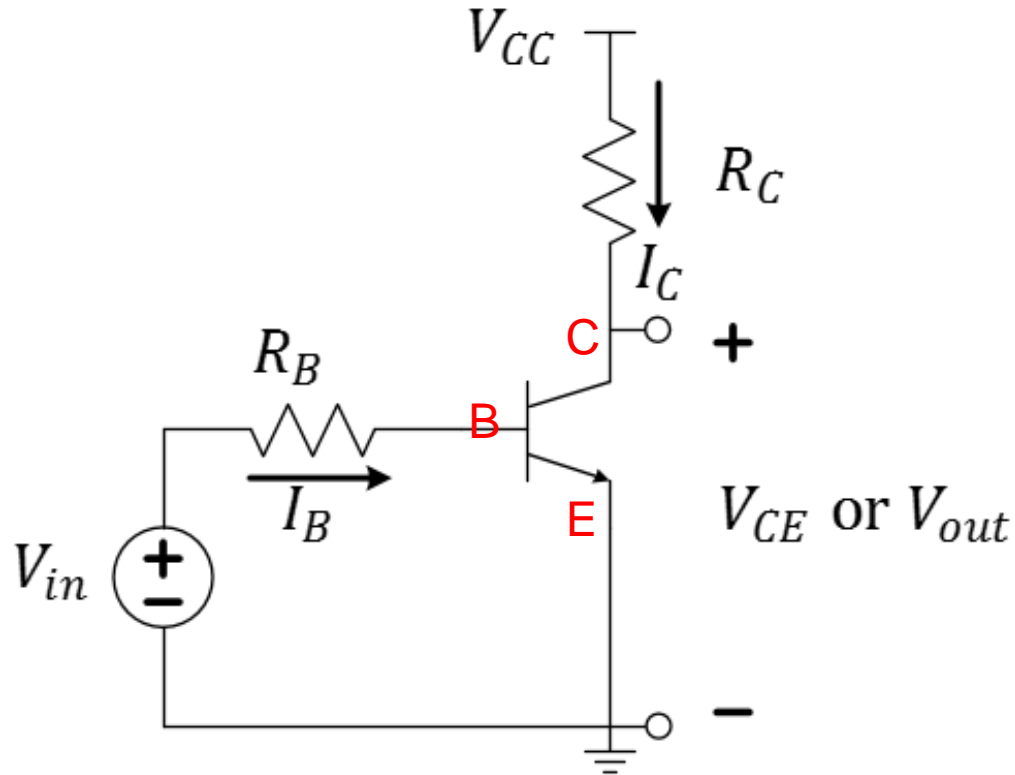L21Q2: What is the formula for minimum V_{IN} which causes saturation?



A. $V_{in} = \frac{V_{CC} - V_{CE,sat}}{R_C}$

B. $V_{in} = V_{CC} + V_{BEon}$



C. $V_{in} = V_{CE,sat} + I_B R_B$

D. $V_{in} = V_{CC} - I_C R_C + I_B R_B$

E. $V_{in} = V_{BEon} + \frac{R_B}{\beta R_C} (V_{CC} - V_{CE,sat})$

$$V_{in,sat} = V_{BEon} + R_B \times \frac{I_C}{\beta} = V_{BEon} + R_B \times \frac{1}{\beta} \times \frac{V_{CC} - V_{CE,sat}}{R_C} = V_{BEon} + R_B \times \frac{I_{C,sat}}{\beta} = V_{BEon} + R_B \times I_{B,sat}$$


Voltage transfer characteristics

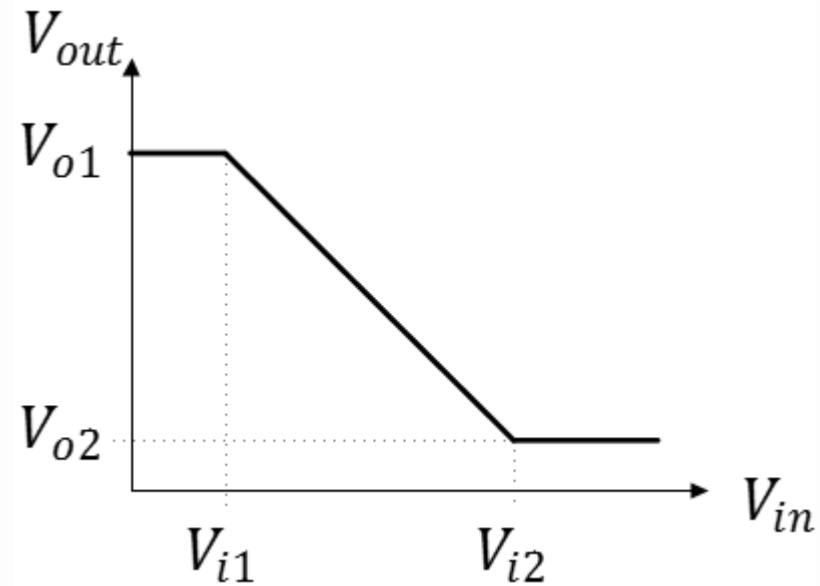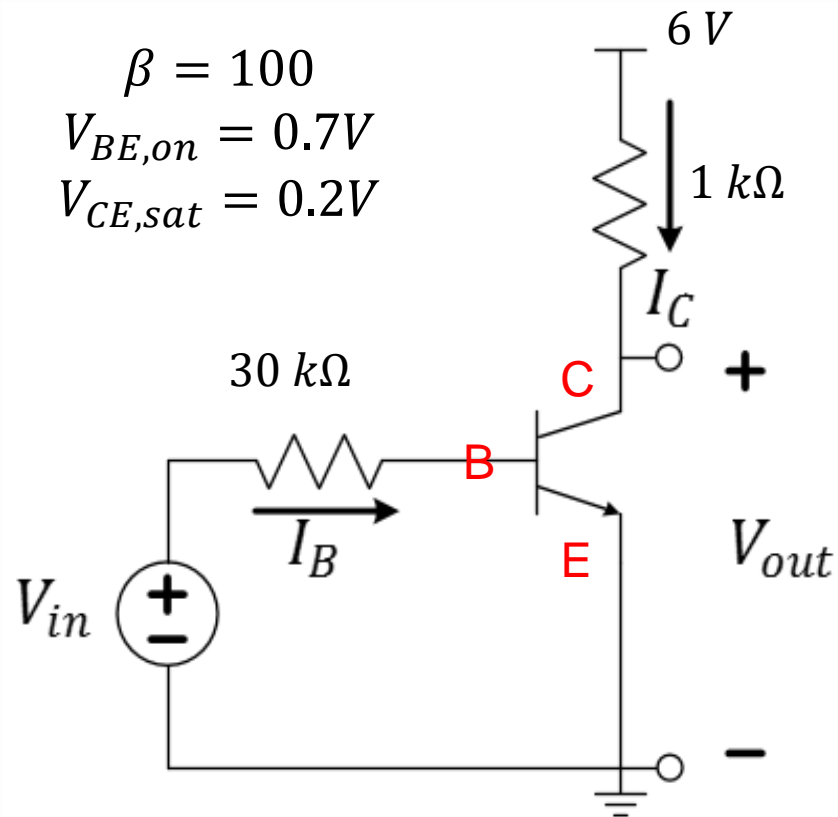

L21Q3: What are the four values V_{o1} , V_{o2} , V_{i1} , V_{i2} ?

L21Q4: What is the $\frac{\Delta V_{out}}{\Delta V_{in}}$ slope in the active region?

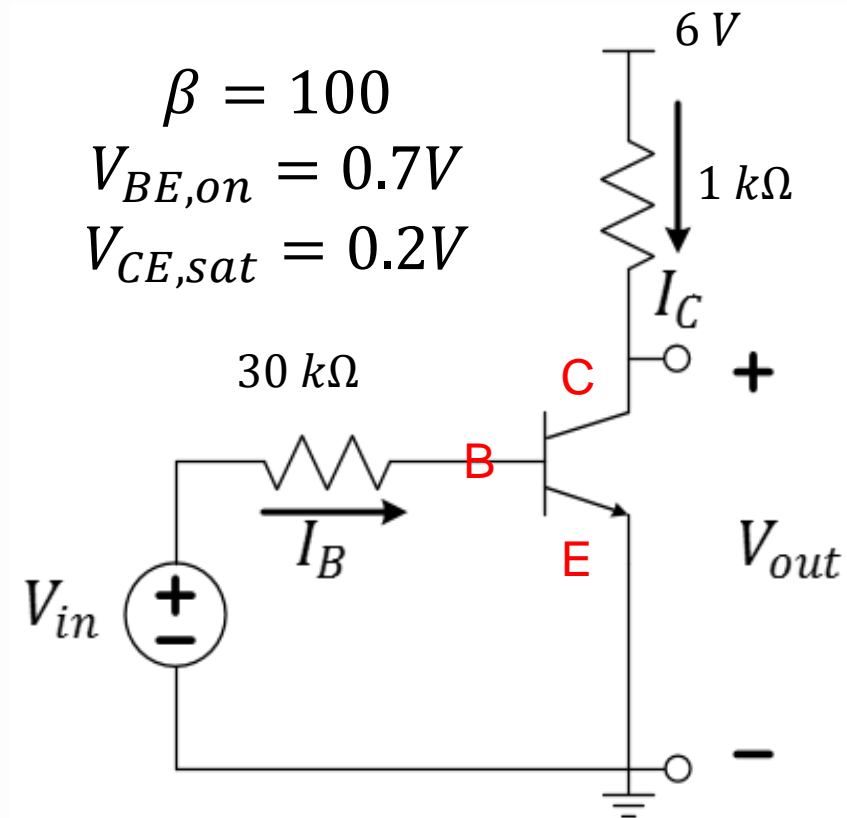
L21Q3: What are the four values $V_{o1}, V_{o2}, V_{i1}, V_{i2}$?



$$V_{o1} = V_{CC} = 6V$$

$$V_{o2} = V_{CE,sat} = 0.2V$$


$$V_{i1} = V_{BE,on} = 0.7V$$

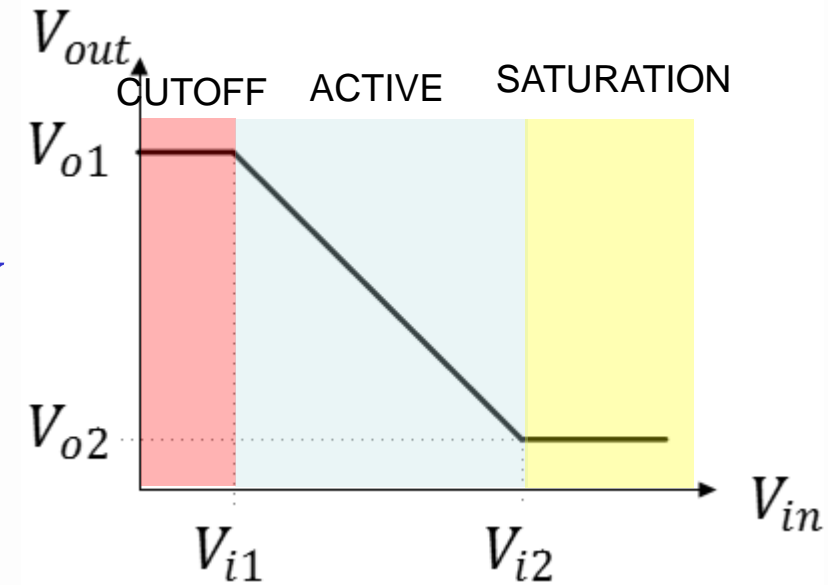

$$\begin{aligned}
 V_{i,2} &= V_{BEon} + \frac{R_B}{\beta R_C} (V_{CC} - V_{CE,sat}) = 0.7 + \frac{30k}{(100)(1k)} (6 - 0.2) \\
 &= 2.44V
 \end{aligned}$$

L21Q4: What is the $\frac{\Delta V_{out}}{\Delta V_{in}}$ slope in the active region?
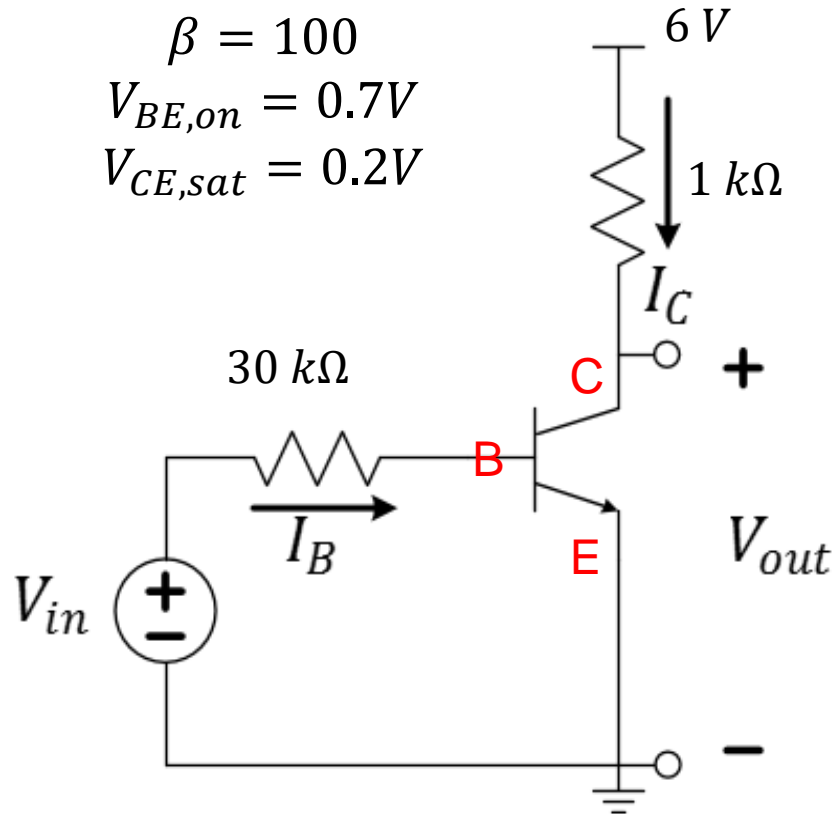
$$\begin{aligned}\beta &= 100 \\ V_{BE,on} &= 0.7V \\ V_{CE,sat} &= 0.2V\end{aligned}$$




$$V_{o1} = 6V$$

$$V_{o2} = 0.2V$$

$$V_{i1} = 0.7V$$


$$V_{i2} = 2.44V$$
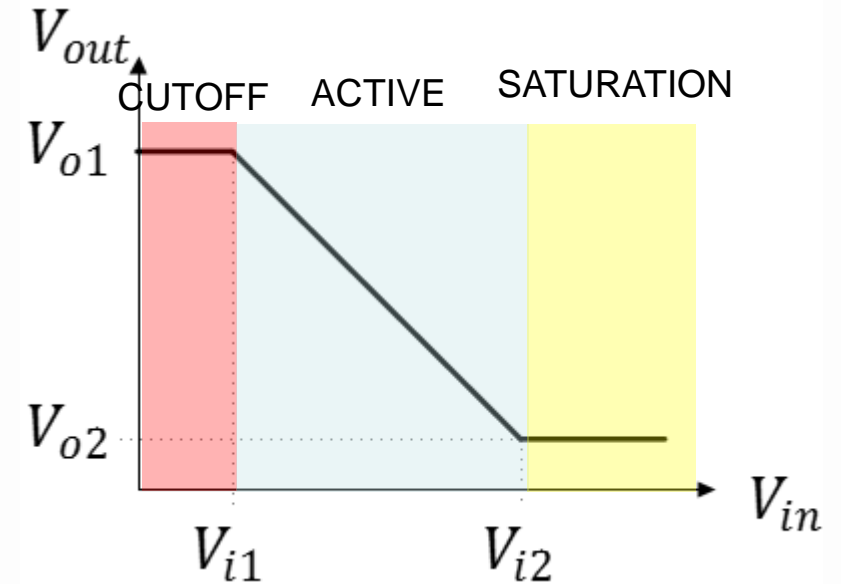
$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{V_{o2} - V_{o1}}{V_{i2} - V_{i1}} = \frac{0.2 - 6}{2.44 - 0.7} = -3.\bar{3}$$



MORE on incremental Voltage Gain
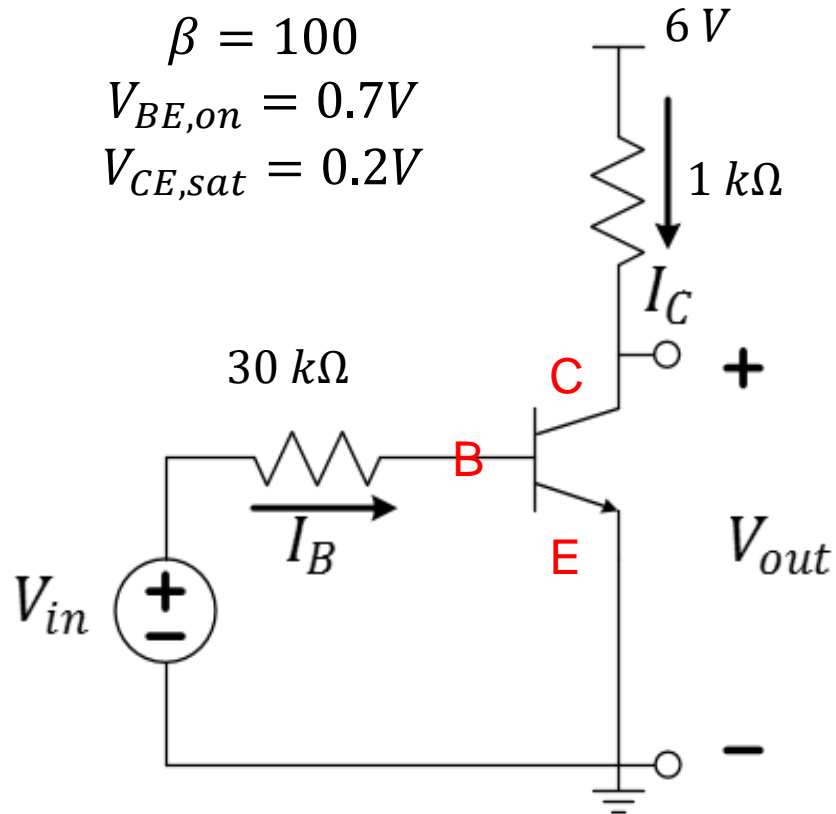
$$\begin{aligned}\beta &= 100 \\ V_{BE,on} &= 0.7V \\ V_{CE,sat} &= 0.2V\end{aligned}$$




$$G_V = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{-\Delta I_C R_C}{\Delta I_B R_B} = -\beta \frac{R_C}{R_B}$$

$$G_V = -\beta \frac{R_C}{R_B} = -100 \frac{1k}{30k} = -3.\bar{3}$$

Same as previous result

$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{V_{o2} - V_{o1}}{V_{i2} - V_{i1}} = -3.\bar{3}$$

Active regime for signal amplification

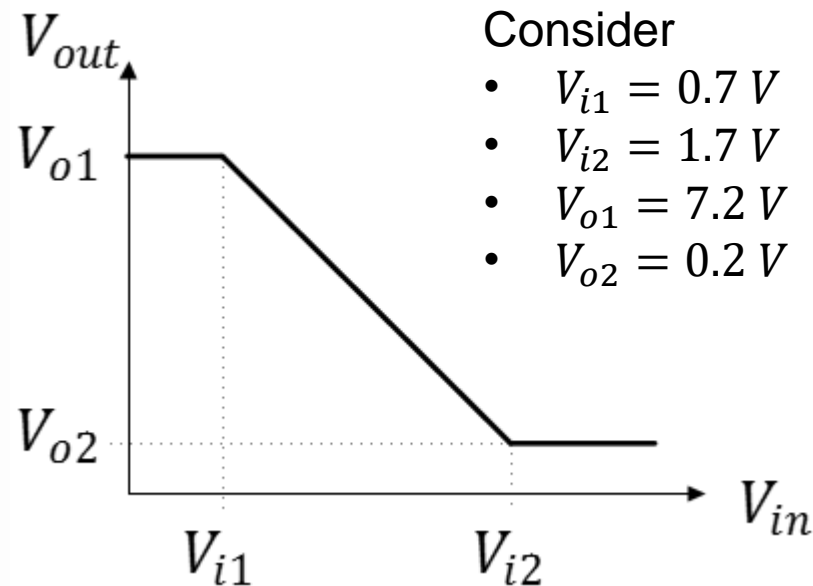

Q7:


- A. Active only
- B. Cutoff and active
- C. Active and saturation
- D. Saturation only
- E. Cutoff, active, and saturation

L21Q5: If $V_{IN} = 1.2 + 0.2\cos(2\pi 100t)$ what is the equation for V_{out} ?

L21Q6: What is different if $V_{in} = 1.2 + 0.6\cos(2\pi 100t)$?


L21Q7: What transistor regimes are entered if $V_{in} = 1.1 + 0.3\cos(\omega t)$?

What is the Voltage Gain?

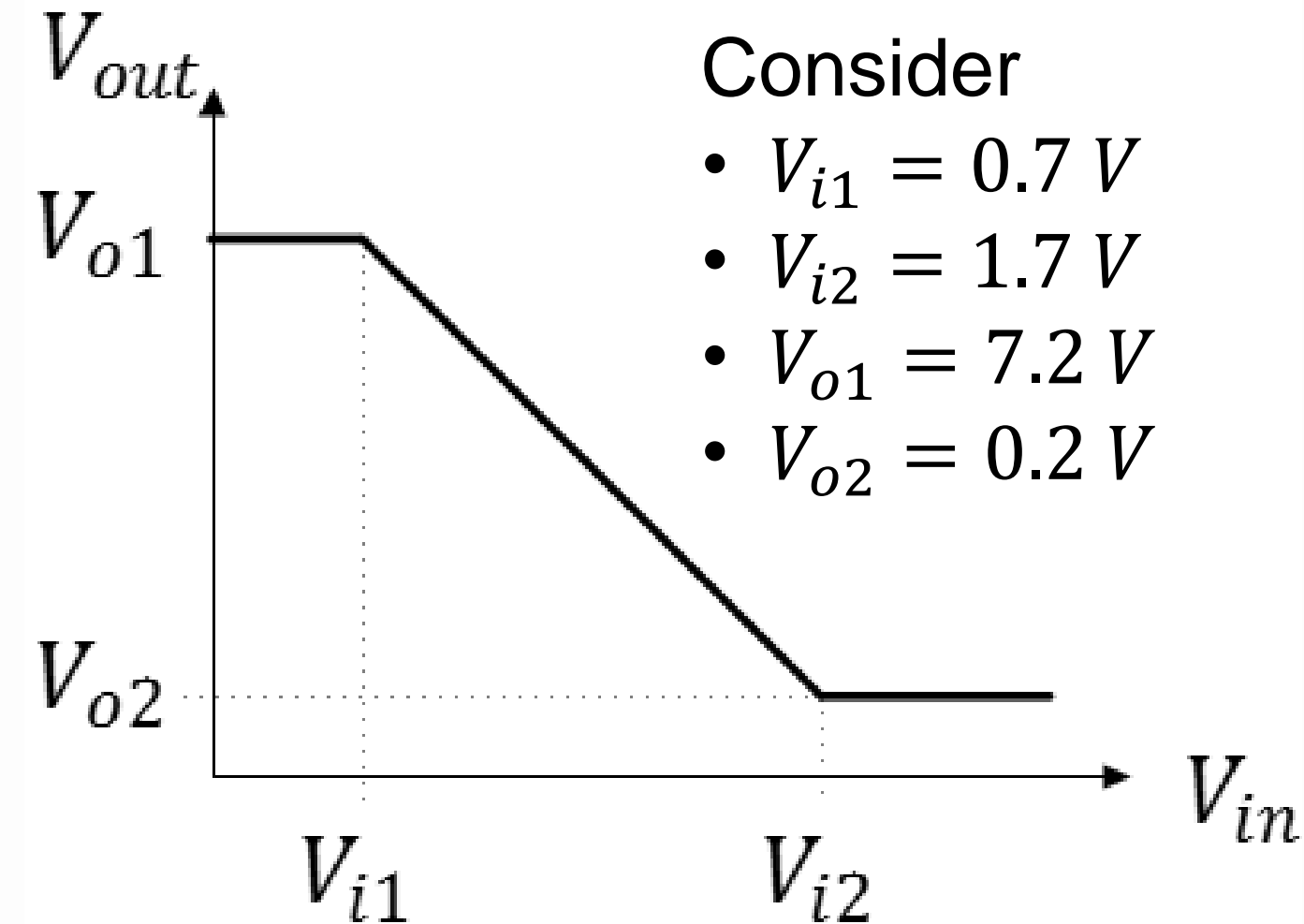

What is the Voltage Gain?

Voltage gain is not β

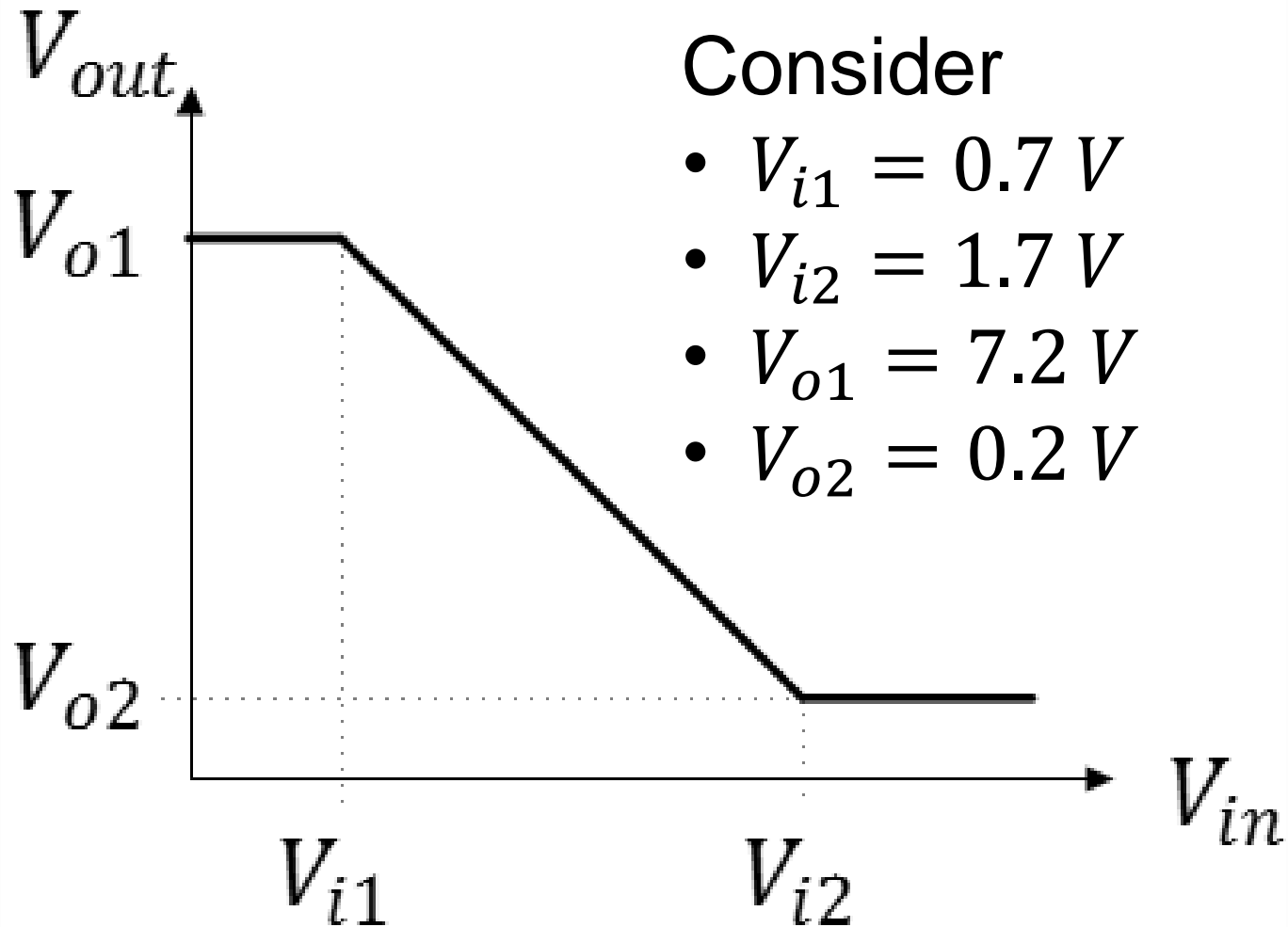


$$G_V = \frac{V_{o2} - V_{o1}}{V_{i2} - V_{i1}}$$

$$G_V = \frac{0.2 - 7.2}{1.7 - 0.7} = -7$$

$$V_{out} = G_V(V_{in} - V_{i1}) + V_{o1}$$

$$V_{out} = G_V(V_{in} - V_{i2}) + V_{o2}$$

Find the formula for V_{out}

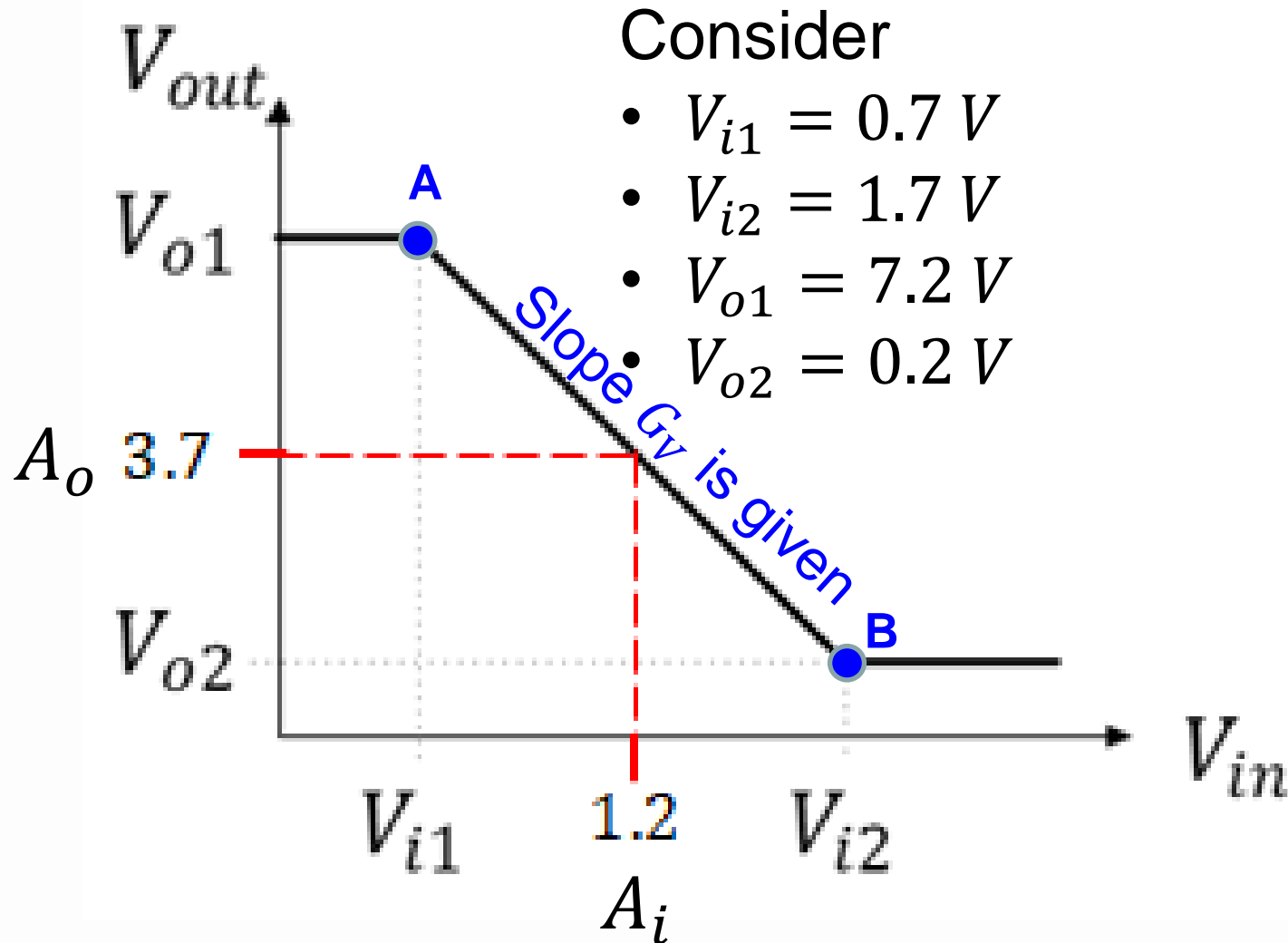

$$V_{IN}(t) = A_i + B_i \cos(\omega t)$$

$$V_{out}(t) = A_o + B_o \cos(\omega t)$$


~~$$A_o = V_{o2} + G_V(V_{i1} - A_i)$$~~

$$A_o = V_{o2} + G_V(A_i - V_{i2})$$

For this specific problem

$$A_o = 0.2 - 7(0.7 - 1.2) = 3.7 \text{ V}$$

Find the formula for V_{out}

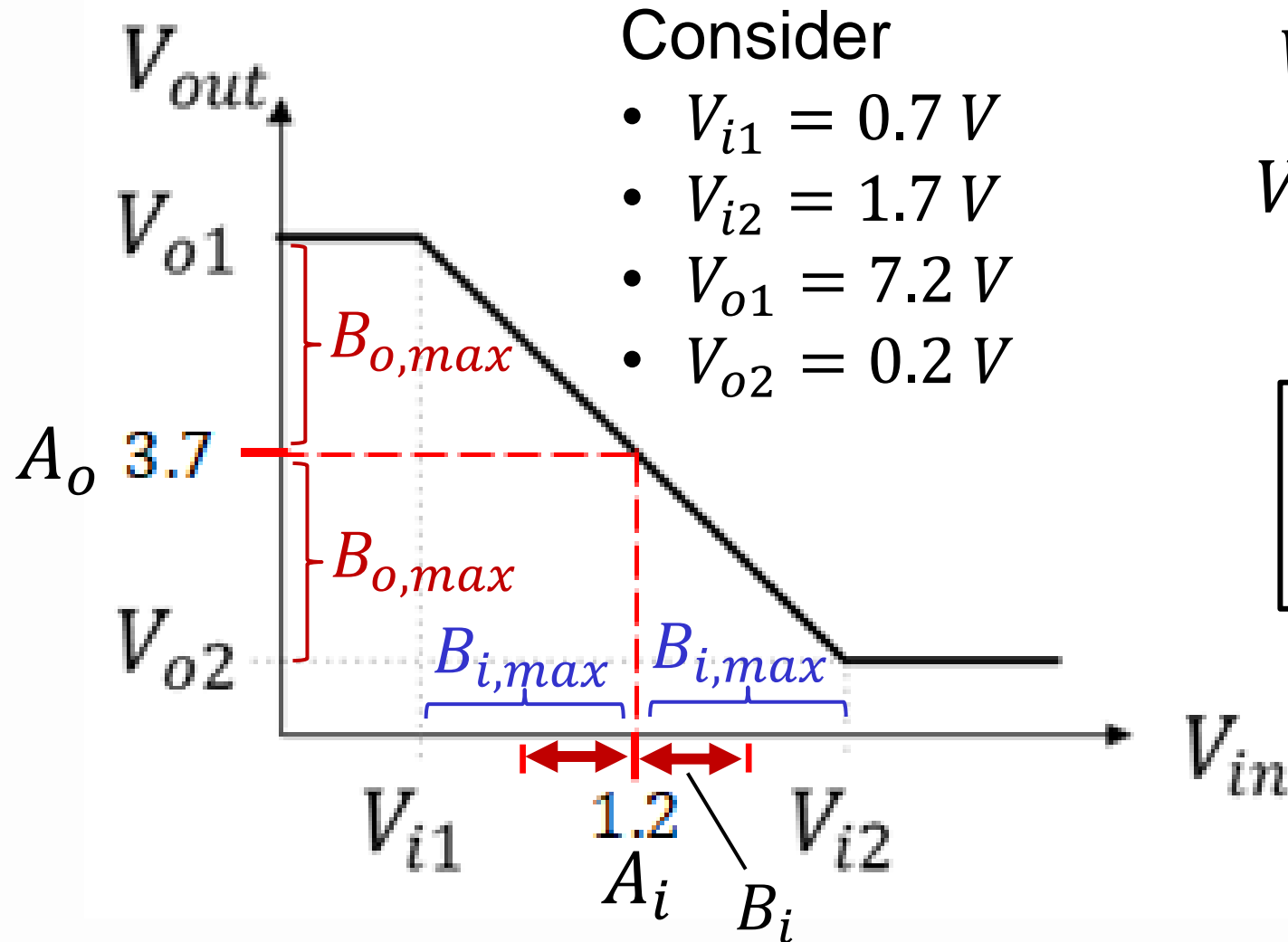

Consider


- $V_{i1} = 0.7 \text{ V}$
- $V_{i2} = 1.7 \text{ V}$
- $V_{o1} = 7.2 \text{ V}$
- $V_{o2} = 0.2 \text{ V}$

$$V_{IN}(t) = A_i + B_i \cos(\omega t)$$

$$V_{out}(t) = A_o + B_o \cos(\omega t)$$

$B_{i,max}$ & $B_{o,max}$
Limits for Active Region

Find the formula for V_{out}

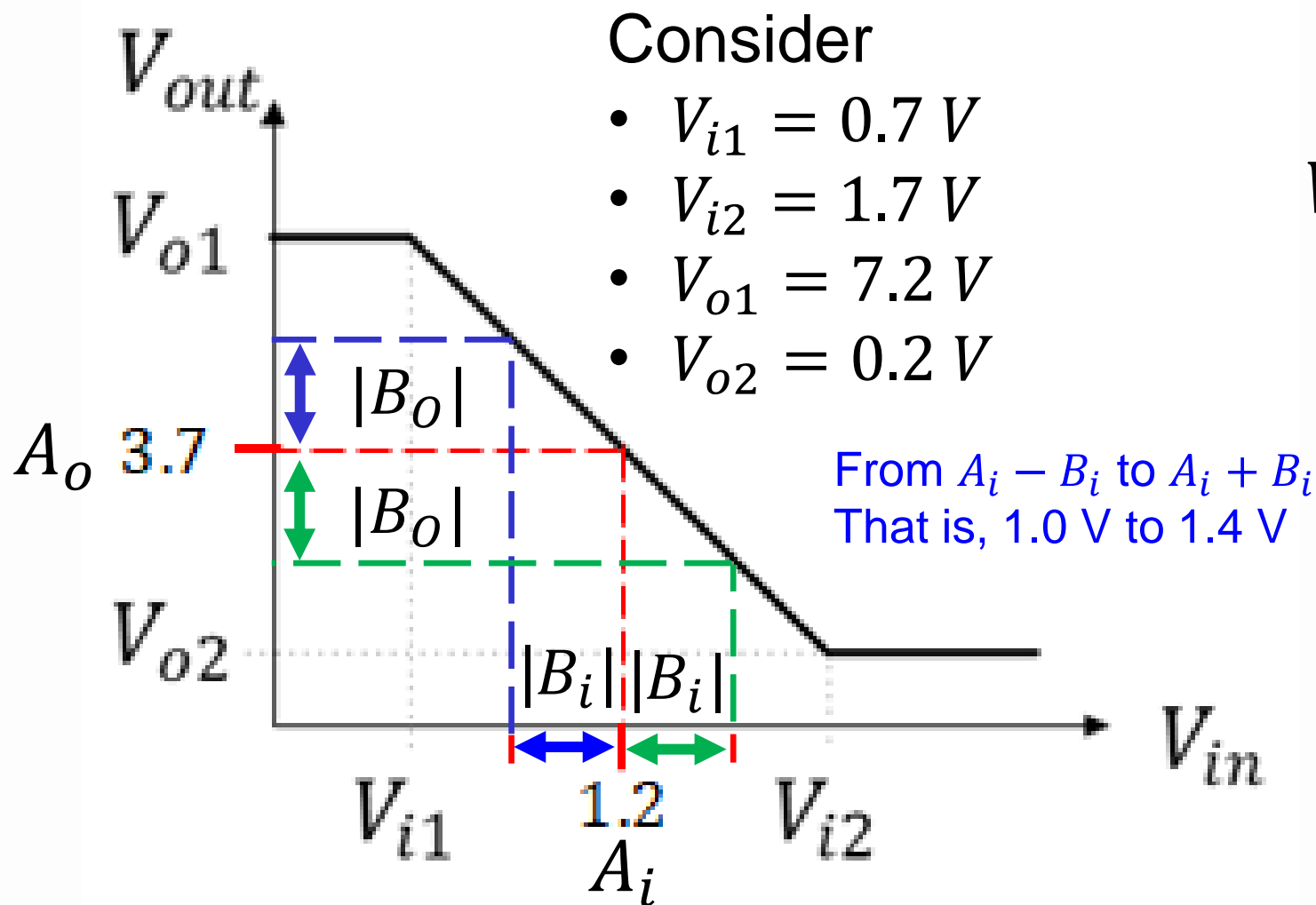

$$V_{IN}(t) = A_i + B_i \cos(\omega t)$$

$$V_{out}(t) = A_o + B_o \cos(\omega t)$$



$$B_o = G_V B_i$$

For this specific problem

$$B_i = 0.2$$


$$B_o = -7B_i = -1.4$$

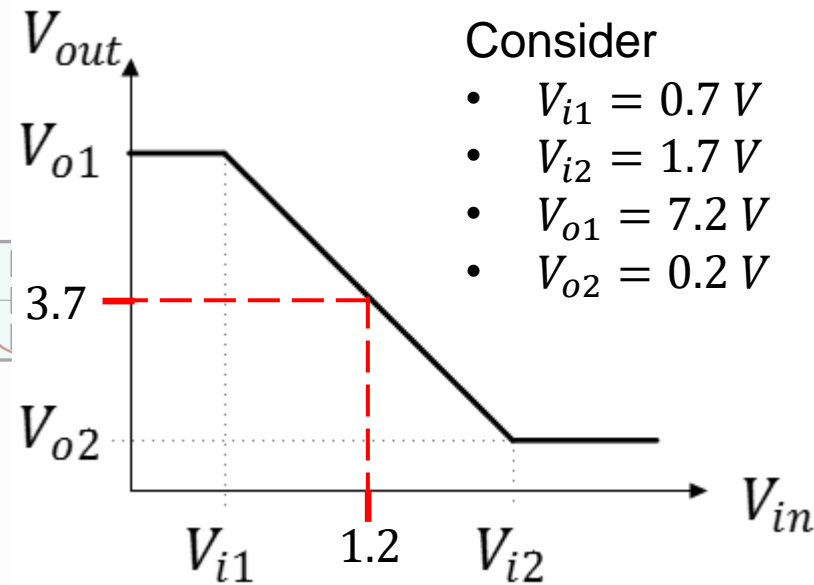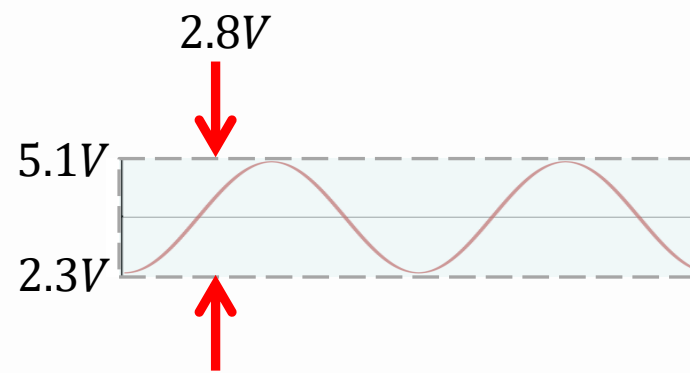L21Q5: If $V_{IN} = 1.2 + 0.2\cos(2\pi 100t)$ what is the equation for V_{out} ?






$$V_{IN} = 1.2 + 0.2\cos(2\pi 100t)$$

$$V_{OUT} = 3.7 - 1.4\cos(2\pi 100t)$$

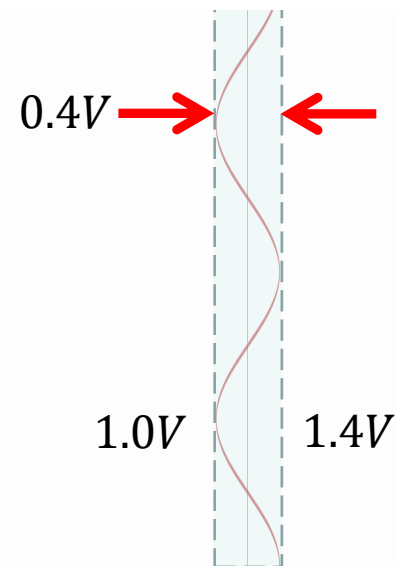

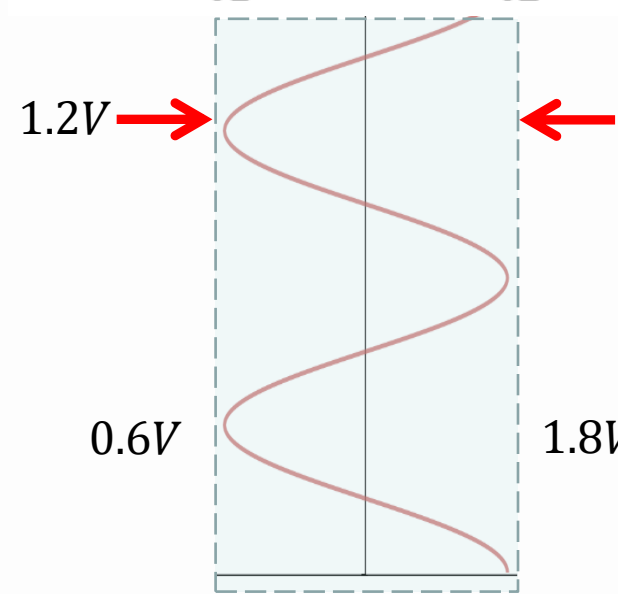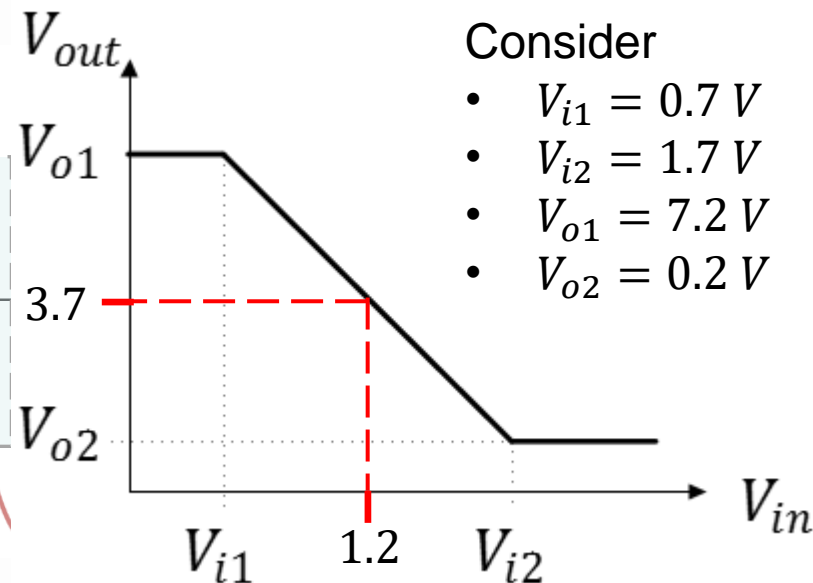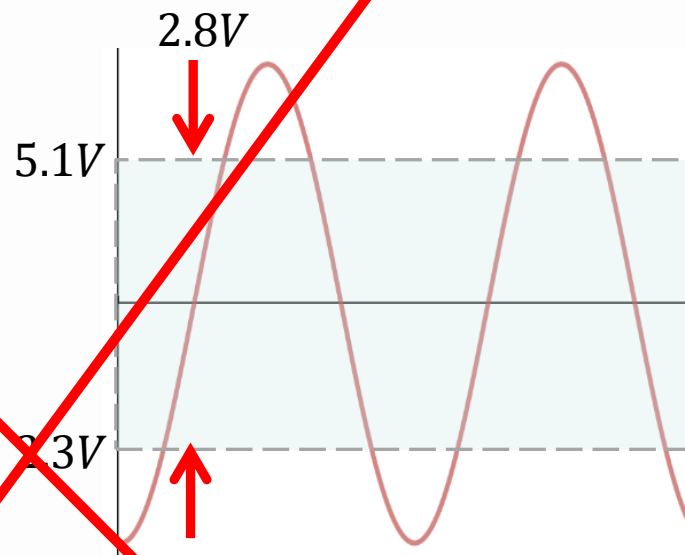L21Q6: If $V_{IN} = 1.2 + 0.6\cos(2\pi 100t)$ what is the equation for V_{out} ?



$$V_{IN} = 1.2 + 0.6\cos(2\pi 100t)$$

$$V_{OUT} = 2.3$$

$$\{V_{in} \leq 0.7V\}$$


$$V_{OUT} = 3.7 - 4.2\cos(2\pi 100t) \quad \{2.3 \geq V_{out} \leq 5.1V\}$$

$$V_{OUT} = 5.1V$$

$$\{V_{in} \geq 1.7V\}$$

L21Q6: If $V_{IN} = 1.2 + 0.6\cos(2\pi 100t)$ what is the equation for V_{out} ?

$$G_V = -7$$

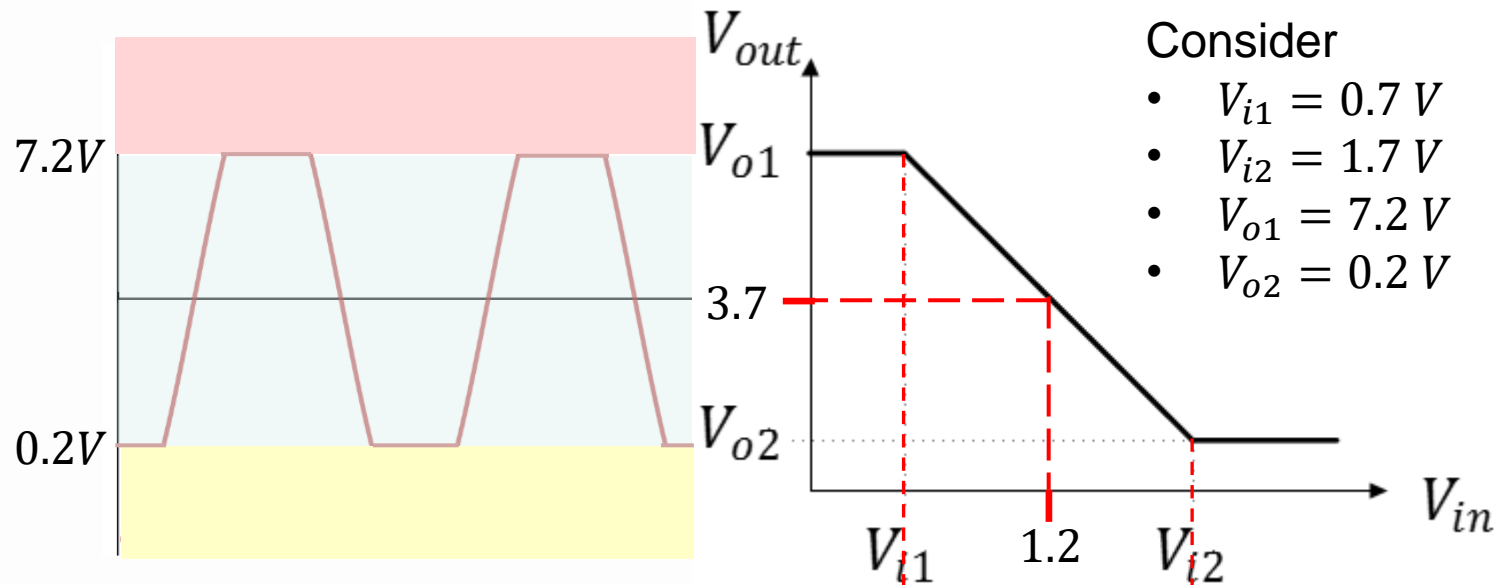

Consider


- $V_{i1} = 0.7V$
- $V_{i2} = 1.7V$
- $V_{o1} = 7.2V$
- $V_{o2} = 0.2V$

$$V_{IN} = 1.2 + 0.6\cos(2\pi 100t)$$

$$V_{OUT} = 7.2V \quad \{V_{in} \leq 0.7V\}$$


$$V_{OUT} = 3.7 - 4.2\cos(2\pi 100t) \quad \{0.7 \leq V_{in} \leq 1.7V\}$$
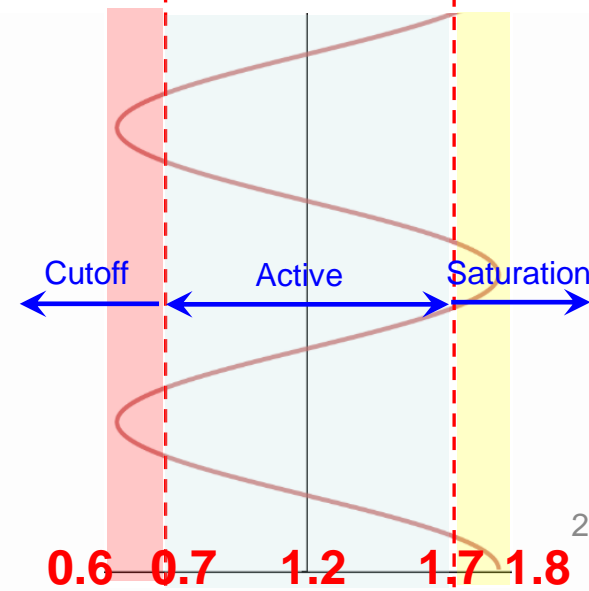
$$V_{OUT} = 0.2V \quad \{V_{in} \geq 1.7V\}$$



L21Q7: What transistor regimes are entered if

$$V_{in} = 1.1 + 0.3\cos(\omega t)?$$

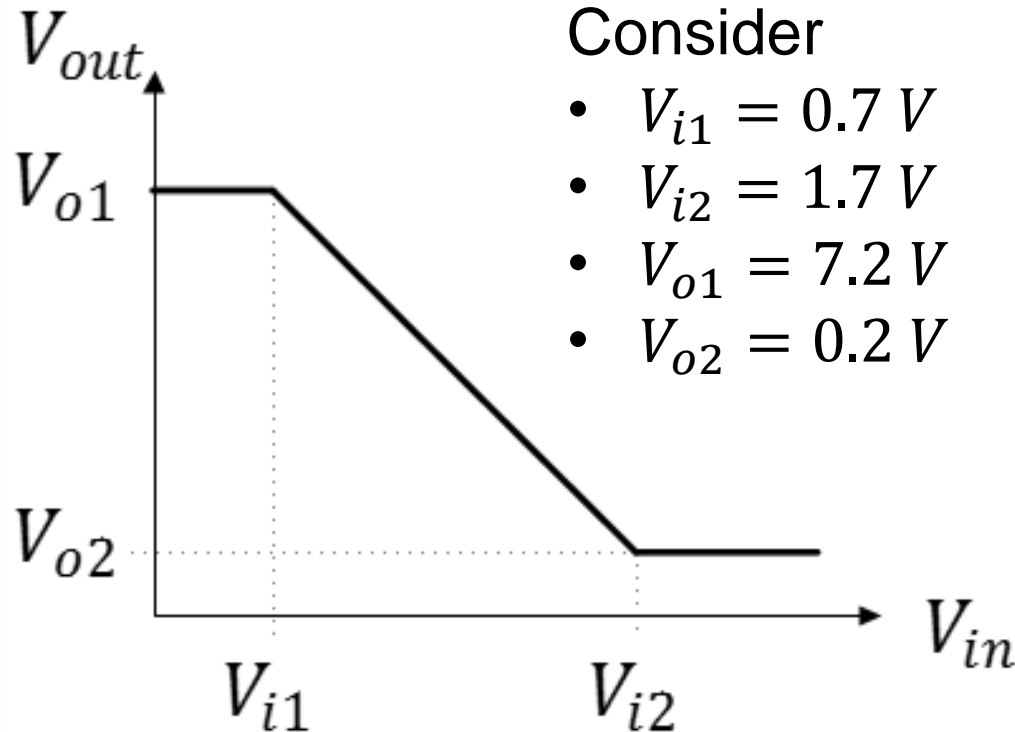

Q7:

- A. Active only
- B. Cutoff and active
- C. Active and saturation
- D. Saturation only
- E. Cutoff, active, and saturation

$$V_{in,min} = 1.1 - 0.3 = 0.8\text{ V} > V_{i1}$$

$$V_{in,max} = 1.1 + 0.3 = 1.4\text{ V} < V_{i2}$$



MORE About current in BJTs

- In the Active Region $I_C = \beta I_B$
- The KVL for a BJT $I_C + I_B - I_E = 0$
- Combine the two expressions to obtain


$$I_E = (1 + \beta)I_B$$

$$I_C = \frac{\beta}{1 + \beta} I_E \quad \text{where} \quad \alpha = \frac{\beta}{1 + \beta} \quad \Rightarrow \quad I_C = \alpha I_E$$

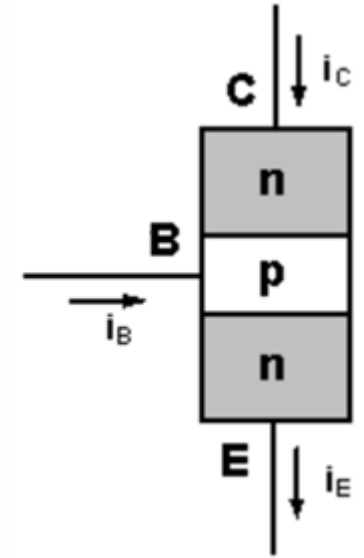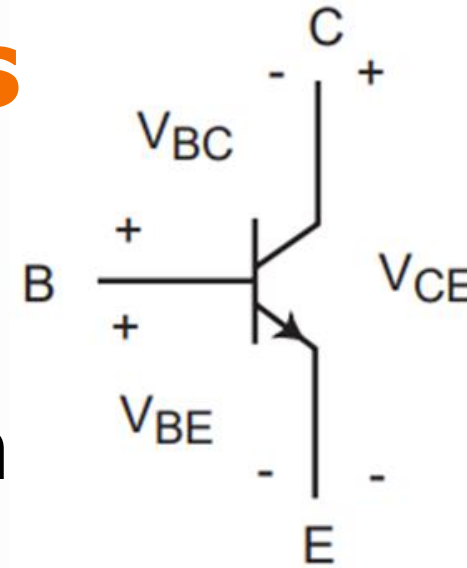- α quantifies the % of electrons originating from the emitter which are able to reach the collector




MORE on BJT common emitter amplifiers

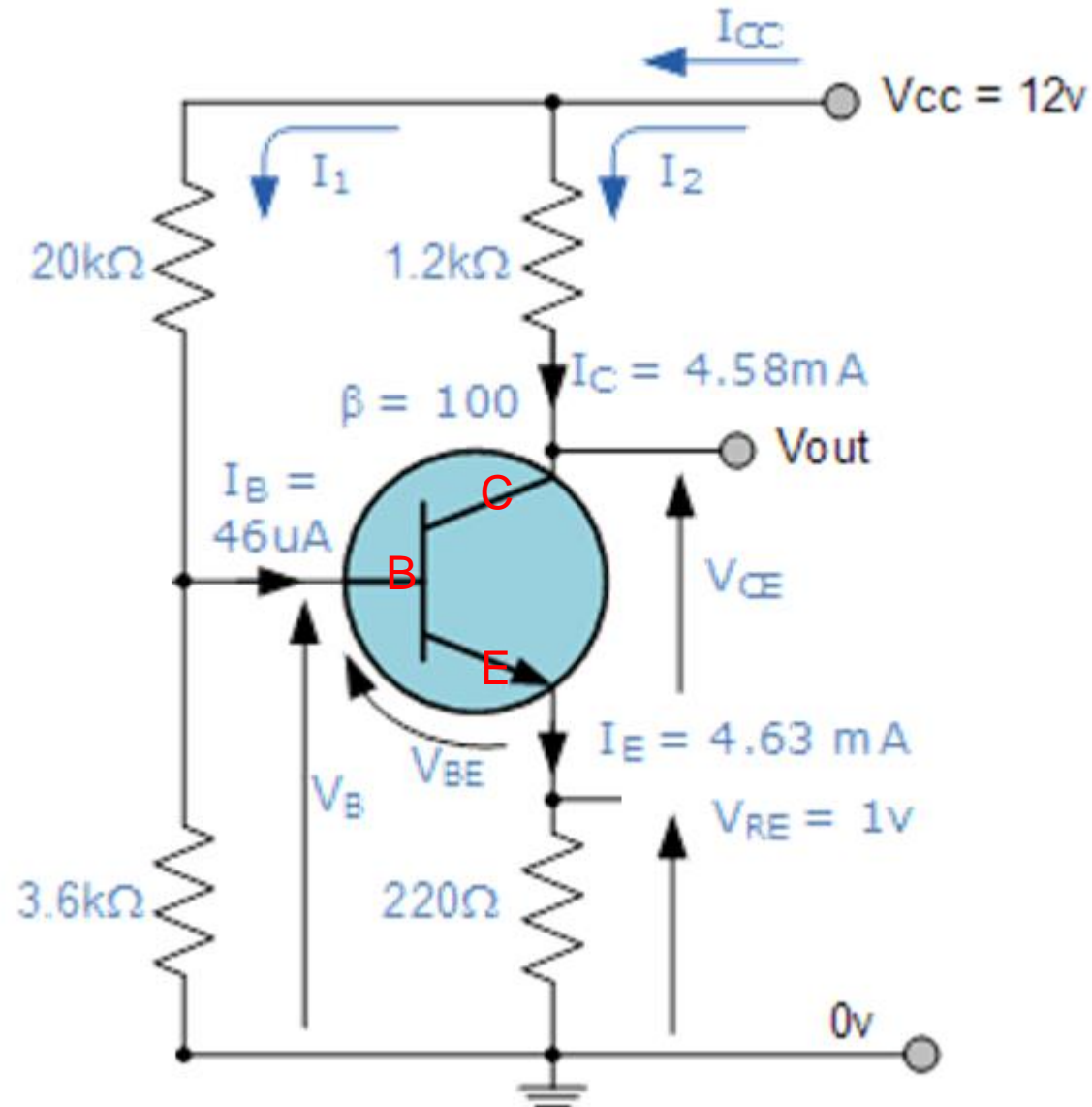

PRACTICAL DESIGN

- Single battery bias


MORE on BJT common emitter amplifiers

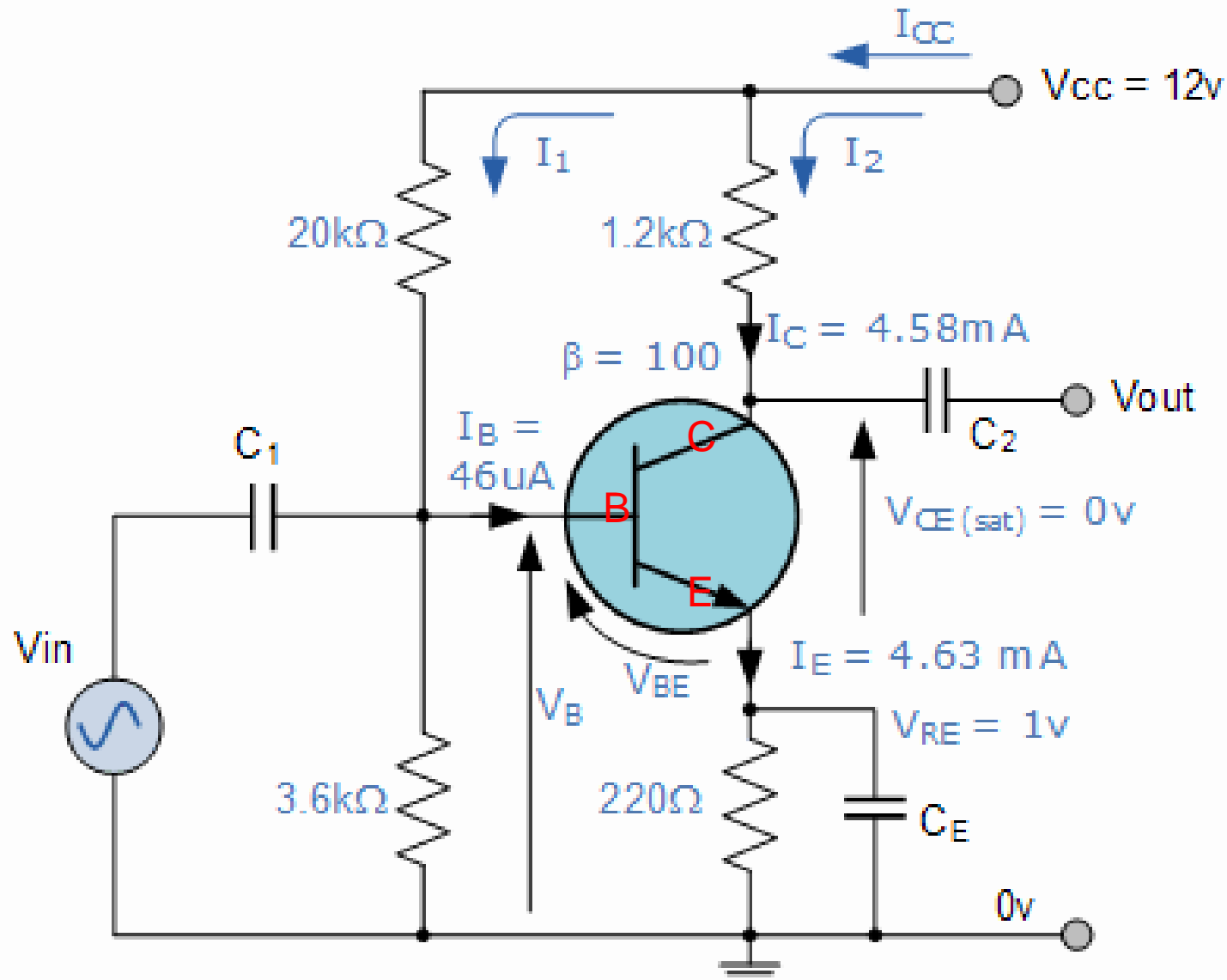

PRACTICAL DESIGN

- Single battery bias
- Coupling capacitors for A.C. signal components

MORE on BJT common emitter amplifiers


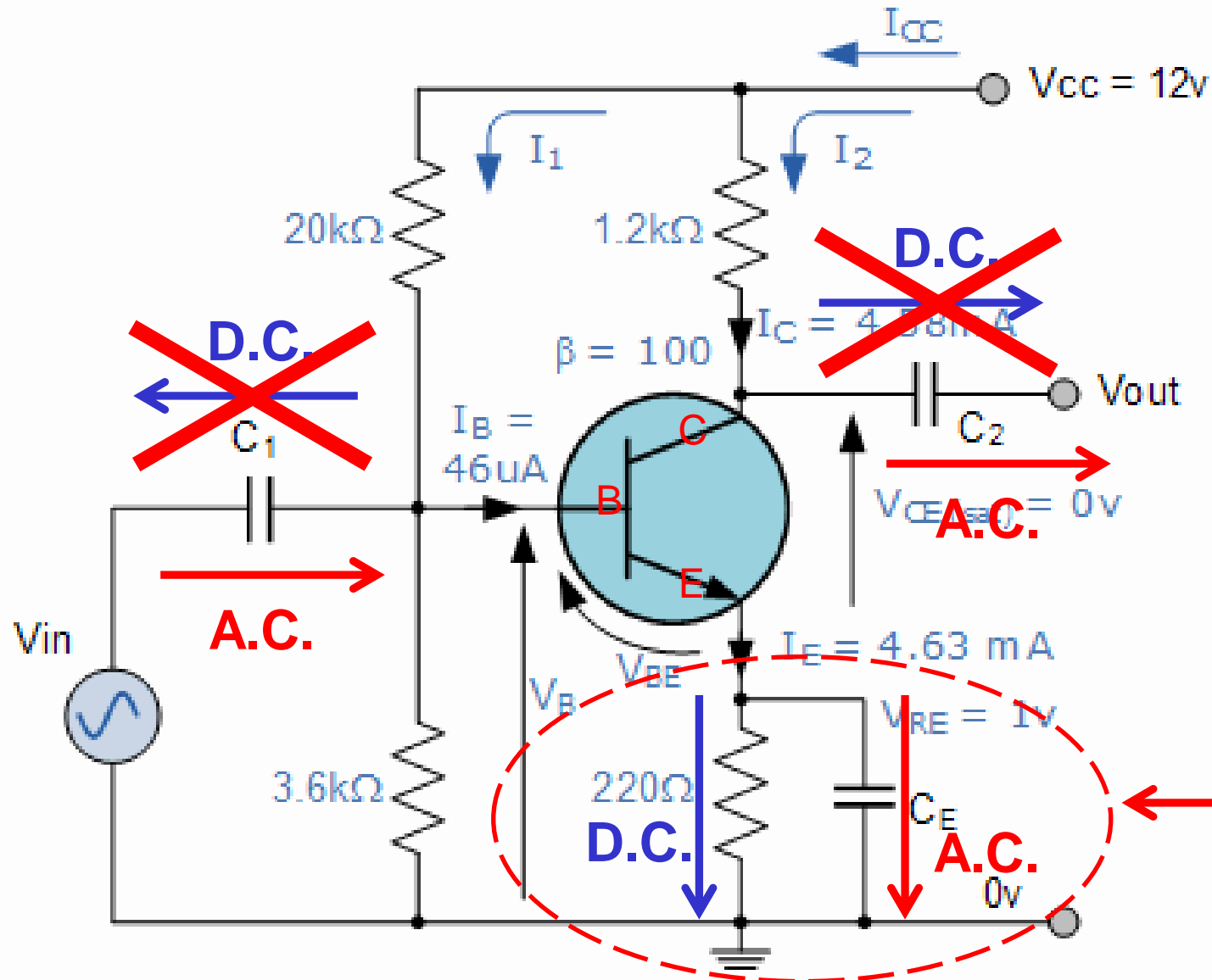


PRACTICAL DESIGN



- Single battery bias
- Coupling capacitors for A.C. signal components

- Resistor conducts for D.C. current
- Capacitor bypasses resistor for A.C. signal so emitter is effectively connected to ground

With DC bias

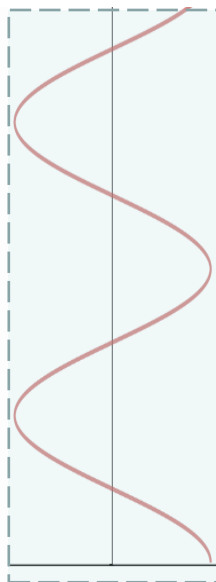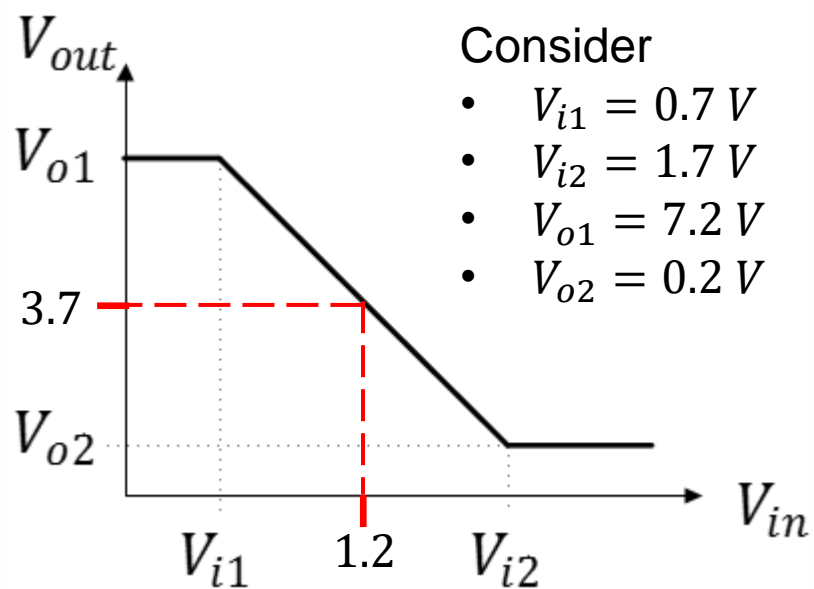


Without DC bias

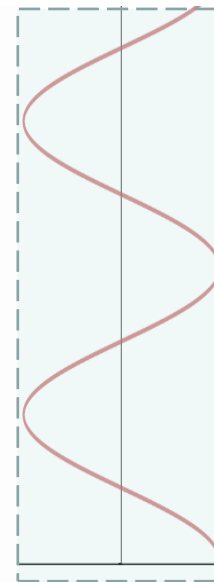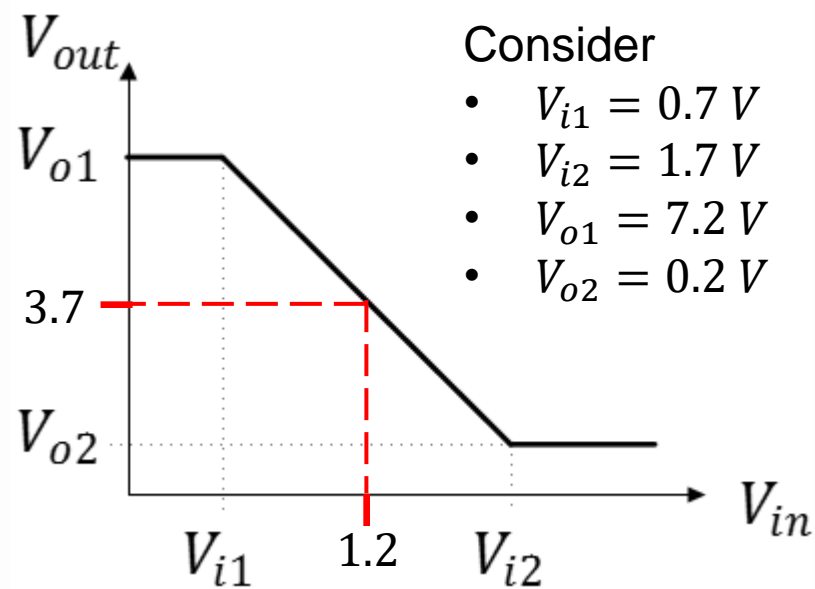


The output may be distorted
Since a large part of locates
outside the active regime.


MORE

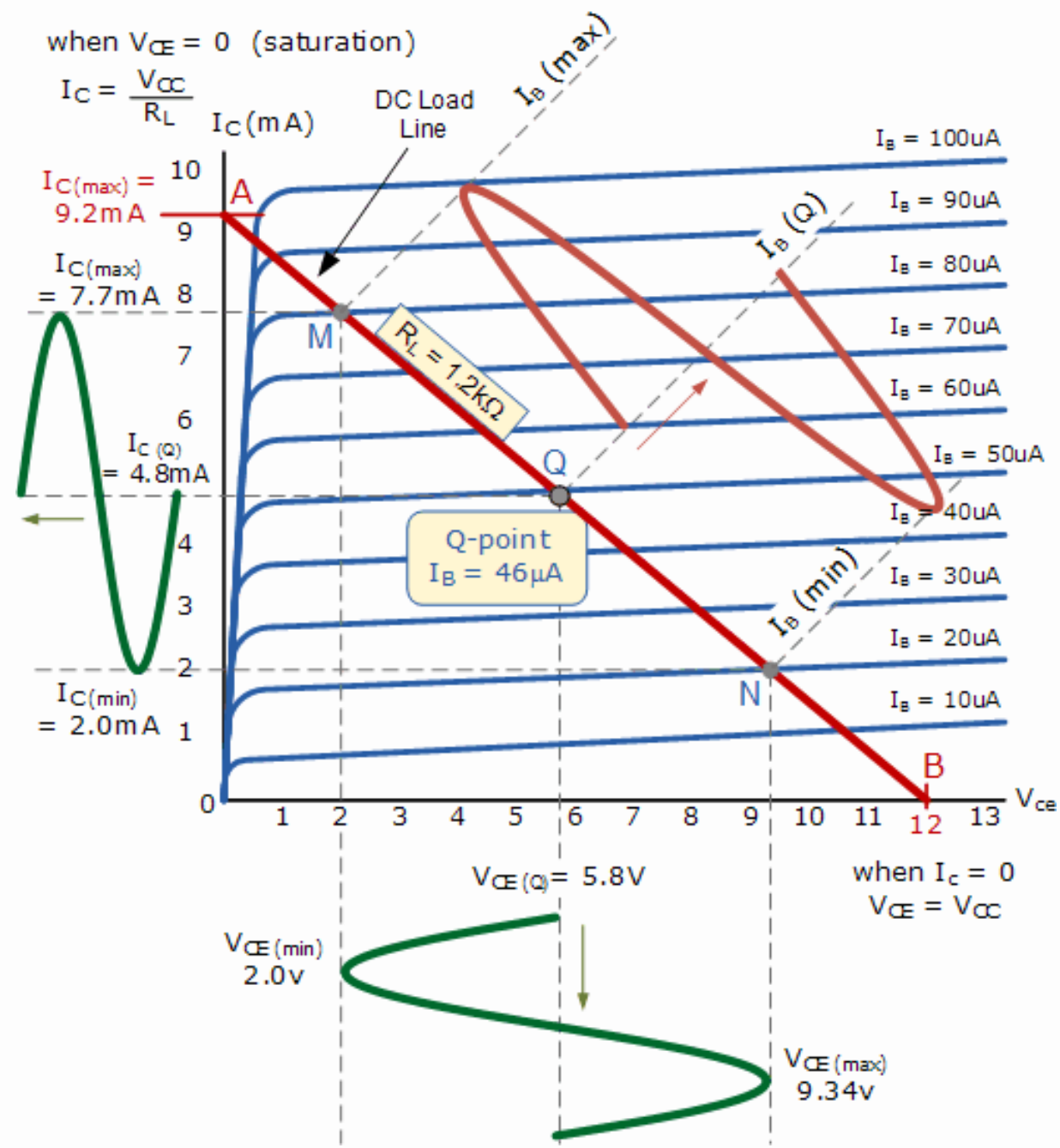

MORE


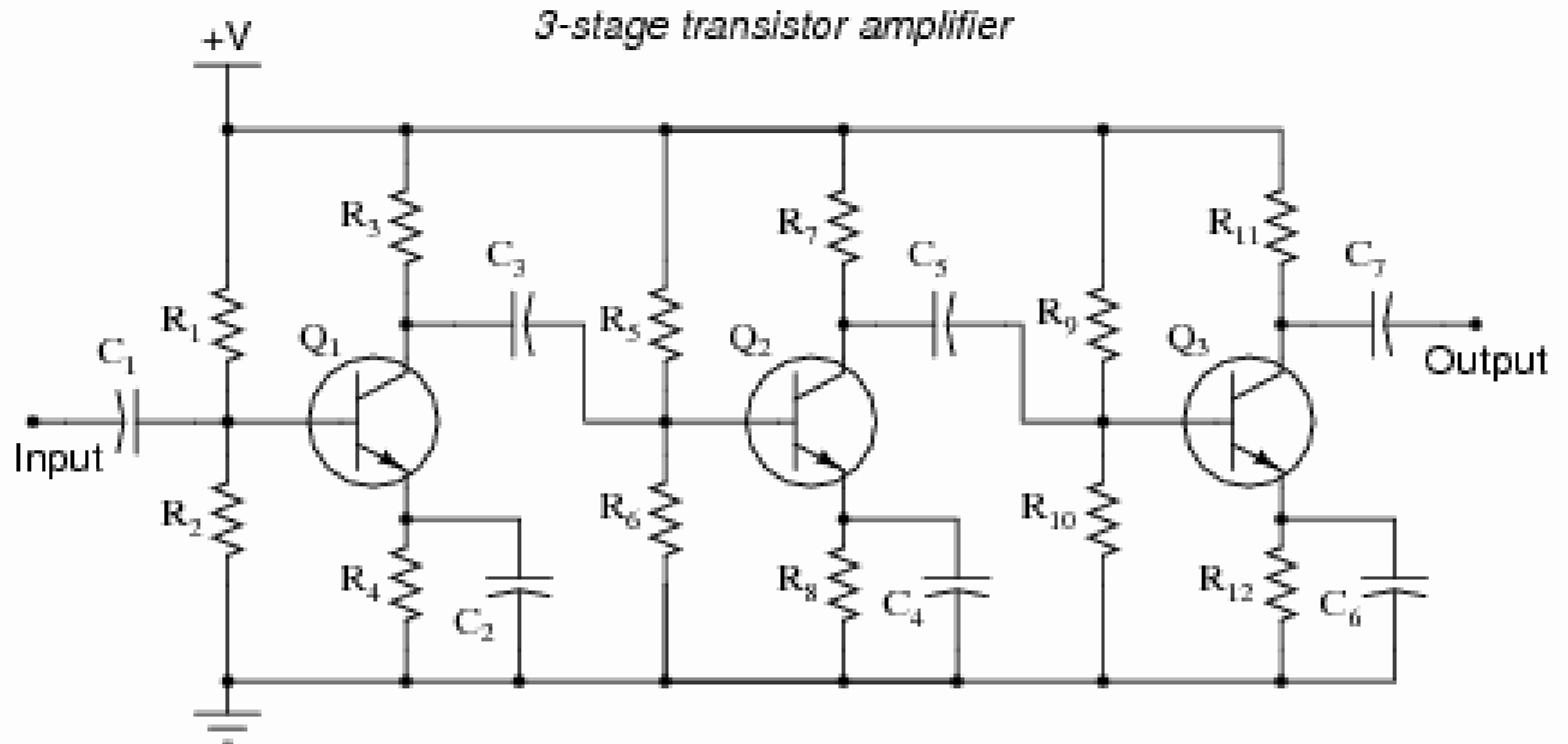


MORE

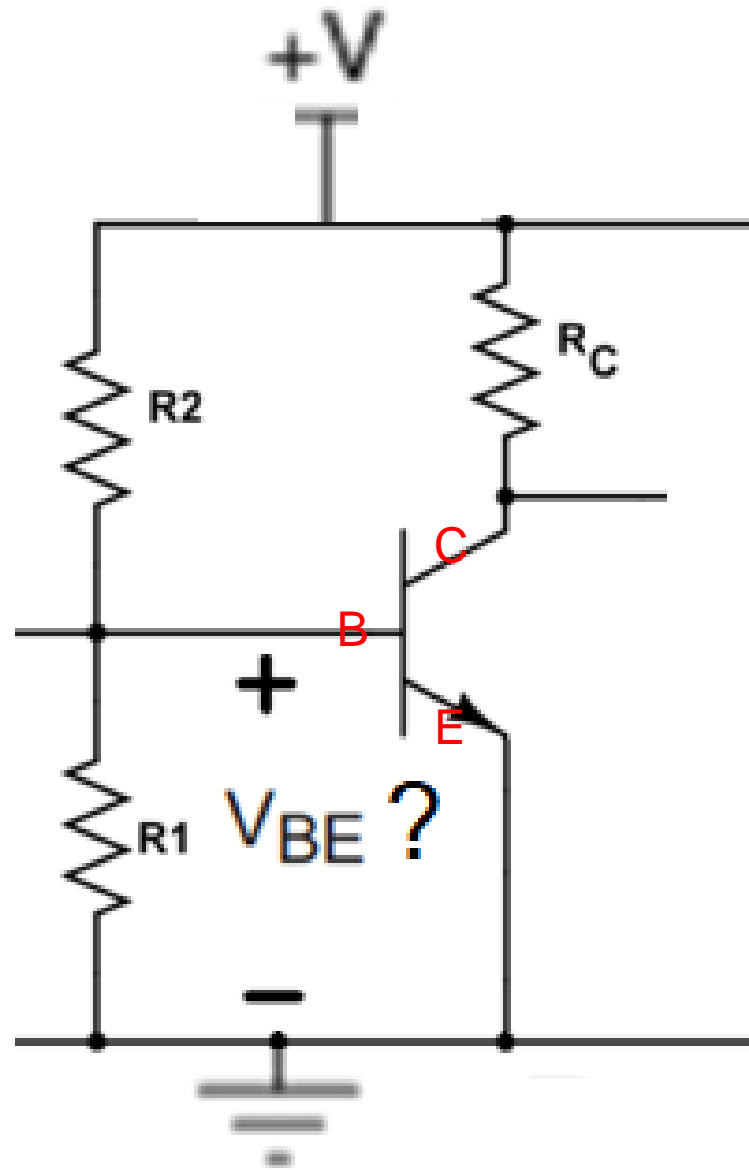

MORE

FIND THEVENIN EQUIVALENT

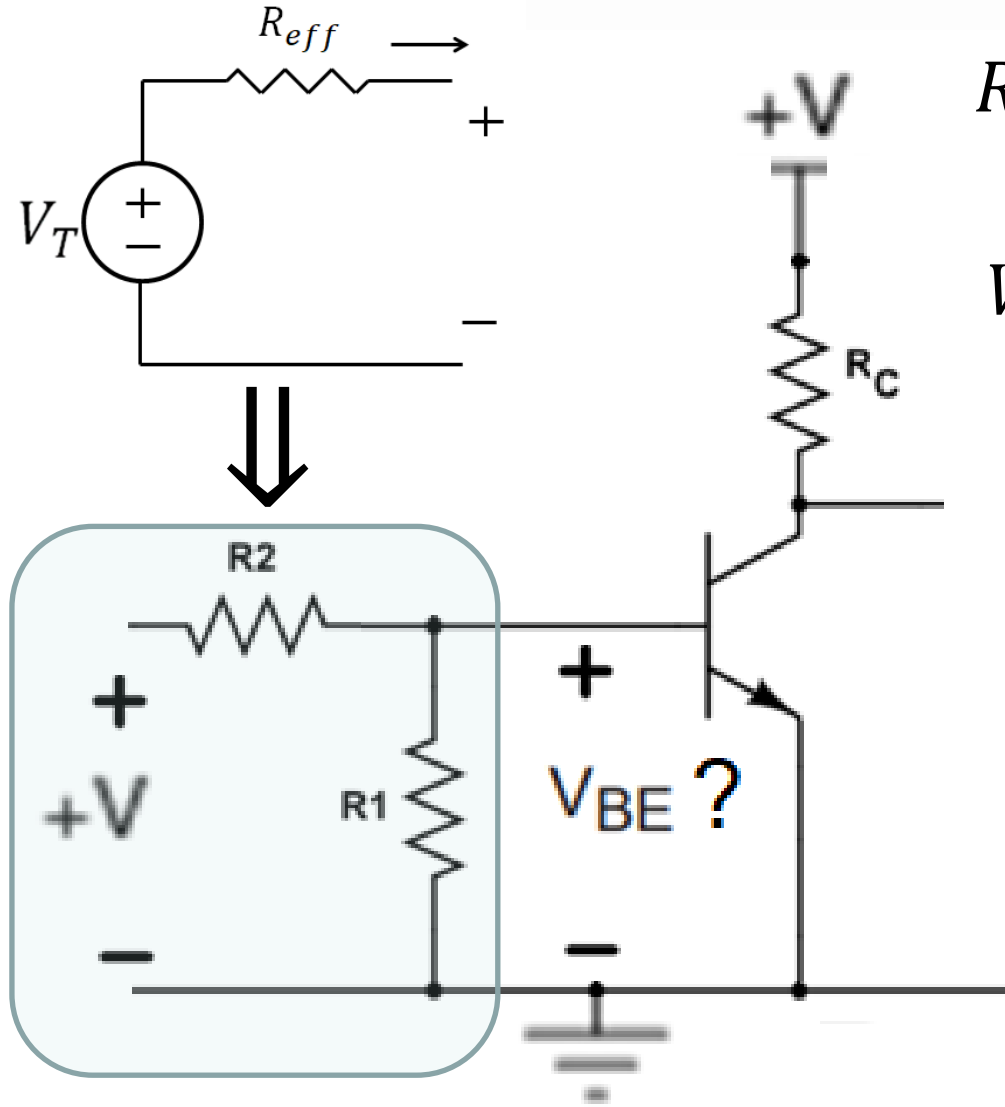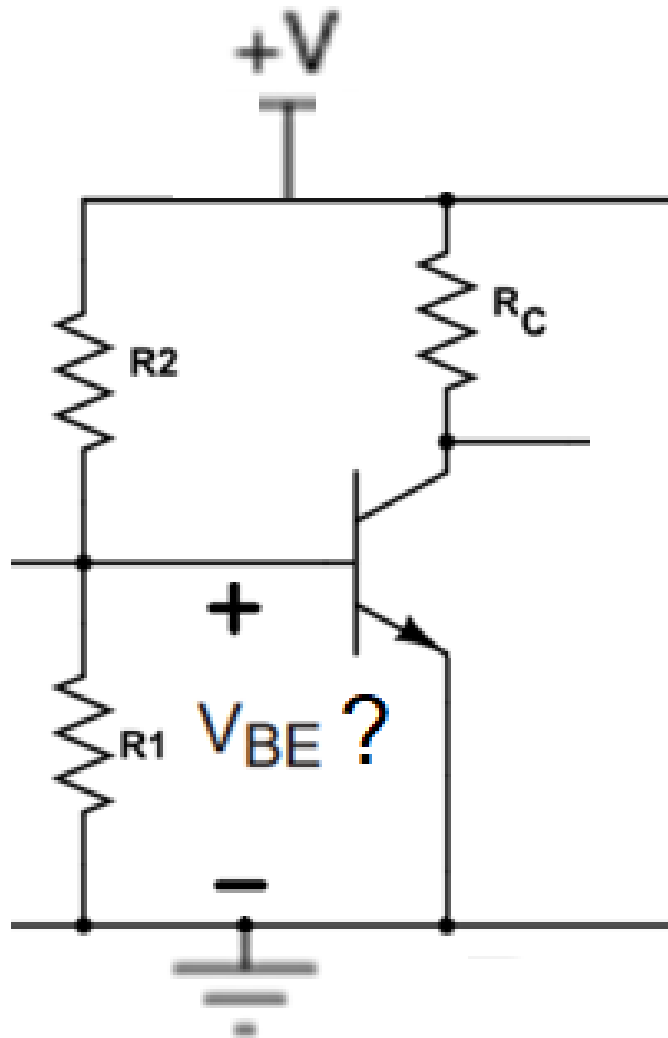

$$R_{eff} = R_1 // R_2$$

$$V_T = V \frac{R_1}{R_2 + R_1}$$

L21 Learning Objectives

- a. Explain the voltage transfer curve (V_{out} vs. V_{in})
- b. Find the transition points on the voltage transfer curve
- c. Find the slope of the active region in the transfer curve
- d. Determine the operating regions for an AC+DC input
- e. Evaluate and AC+DC output for linear amplification

Lecture 22: Exercises

- We will use this lecture to catch up, if needed
- We will also do multiple exercises
- Slides may be distributed in lecture