

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 5 \text{ k}\Omega$$

$$R_3 = 7 \text{ k}\Omega$$

The measured nodal voltages are:

$$V_a = 19 \text{ V}$$

$$V_b = 14.441176470588236 \text{ V}$$

$$V_c = 9.882352941176471 \text{ V}$$

Find voltage  $V_{ab}$  and the current  $I_1$ .

$$V_{ab} = \boxed{\phantom{000000}} \text{ V}$$

$$I_1 = \boxed{\phantom{000000}} \text{ mA}$$

(within three significant digits)

What is the power for the voltage and current source in watts?

$$V_{ab} = V_a - V_b = 4.559 \text{ V}$$

$$I_1 = \frac{V_{ab}}{5 \text{ k}} = \frac{4.559}{5} \text{ mA}$$

$$P_{V_s} = - (19 \cdot I_1)$$

$$I_s = I_1 - V_c / 7 \text{ k}$$


$$\therefore P_{I_s} = - (V_c \cdot I_s)$$

# Lecture 16: Introduction to Diodes

- Diode IV characteristics
- Connecting diode to a linear circuit
- Piecewise linear models of diodes


Recommended: <https://learn.sparkfun.com/tutorials/diodes>

# Diode as a two-terminal device

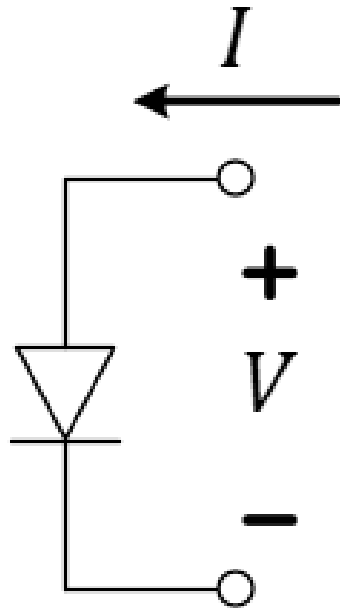

Made out of *semiconductor* materials like Si, Ge, GaAs, AlGaAs, GaN with some additives called *dopants*.

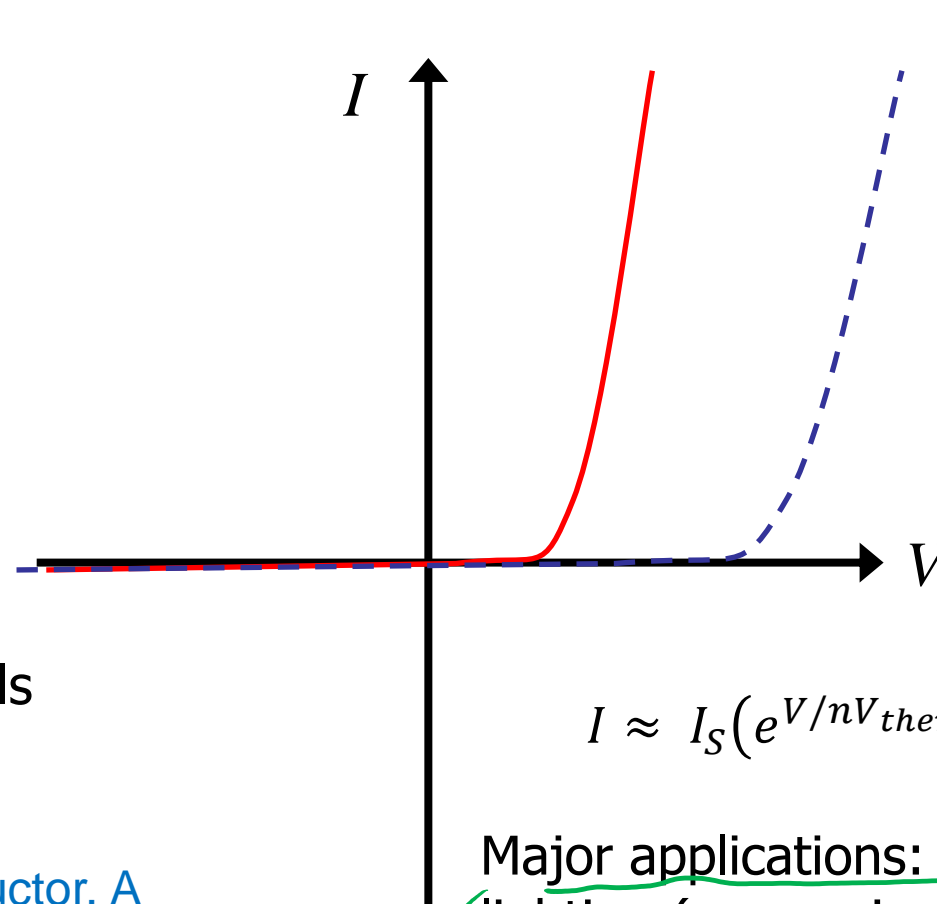Refer to L15 introduction to a semiconductor. A diode is formed by bringing two semiconductor regions together. One has excess mobile electrons (n-type) and the other excess mobile holes (p-type) due to different *dopants* (e.g. As, B in Si)



Q: Based on the exponential equation for IV as shown, can the diode supply power?



- A. Yes
- B. No

Major applications:

lighting (conversion of  $I$  to photons), electronics


But when exposed to light  $I$  can reverse ( $-I$ ) with  $+V$  to supply power: Which is how a solar power cell works! Will discuss in later lectures.

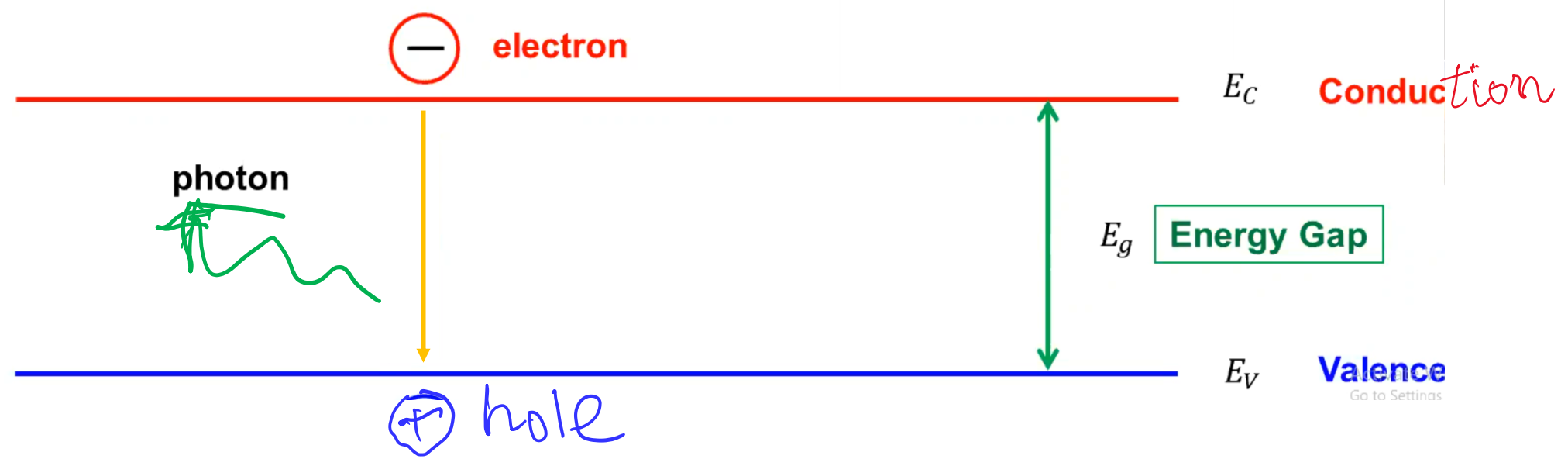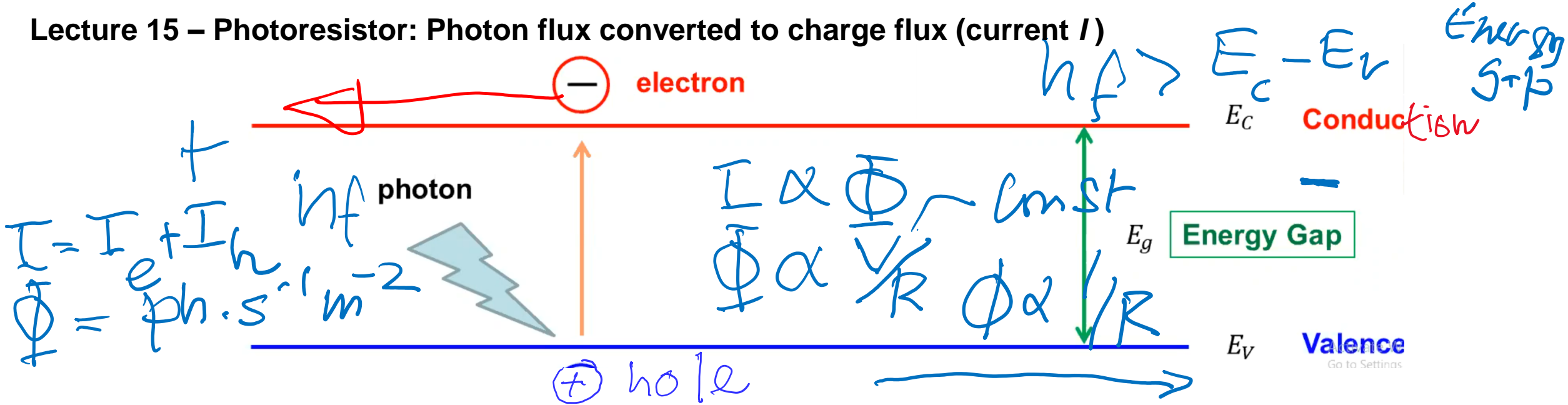Lecture 15 – Photoresistor: Photon flux converted to charge flux (current I)




Reverse process to convert current I to a photon flux also possible - LED

# Connecting diode to a linear circuit

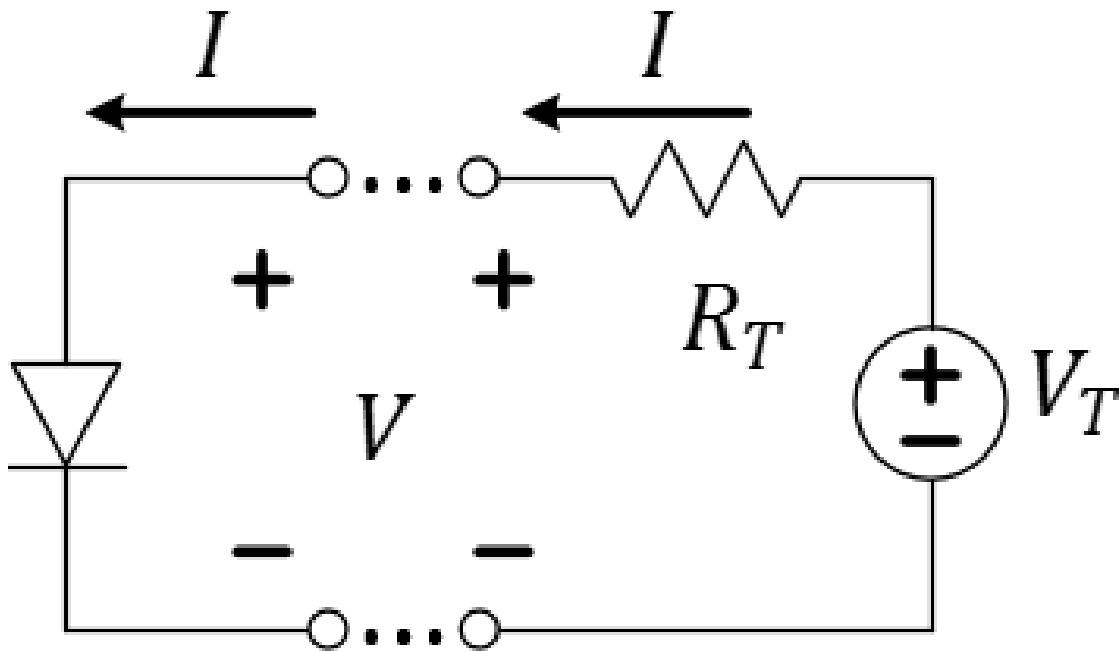

Q: What is the current flowing through the diode if  $V_T < 0$ ?


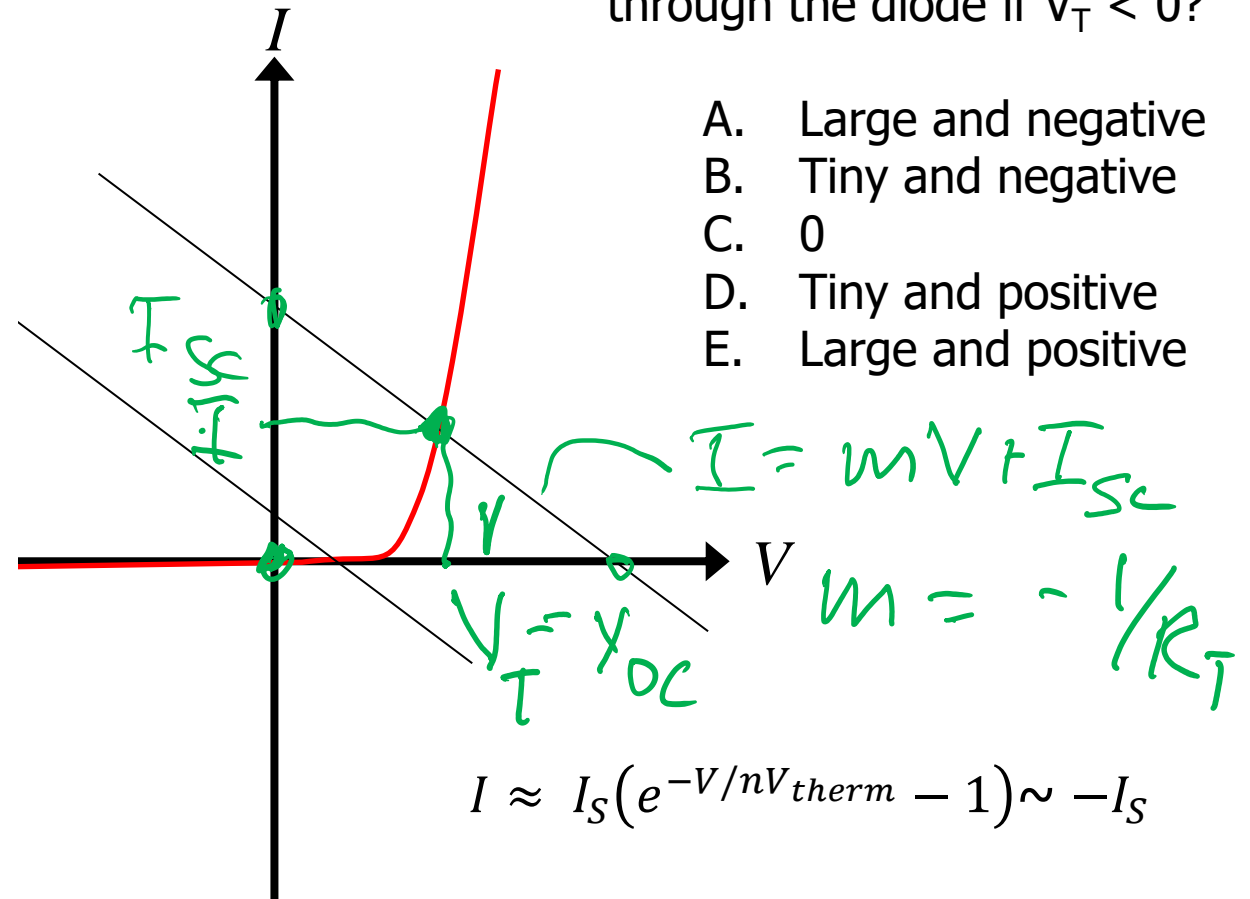
- A. Large and negative
- B. Tiny and negative
- C. 0
- D. Tiny and positive
- E. Large and positive



We can solve graphically for an operating point.  
For an LED more current means more light.
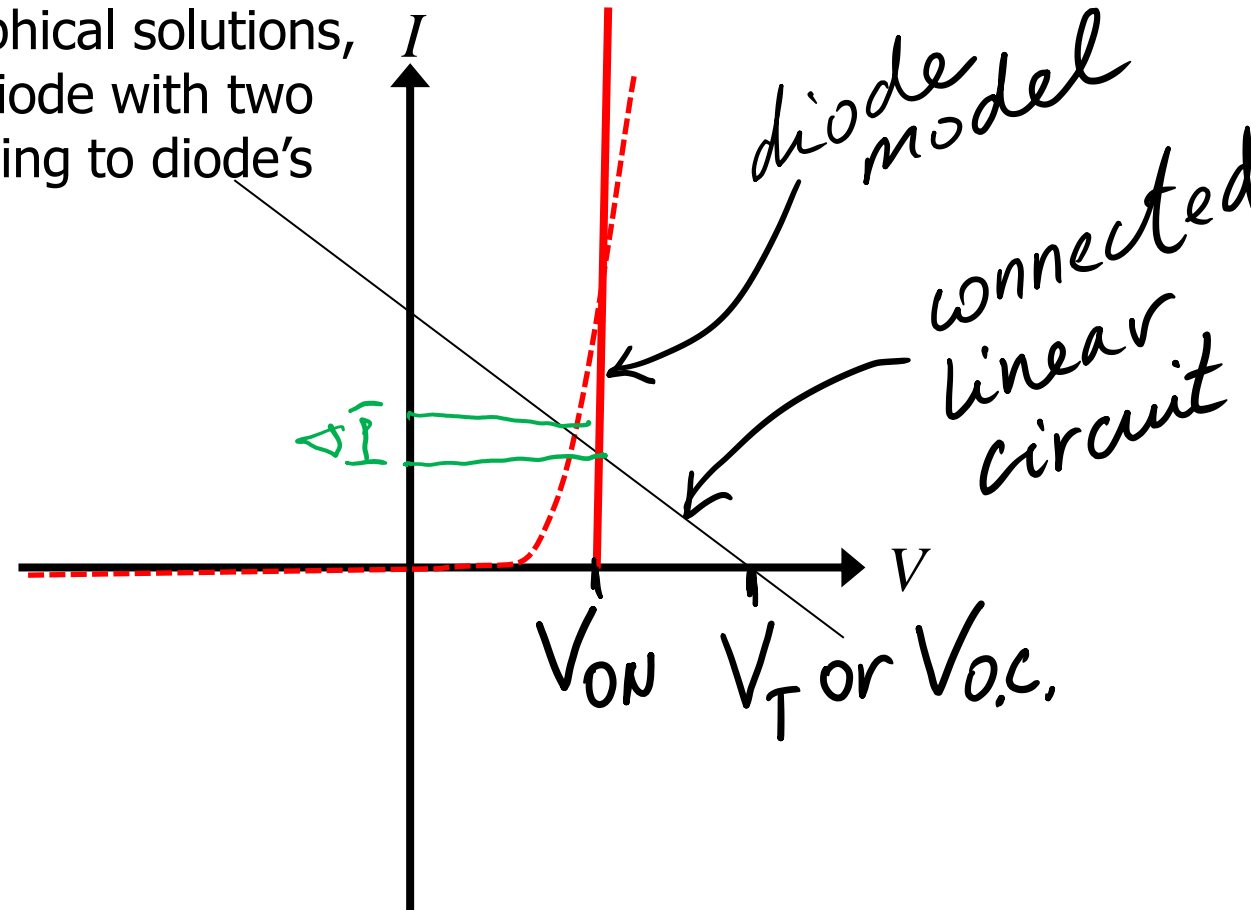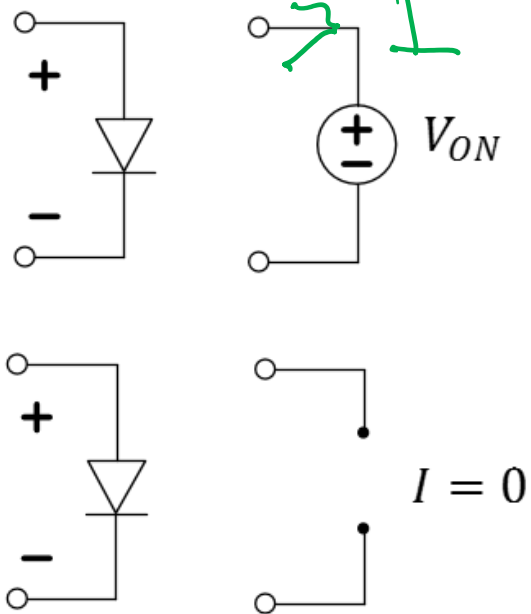
# Modeling diode with linear IV segments

Instead of looking for graphical solutions, we can approximate the diode with two line segments, corresponding to diode's regimes of operation.



Q: What is the minimum  $V_T$  of the connected linear circuit which causes current to flow through the diode assuming the IV model?

- A.  $0\text{ V}$
- B.  $V_T$
- C.  $V_{oc}$
- D.  $V_{ON}$
- E. None of these.


## Different diode types have different $V_{ON}$

Diode Type	$V_{ON}(V)$	Applications
Silicon	0.6-0.7	General; integrated circuits; switching, circuit protection, logic, rectification, etc.
Germanium	~0.3	Low-power, RF signal detectors
Schottky	0.15-0.4	Power-sensitive, high-speed switching, RF
Red LED (GaAs)	~2	Indicators, signs, color-changing lighting
Blue LED (GaN)	~3	Lighting, flashlights, indicators
“Ideal”	0	Can neglect $V_{ON}$ for high voltage applications

Q: What is the power dissipated by a Ge diode if 30 mA is flowing through it?

- A. 3 mW
- B. 9 mW
- C. 30 mW
- D. 90 mW
- E. 900 mW
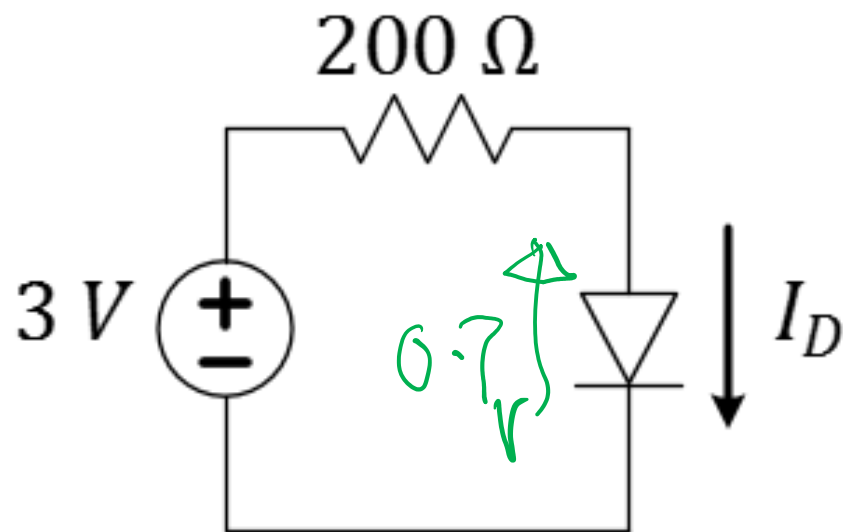
## Diode circuit examples (offset ideal model)



Assume offset-ideal model with  $V_{ON} = 0.7$  (common Si diodes)


Q: What is the current through the diode?

- A. 15 mA
- B. 11.5 mA
- C. 5 mA
- D. 1.15 mA
- E. 0 mA

$$\frac{3 - 0.7}{200} = \frac{2.3}{200} = 11.5 \text{ mA}$$



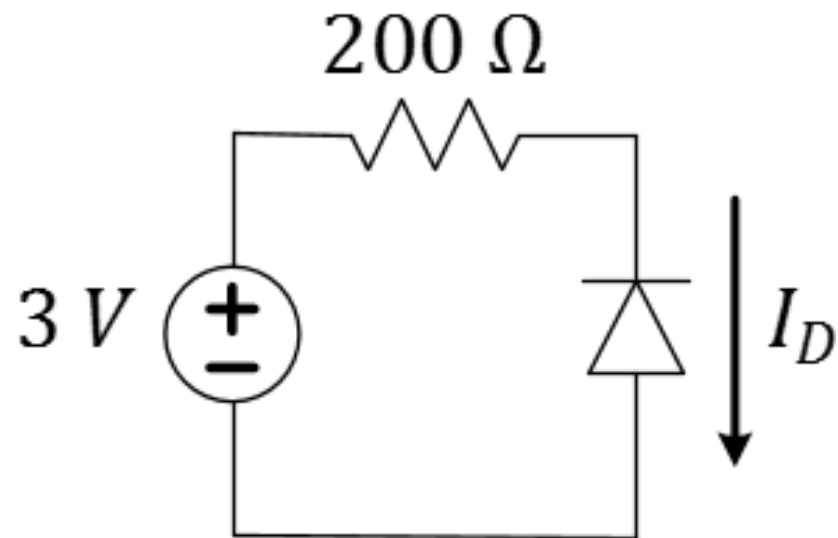
## Diode circuit examples (offset ideal model)



Assume offset-ideal model with  $V_{ON} = 0.7$   
(common Si diodes)

Q: What is the current through the diode?

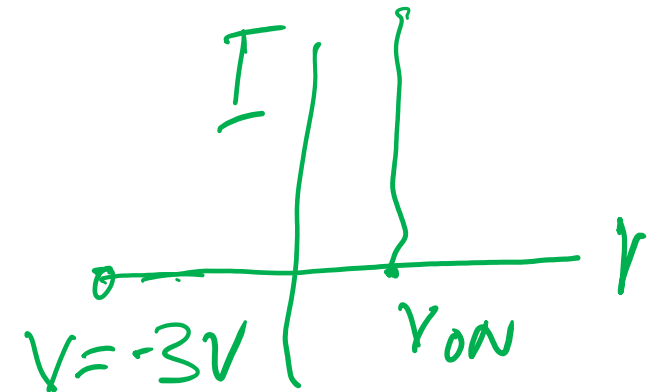- A. 15 mA
- B. 11.5 mA
- C. 5 mA
- D. 1.15 mA
- E. 0 mA






# Diode circuit examples (offset ideal model)

Assume offset-ideal model with  $V_{ON} = 0.7$  (common Si diodes)

Q: What is the current through the diode in the circuit?

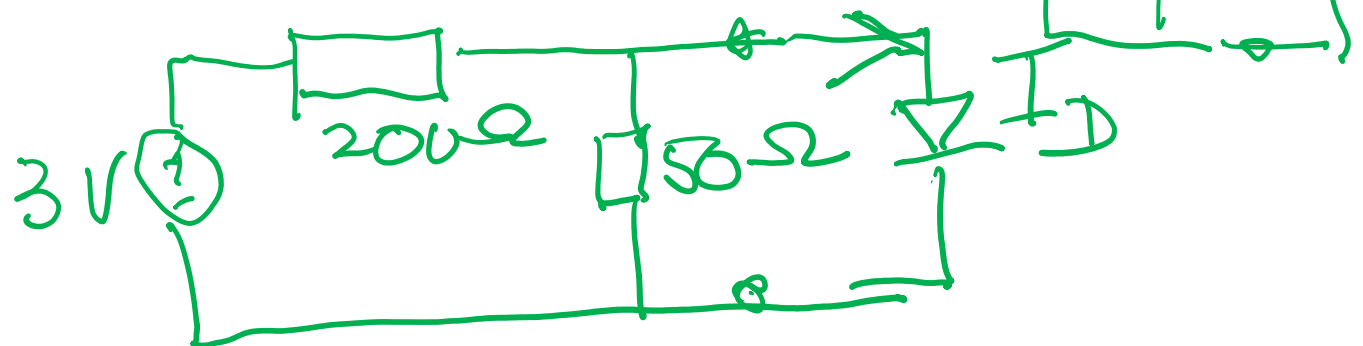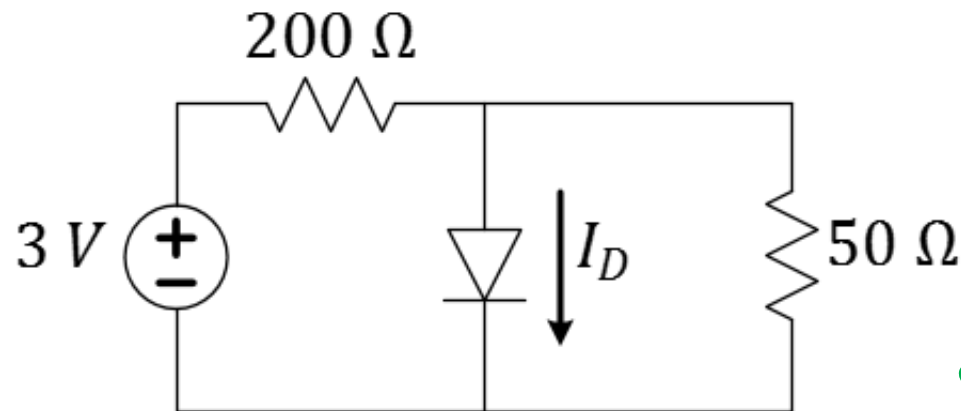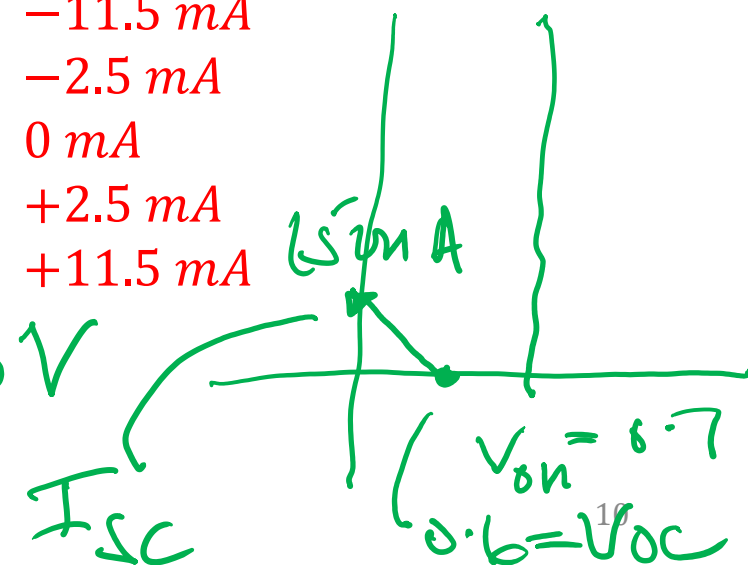
- $I_D =$
- A.  $-11.5 \text{ mA}$
  - B.  $-2.5 \text{ mA}$
  - C.  $0 \text{ mA}$
  - D.  $+2.5 \text{ mA}$
  - E.  $+11.5 \text{ mA}$



$$R_T = \frac{10000}{250} = 40 \Omega$$

$$V_{OC} = V_T = \frac{50 \cdot 3}{250} = 0.6 \text{ V}$$
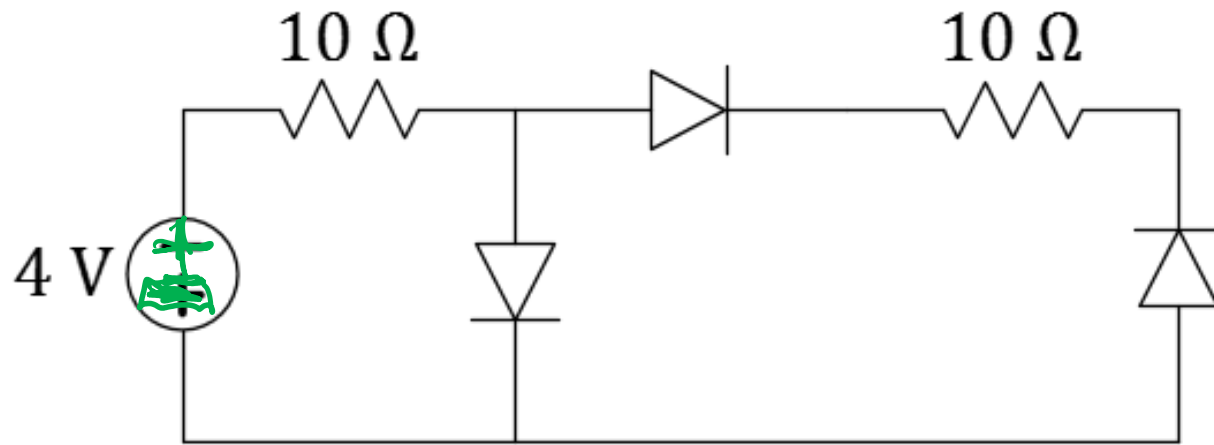
## Back-to-back diodes in series are modeled by OIM as an open circuit



Q: Assume OIM with  $V_{ON} = 0.7 \text{ V (Si)}$   
What is the current through the left-most diode?

- A. 0 Amps
- B. 0.2 Amps
- C. 0.33 Amps
- D. 0.4 Amps
- E. 3.3 Amps

# L16 Learning Objectives

- a. Draw a “typical” diode IV curve and describe its shape
- b. Explain how to use graphical analysis to find the operating point of a non-linear diode connected to a linear circuit
- c. Describe the offset ideal diode model (open, V-source)
- d. Solve simple circuit problems with one diode, given  $V_{ON}$