
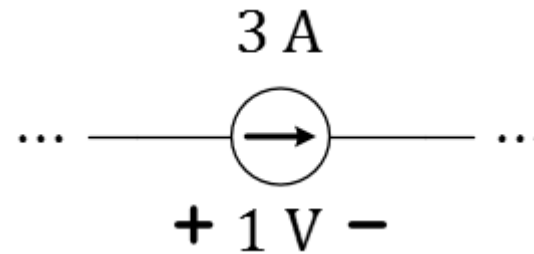


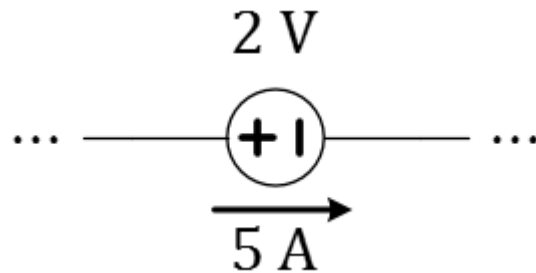

Lecture 10: Signed Power and Design


- The purpose of a signed power convention
- Exercises under constraints on components

Which of the sources are delivering power?



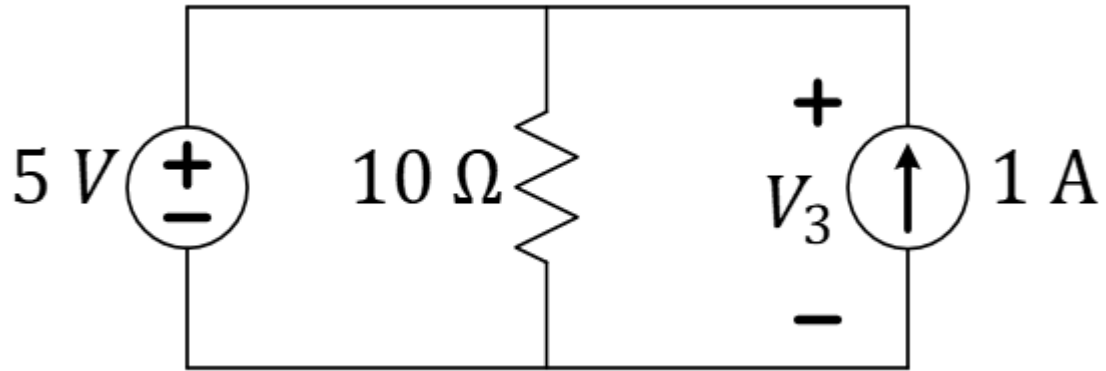
- A. The voltage source only
- B. The current source only
- C. Both
- D. Neither
- E. Not enough information to tell

Polarity labels for Kirchhoff are Arbitrary



Q: Find the value of V_3 .

Q: Find the power of the current source.

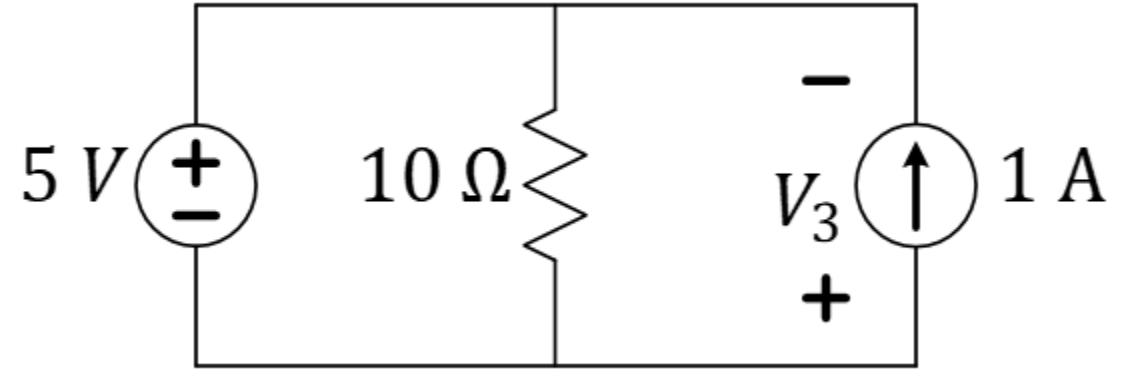


Q: Find the value of V_3 .

Q: Find the power of the current source.

Q: Does the sign of $P_3 = V_3 I_3$ have any meaning?


Standard Reference

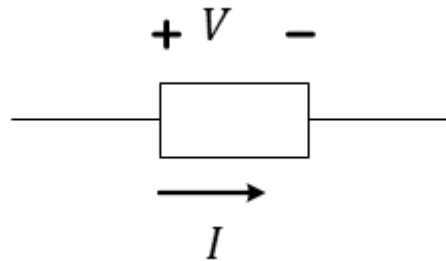

$$V = IR$$

$$P = IV$$

Non-Standard Reference

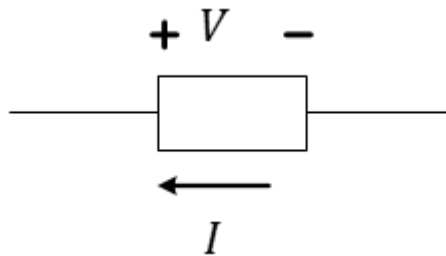


$$V = -IR$$

$$P = -IV$$


Note: Standard convention is also called “passive” convention.

Polarity for *Power* MATTERS!

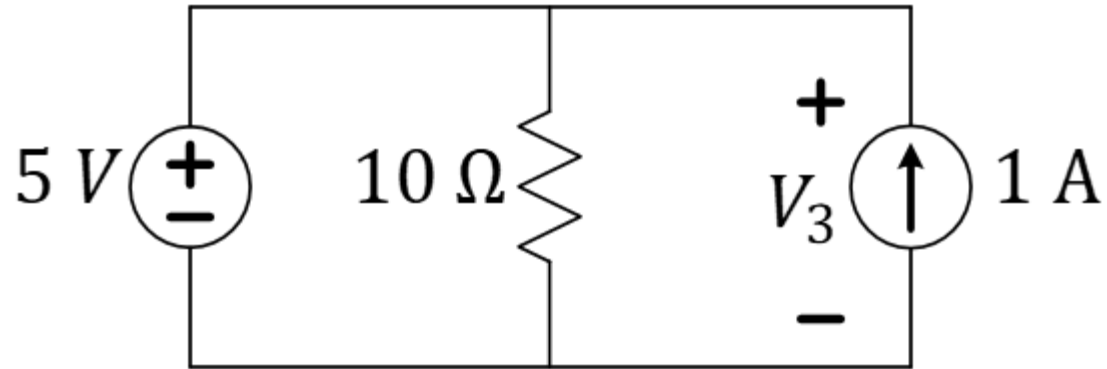


Non-Standard Reference

$$P = -IV = -(1)(V_3)$$

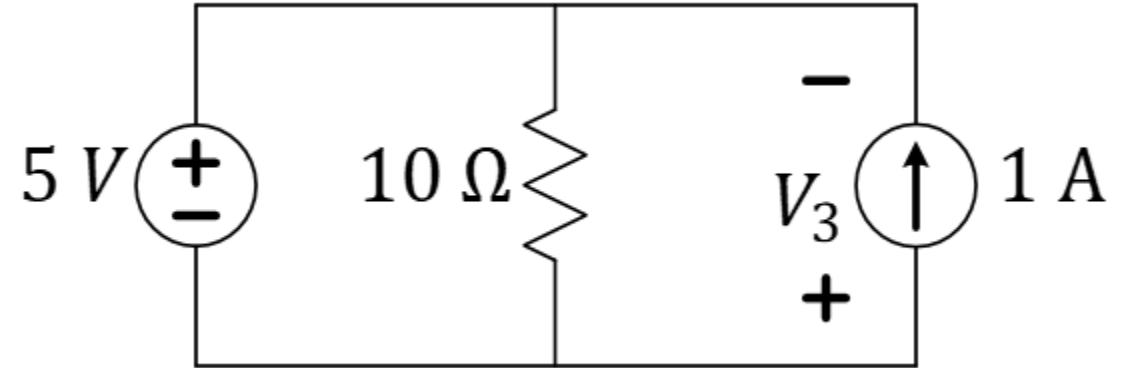


Standard Reference

$$P = IV = +(1)(V_3)$$



$$P = -5 \text{ W}$$

Polarity for *Ohm's Law* MATTERS!

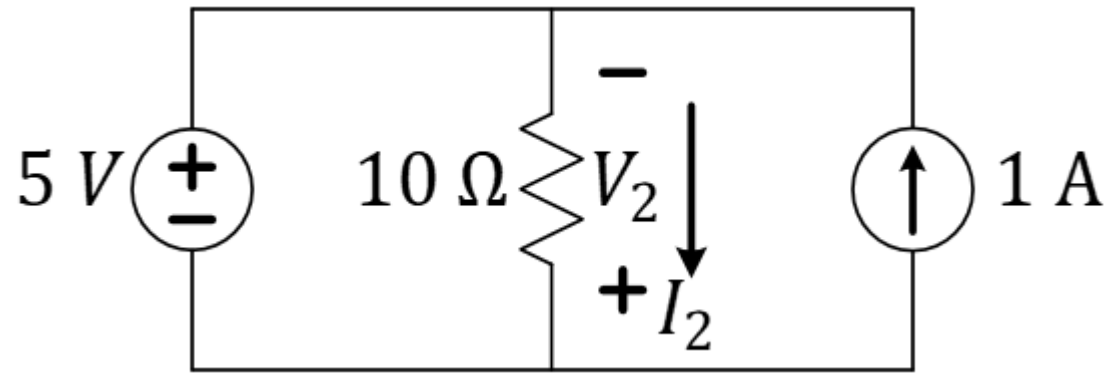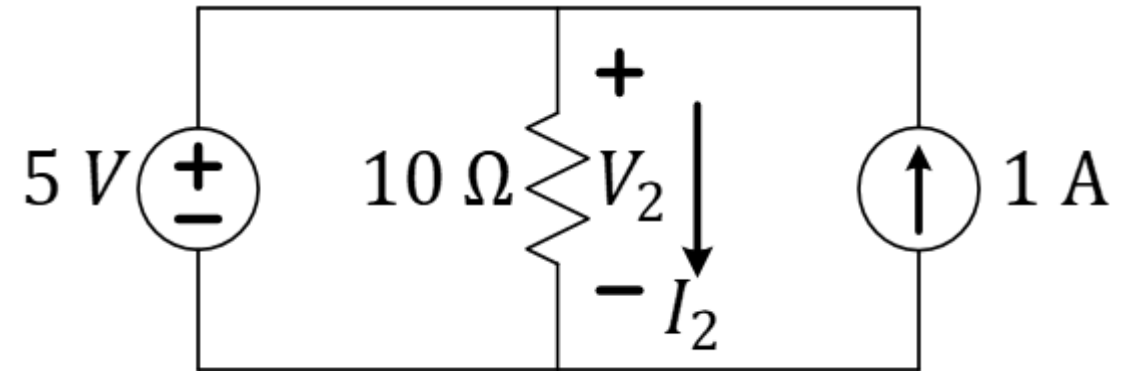


Non-Standard Reference

$$I_2 = -\frac{V_2}{R}$$




Standard Reference

$$I_2 = \frac{V_2}{R}$$


$$I_2 = 0.5 \text{ A}$$

The Equation $P=IV$ Assumes Standard

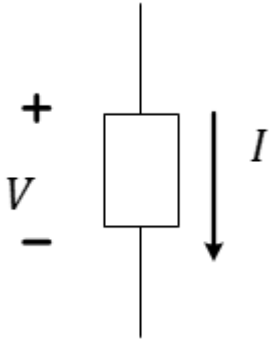
Using the standard polarity labeling: $P = V I_{+ \rightarrow -}$



$P < 0 \Rightarrow$ Element *delivers* power to the circuit

$P > 0 \Rightarrow$ Element *absorbs* power from the circuit


Recap of labeling implication

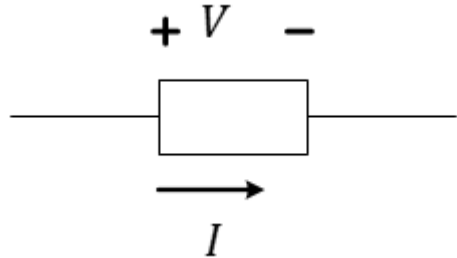

$$R = \frac{V}{I}$$

$$P = VI$$

“Standard Reference”

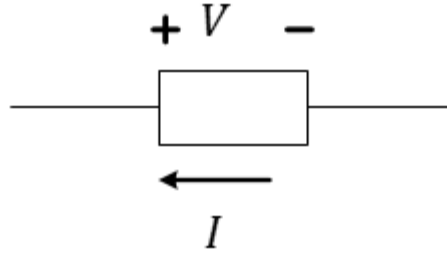

$$R = -\frac{V}{I}$$

$$P = -VI$$

“Non-Standard Reference”


This way, power is defined such that it is negative when it is supplied (sourced) and positive when it is absorbed (sunked).

Q: With power defined as above, what is the sum of powers for all circuit elements?


Universal:

Ohm's Law: $I_{+ \rightarrow -} = \frac{V}{R}$
Power Eqn: $P = VI_{+ \rightarrow -}$

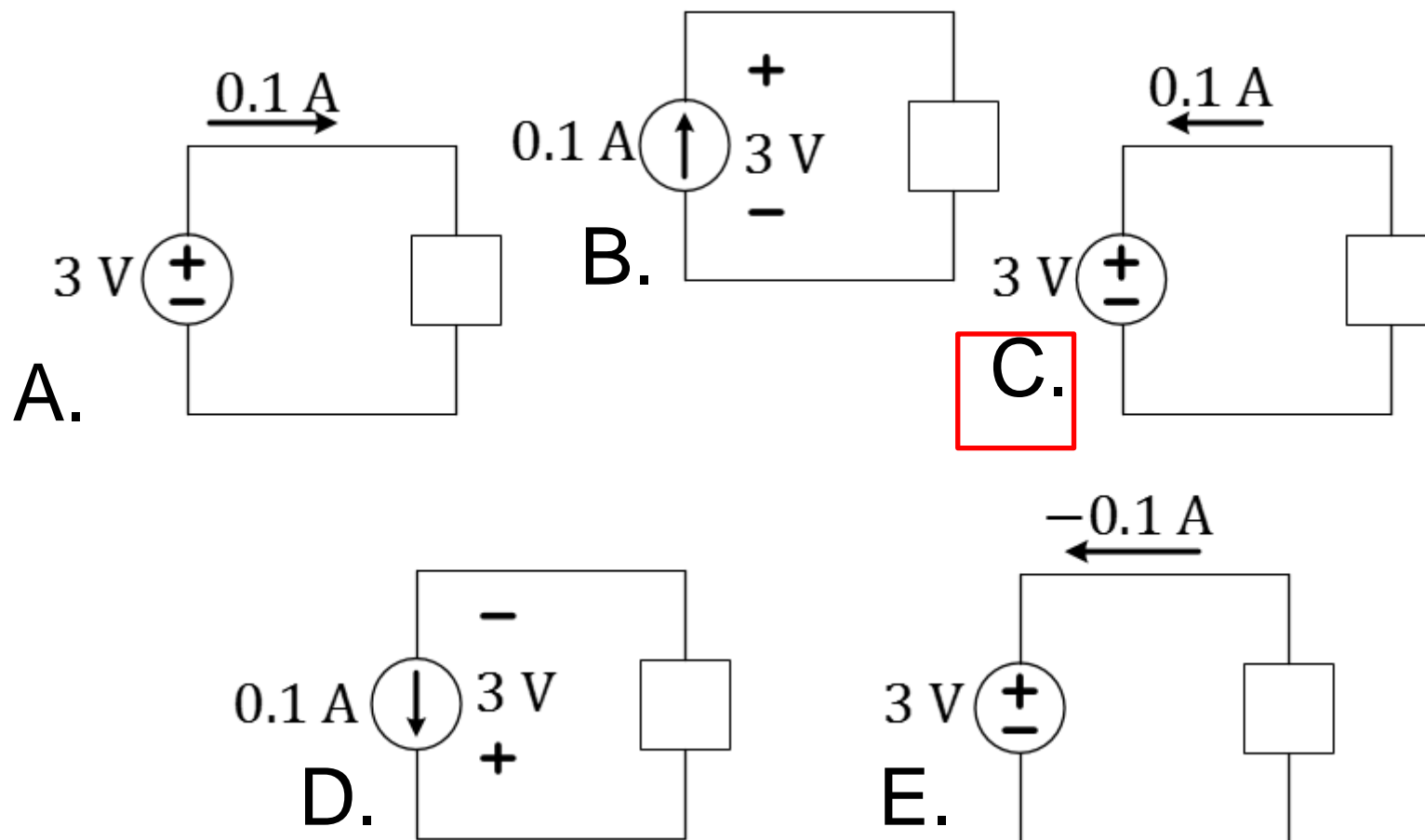Which of the sources below absorbs power?



Using the Power Equation

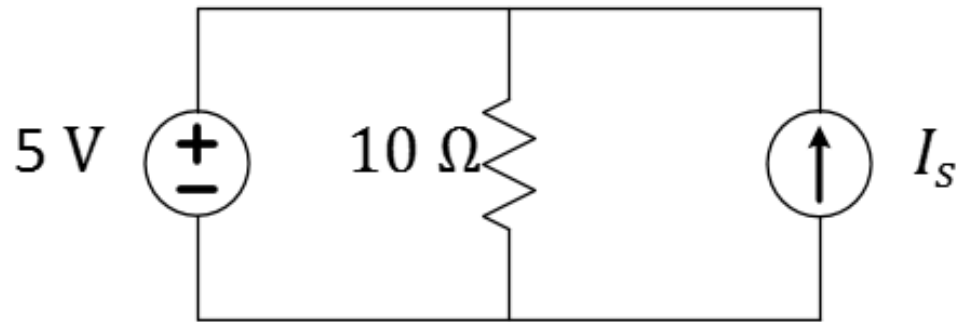

Q: For what values of I_s does the current source supply power?



L10 Learning Objectives

- a. Assign polarity of current and voltage
- b. Properly apply Ohm's Law to conditions of standard and non-standard polarities
- c. Properly apply the signed-Power formula to conditions of standard and non-standard polarities
- d. Design a circuit for specified power constraints.