

$$R_1 R_4 = R_2 R_3$$


R_5 可看作开路



Lecture 8: Application of Circuit Laws

- Example Problems and Practice

VDR for Two Resistances

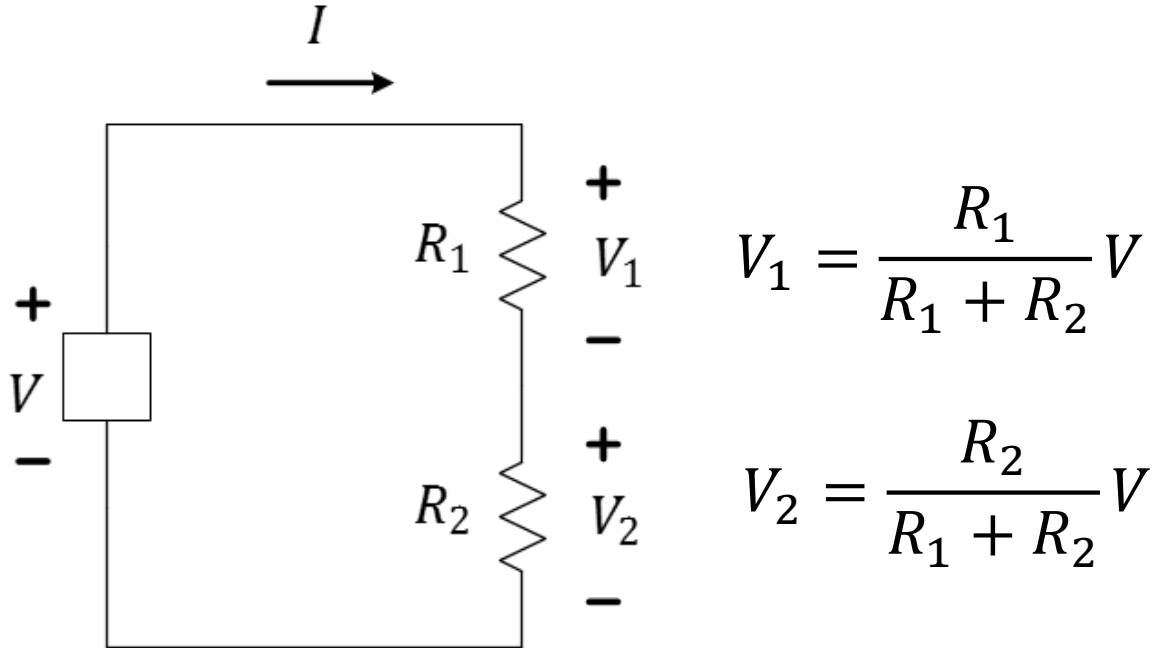


Bad Idea: try to **memorize** these formulae.

Good Idea: try to note trends and **understand concepts** !

Example, if $R_1 = 1 \Omega$ and $R_2 = 2\Omega$, then $V_2:V_1$ will be in a 2:1 ratio for the series circuit.

Why?

VDR and CDR for Two Resistances

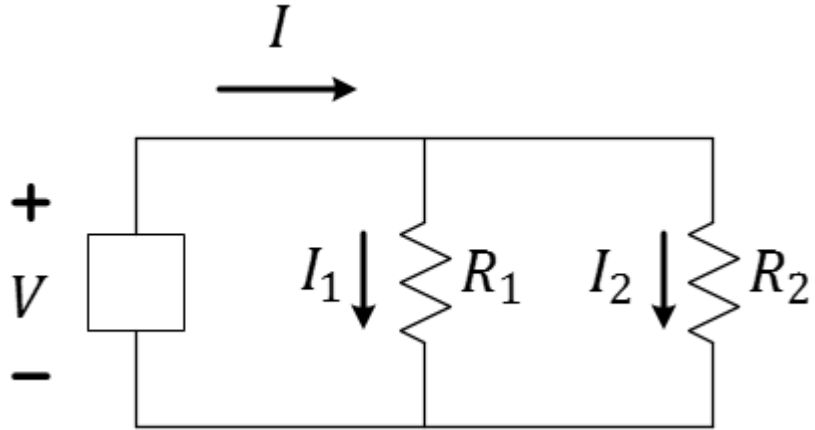

$$I_1 = \frac{R_2}{R_1 + R_2} I \quad I_2 = \frac{R_1}{R_1 + R_2} I$$


Bad Idea: try to **memorize** these formulae.

Good Idea: try to note trends and **understand concepts** !


Example, If $R_1 = 1 \Omega$ and $R_2 = 2\Omega$, then $I_2:I_1$ will be in a 1:2 ratio for the parallel circuit.

Why?

VDR and CDR for Two Resistances

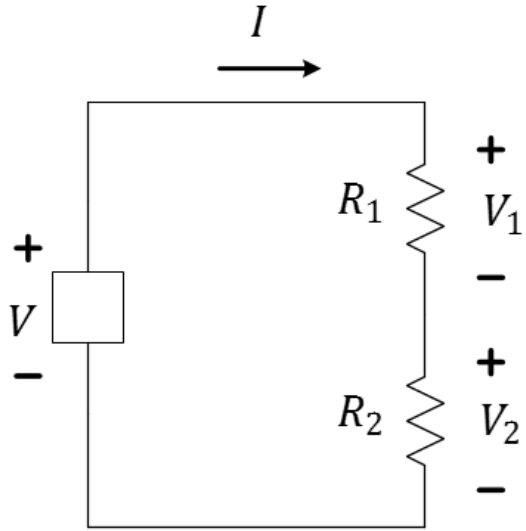


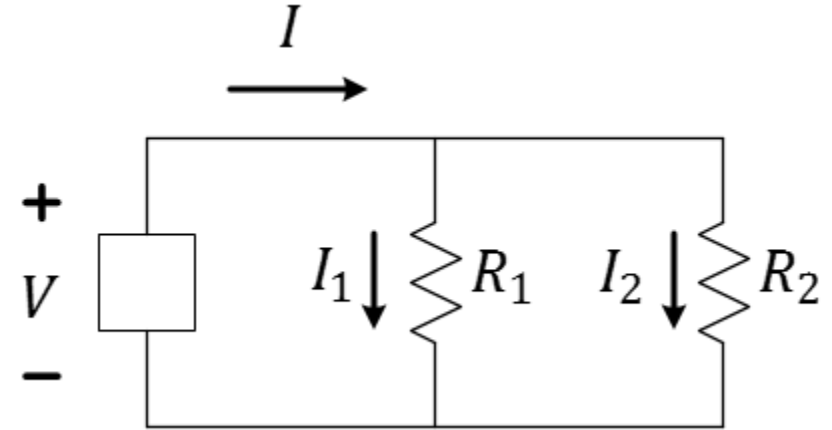Q: If 6 V falls across a series combination of $1\text{ k}\Omega$ and $2\text{ k}\Omega$, what is V across $2\text{ k}\Omega$?




Q: If 0.15 A flows through a parallel combo of $1\text{ k}\Omega$ and $2\text{ k}\Omega$, what is I through $2\text{ k}\Omega$?

VDR and CDR for Two Resistances

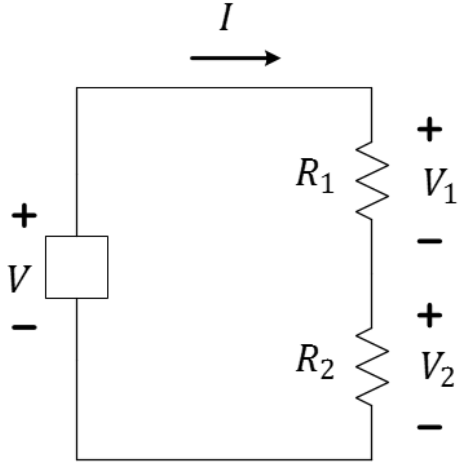


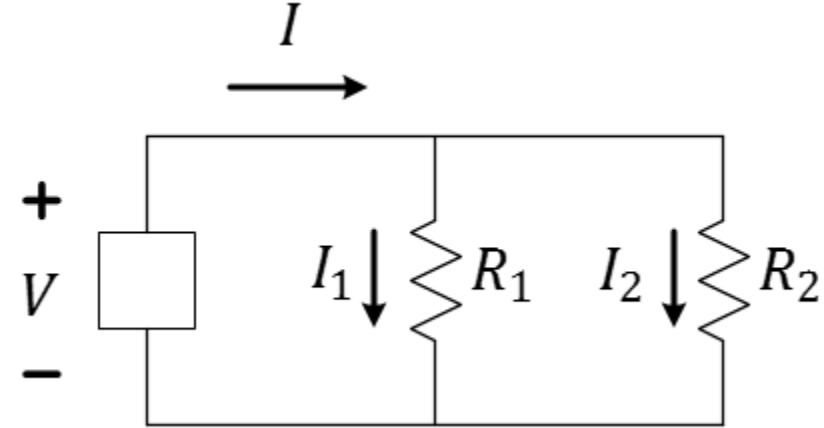Q: If a source supplies 60 W to a series combination of $10\ \Omega$ and $30\ \Omega$, what is the power absorbed by the $10\ \Omega$ resistor? What power is absorbed by the $30\ \Omega$ resistor?



Q: If a source supplies 300 mW to a parallel combination of $3\text{ k}\Omega$ and $2\text{ k}\Omega$, what is the power absorbed by the $3\text{ k}\Omega$ resistor? What power is absorbed by the $2\text{ k}\Omega$ resistor?


Circuits solved with Ohm's + KCL + KVL

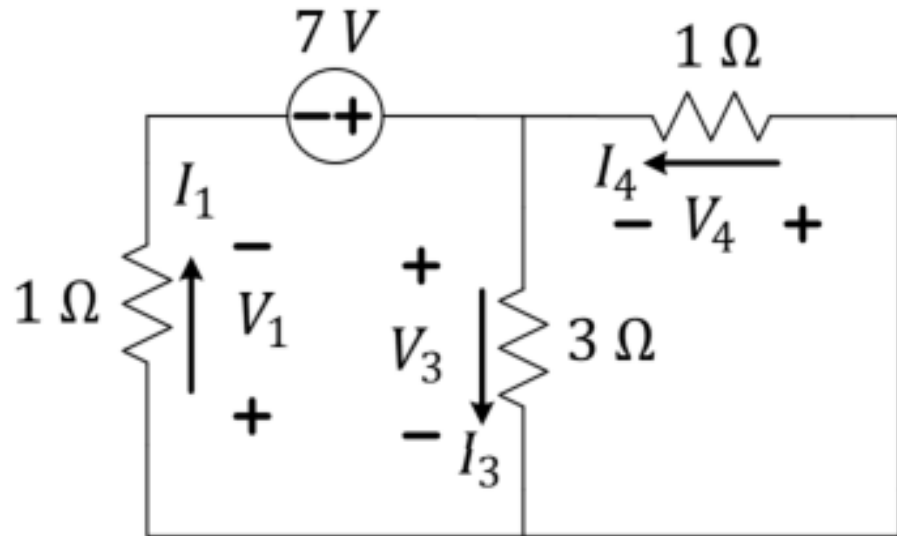

Find the value of the current I_3 .

$$I_3 = 1 A.$$

Circuits solved with Ohm's + KCL + KVL

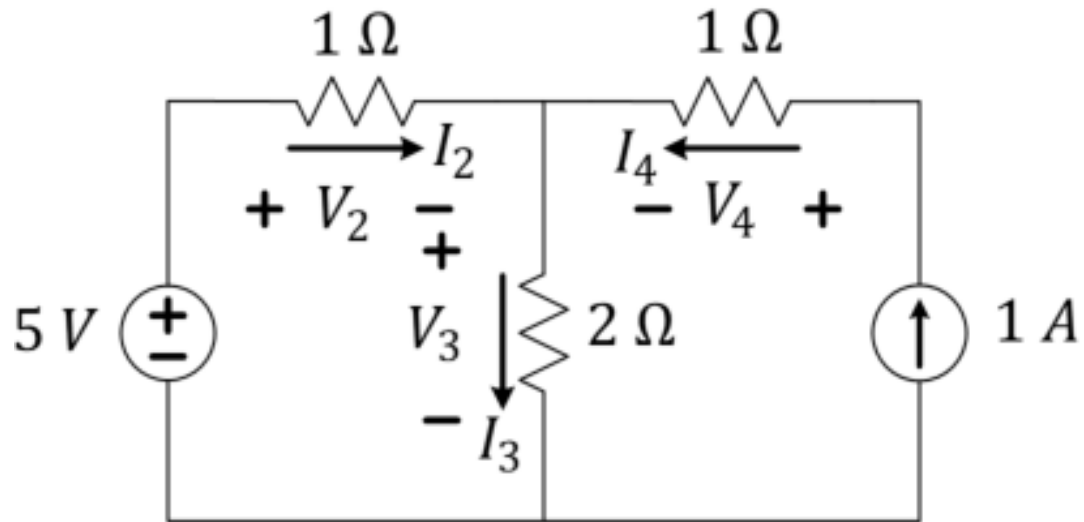

Find the value of the current I_3 .

$$I_3 = 2 A$$



Learning Objectives

- Use resistor ratios to find voltage, current, and power for series and parallel elements.
- More practice on Kirchhoff's Laws for circuit analysis.