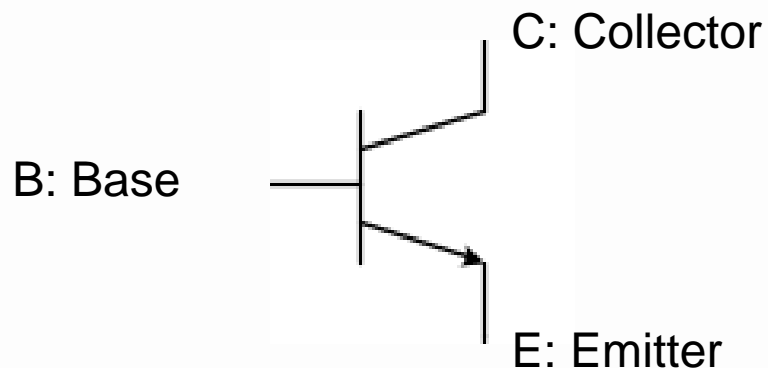


L19: The Bipolar Junction Transistor (BJT)

- BJT is a controlled current source...
 - current amplifier
- The three operating regimes of a BJT
- Controlling a resistive load with a BJT
- Solving for saturation condition



ECE Spotlight...




John Bardeen, the co-inventer of the transistor, was also the Ph.D. advisor at the University of Illinois for Nick Holonyak, Jr. of LED fame.



EXPLORE MORE - Inside the bipolar transistor

Bardeen & Brattain – Point contact

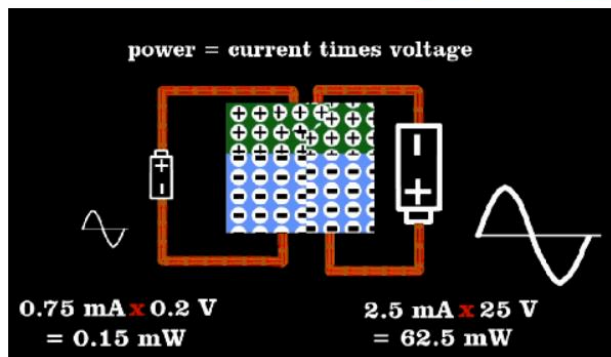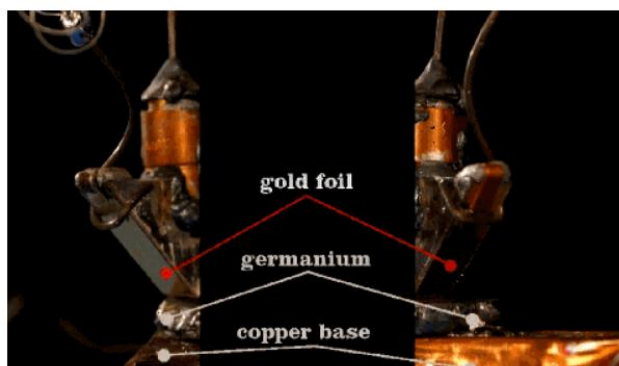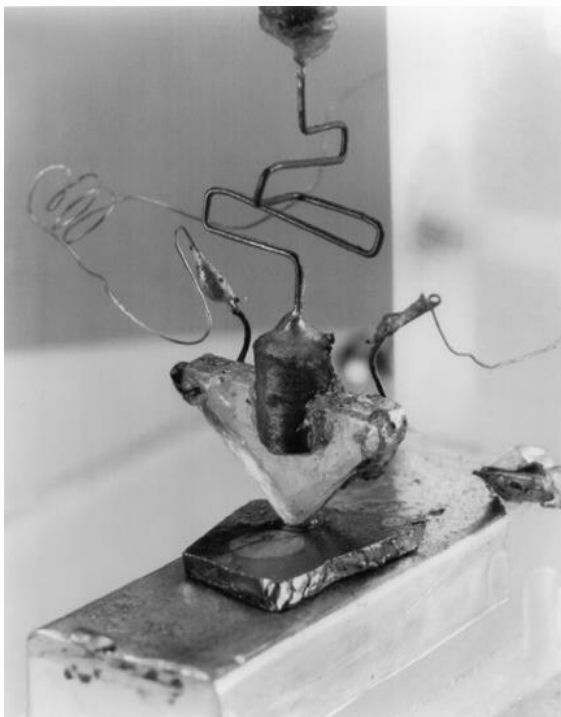In 1947, invention of the point-contact transistor



<https://www.computerhistory.org/siliconengine/invention-of-the-point-contact-transistor/>

<http://www.engineerguy.com/videos.htm#more-videos>

Shockley – p-n junction



In 1956



Photo from the Nobel Foundation archive.
William Bradford Shockley
Prize share: 1/3




John Bardeen
Prize share: 1/3






Photo from the Nobel Foundation archive.
Walter Houser Brattain
Prize share: 1/3

PLANAR TECHNOLOGY



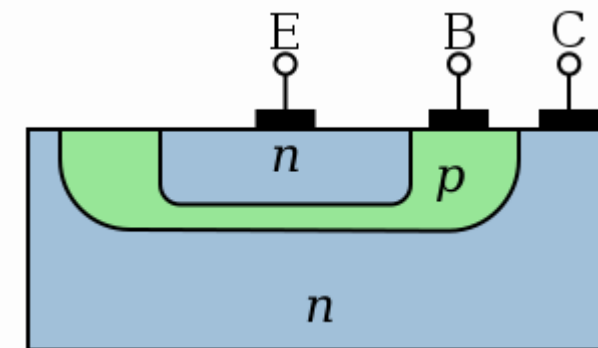


Two types of BJT


NPN

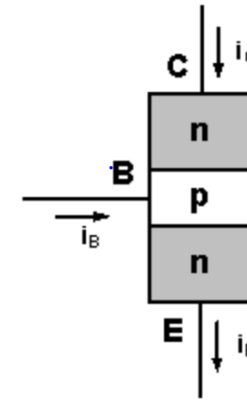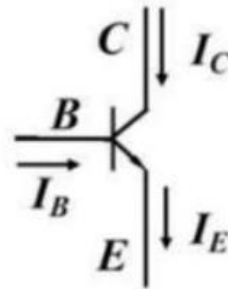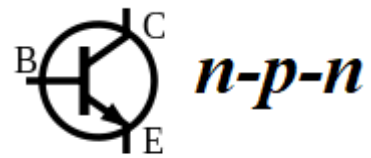

PNP

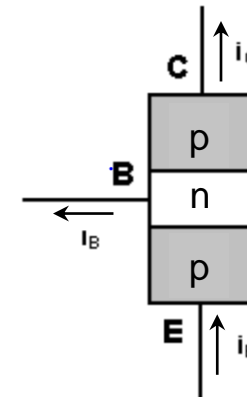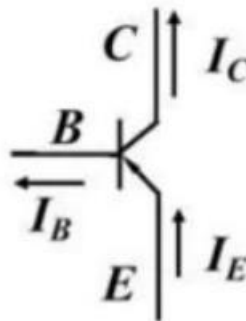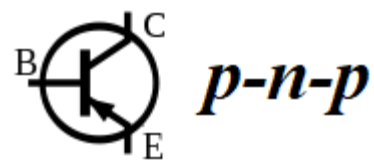


Transistor Trivia: The symbol

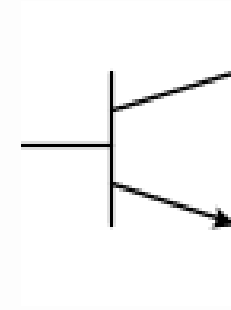

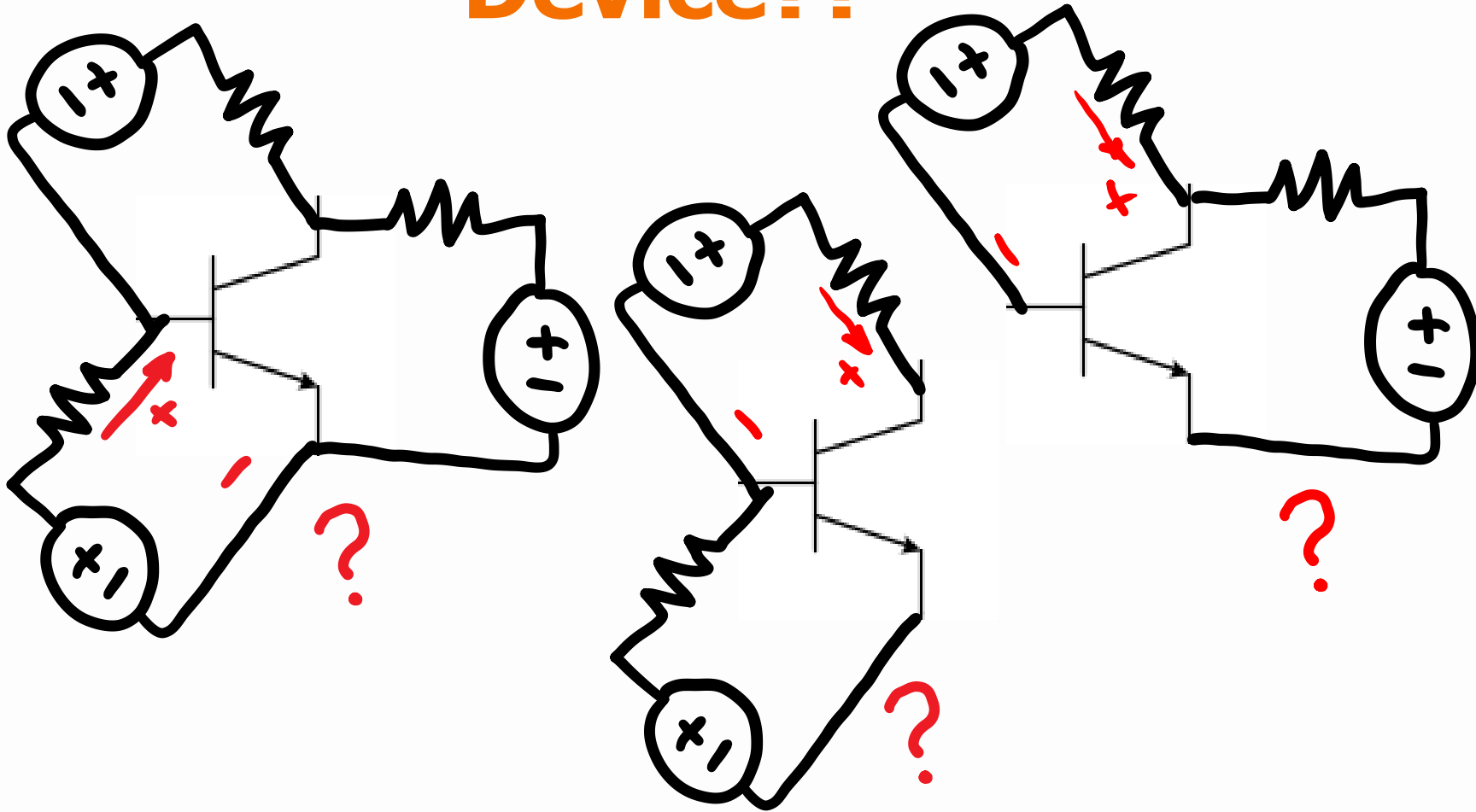- A. was a doodle made by John Bardeen's daughter
- ~~B. represents faithfully the electrical connections of the transistor which need to be resolved exactly with circuit equations~~
- ~~NEVER THIS ONE, PLEASE!!!~~
- C. is simply a conventional representation of a three-terminal bipolar transistor inside a "black box" without specific circuit significance
- D. was the shape of the golden clip, used to tie the red ribbon around the Nobel prize certificate, which Walter Shockley thought could make a good symbol for the device


IV Characteristic of a 3-terminal Device??



No single way to connect three-terminal device to a linear circuit.


**EXPLORE
MORE**

Transistor circuit configurations

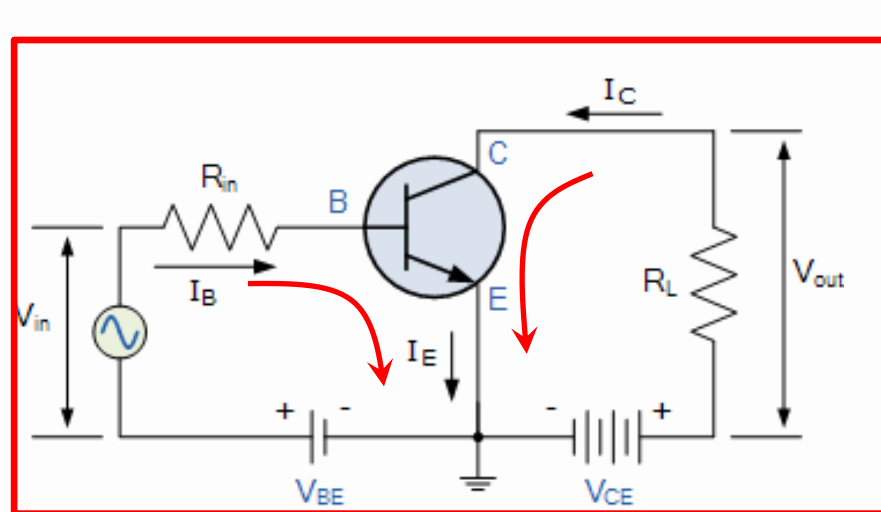


Common Emitter

- Current gain
- Voltage gain

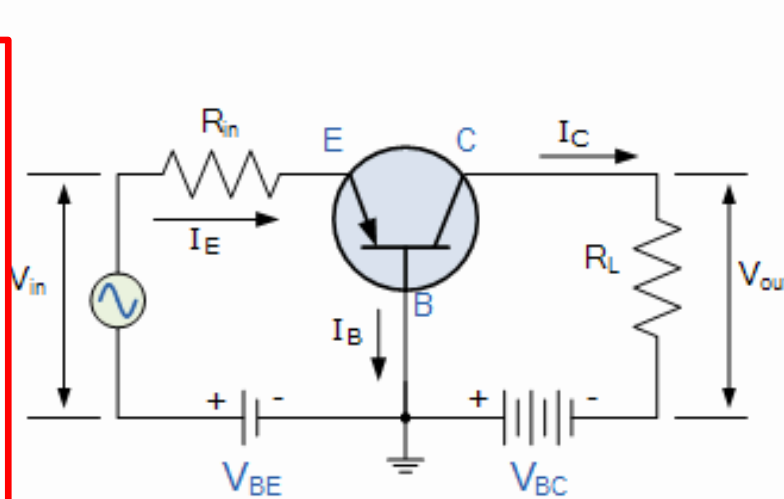

Common Base


- Voltage gain

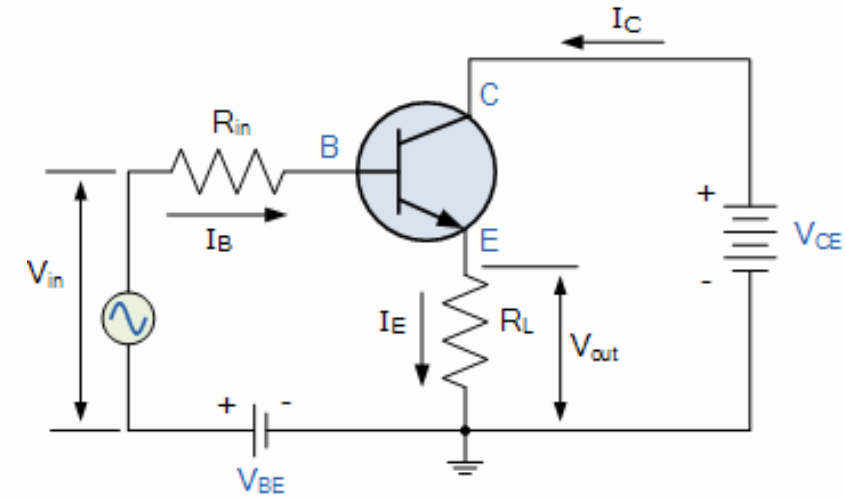


Common Collector

- Current gain

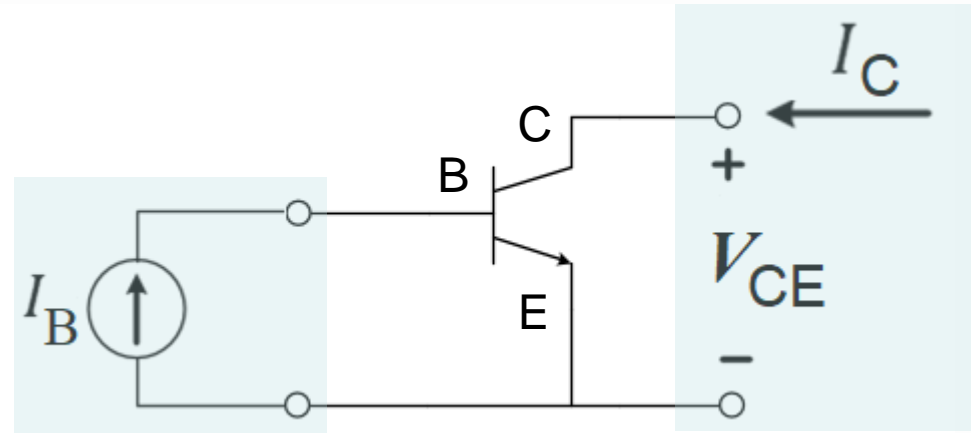
ECE110 considers only the “common-emitter” configuration



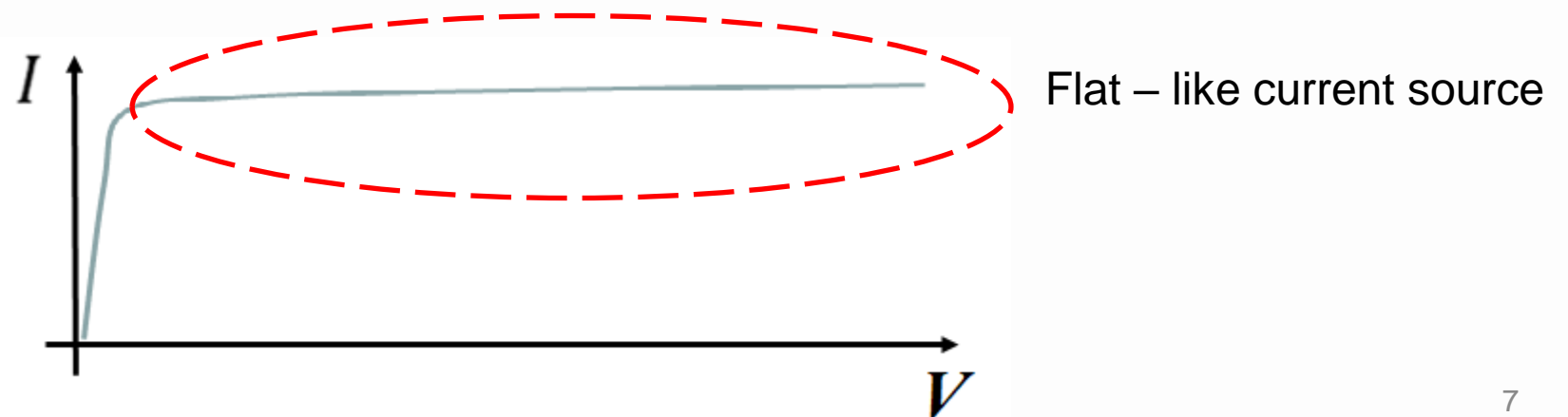If we fix I_B , we can measure the resulting I and V at the other side.



Diode & PN junction

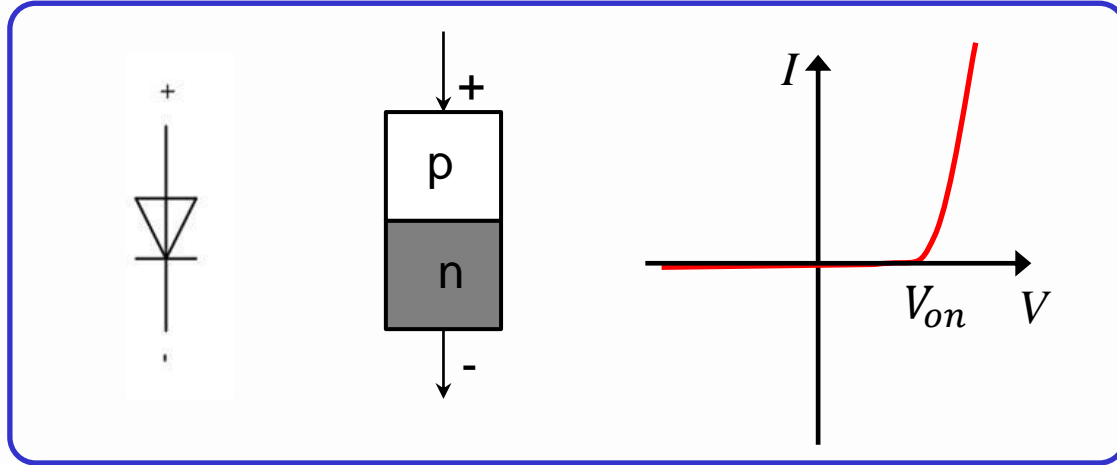

Three operating regimes of BJT

1. Cut-off regime

When $V_{BE} < V_{on}$, $I_B = 0$, $I_C = 0$

In reality, I_C is not exactly zero, due to leakage current. $I_B \approx 0$, $I_C \approx 0$

2. Active regime

When $V_{BE} \geq V_{on}$, $V_C > V_B$

$I_C = \beta I_B$, β is magnification factor, a constant


3. Saturation regime

$V_{BE} \geq V_{on}$

$V_C < V_B$


I_C will not increase with I_B

$\beta I_B > I_C$

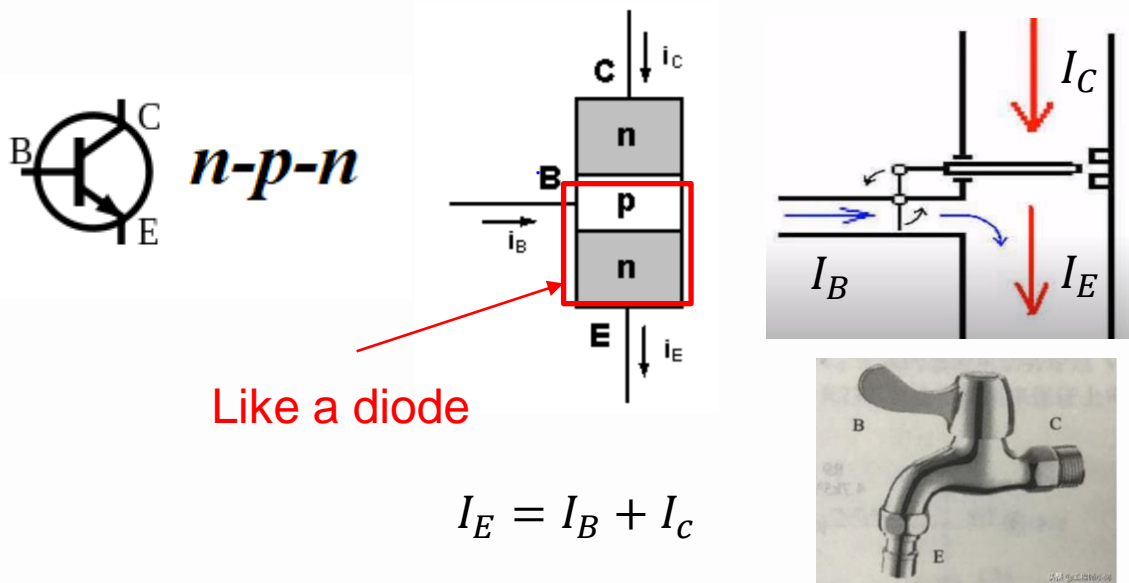


EXPLORE
MORE

BJT Characteristics

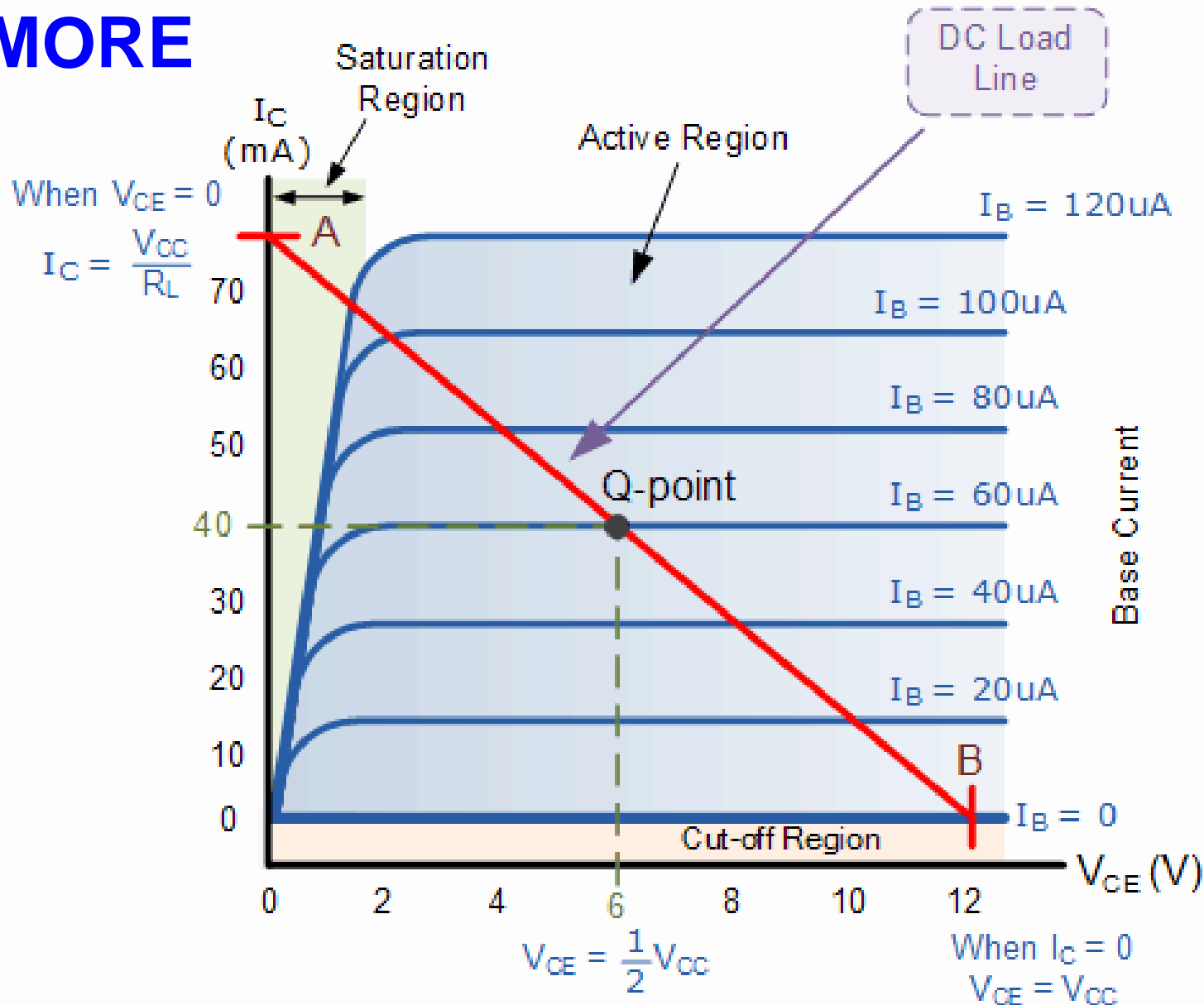

One curve for each value of I_B

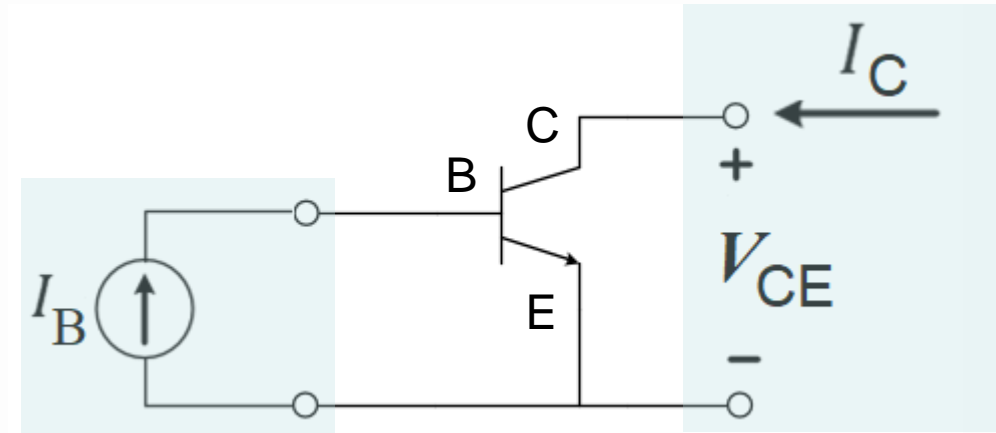

1. Cut-off regime

When $V_{BE} < V_{on}$, thus $I_C \approx 0$

2. Active regime


When $V_{BE} \geq V_{on}$, thus $I_C = \beta I_B$

3. Saturation regime


When $V_{BE} \geq V_{on}$, and $V_C < V_B$

EXPLORE
MORE

BJT as an amplifier or as a switch

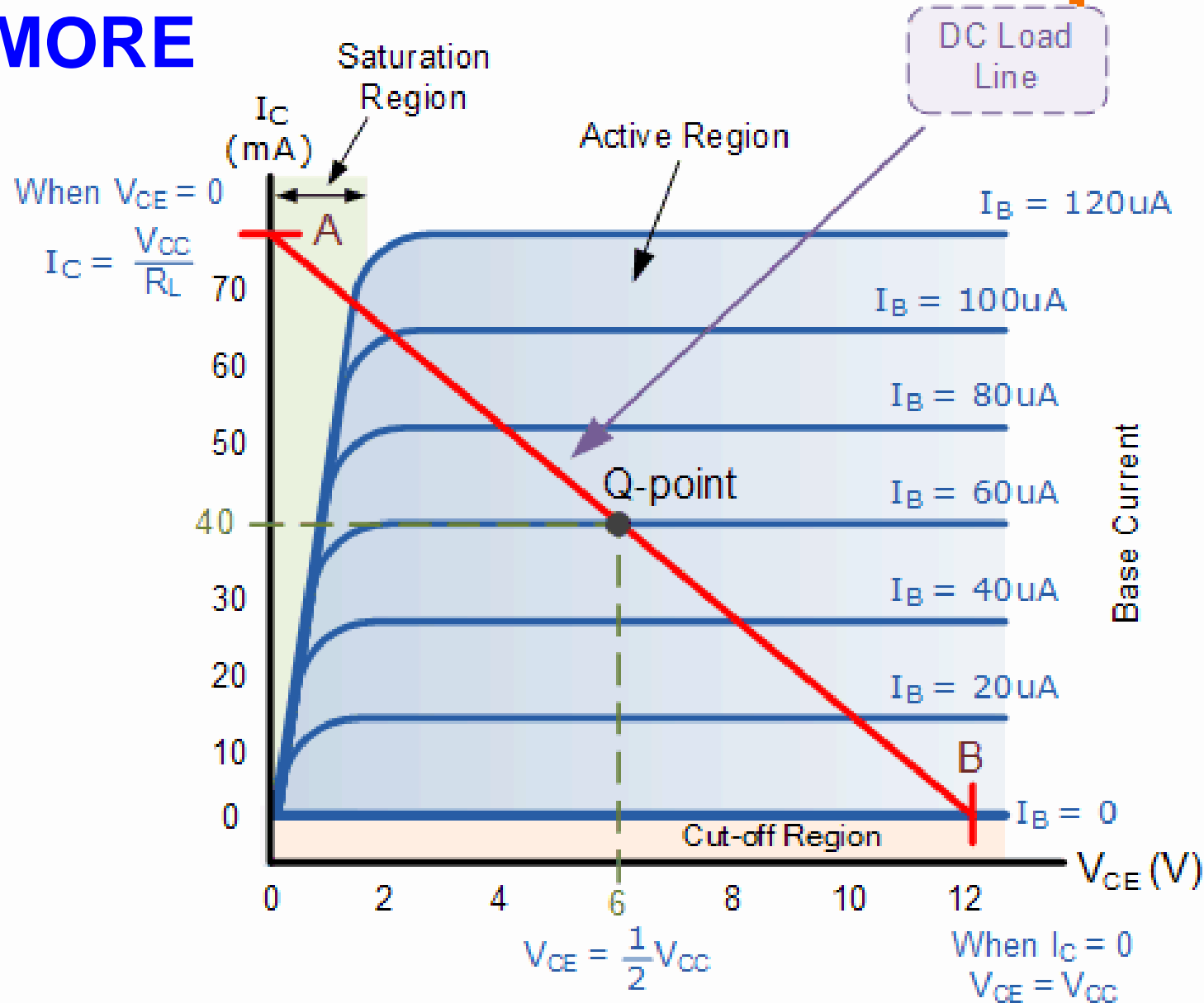



$$I_C = \frac{V_{CC} - V_{CE}}{R_L}$$

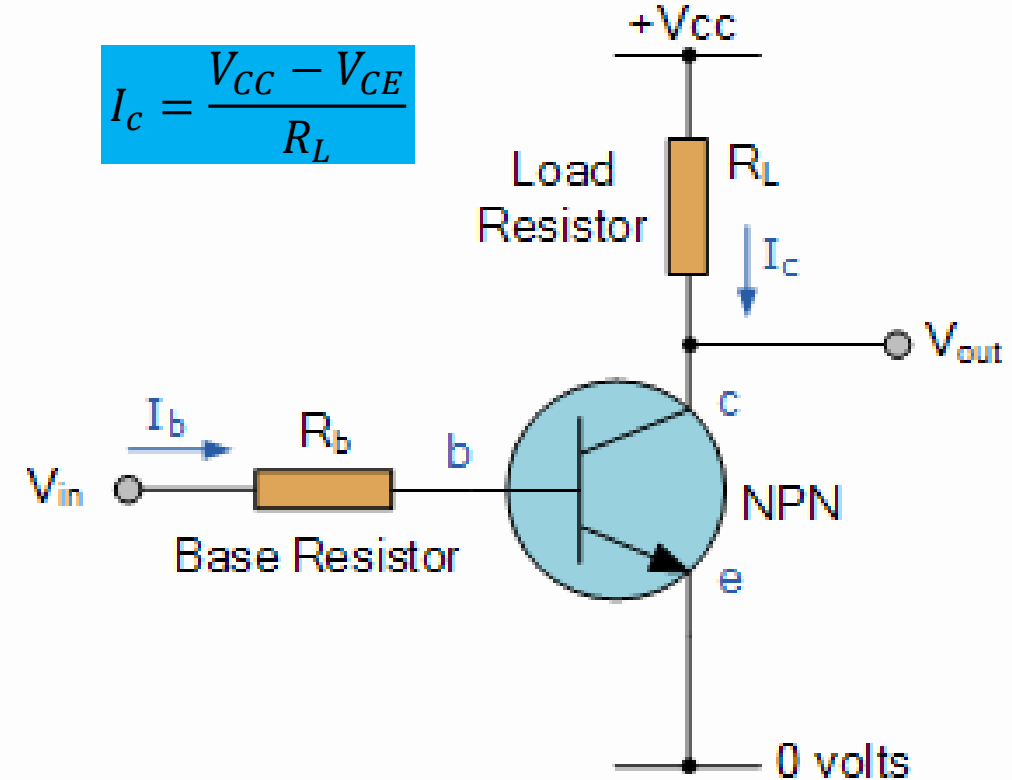

Q bias point – Amplifier

A and B points – Logic Inverter

The BJT's "common-emitter NPN" model

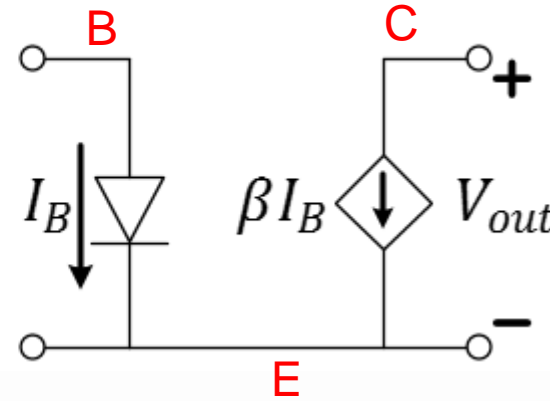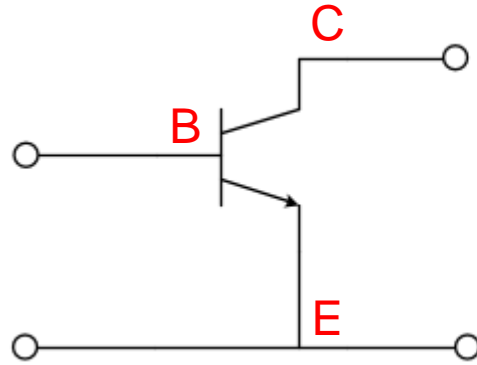

Equivalent model


Constraints:

- Limited current range: $\beta I_B \geq 0$
- Limited voltage range: $V_{out} > 0$

L19Q1: Given these constraints, can this "dependent" current source deliver power?

- A. Yes, all current sources can supply power
- B. No, this current source cannot supply power
- C. Neither A or B is correct.

Two Loops Coupled by Current Equation

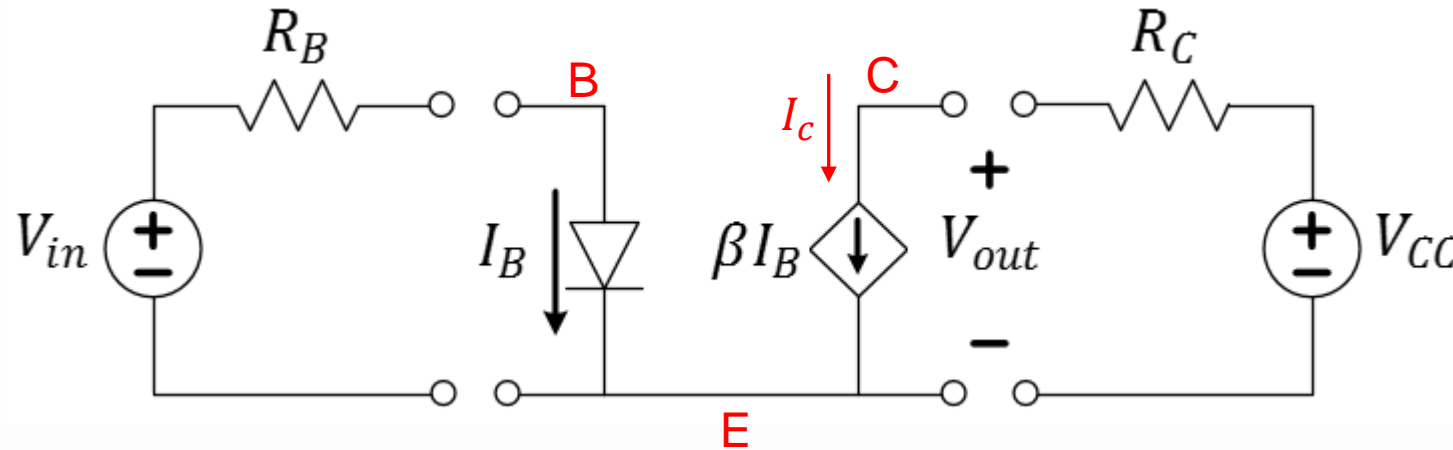

DC bias circuit determines operating point of the transistor

Constraints:


- Limited current range: $0 \leq \beta I_B \leq I_{max}$ (implied by V_{min})
- Limited voltage range: $V_{out} \geq V_{min} \approx 0$

Also called $I_{c,sat}$


$V_{min} = V_{CE,sat}$

MORE

Simplified I-V curves

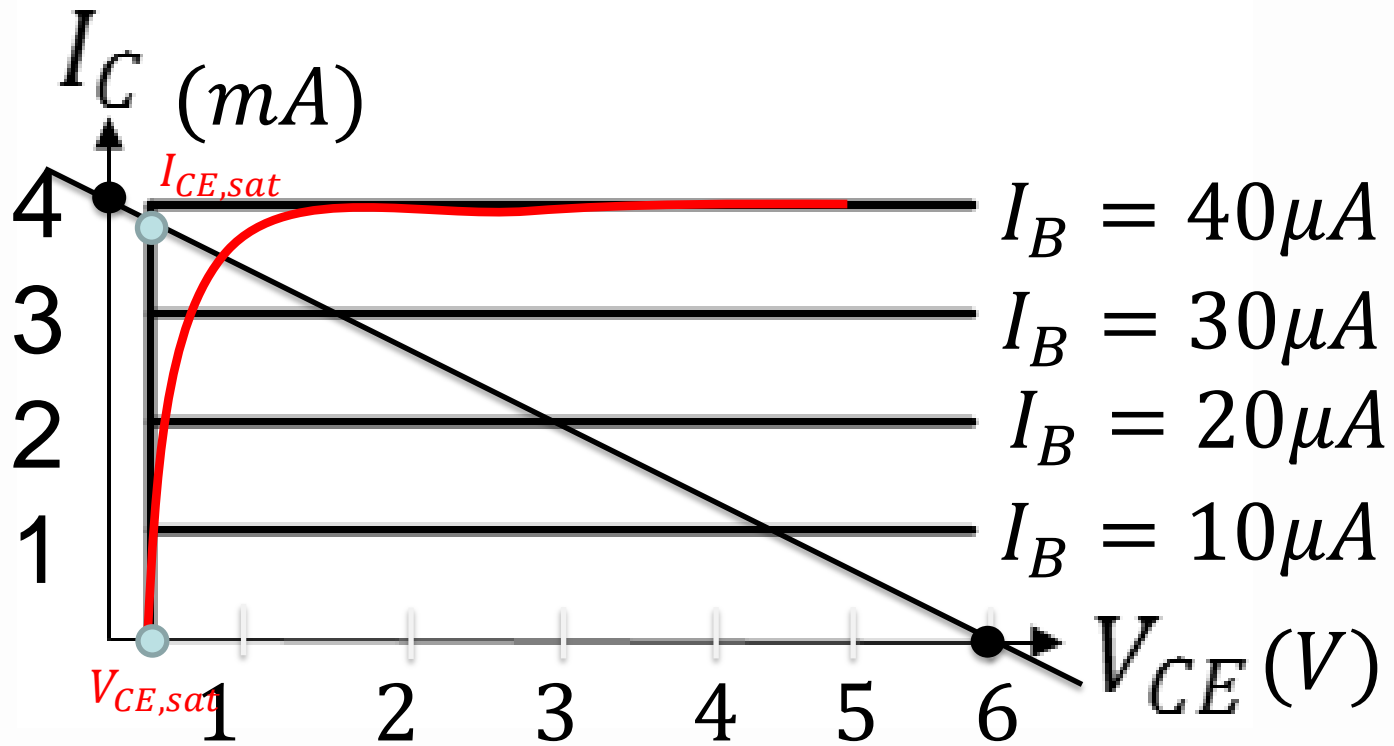


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

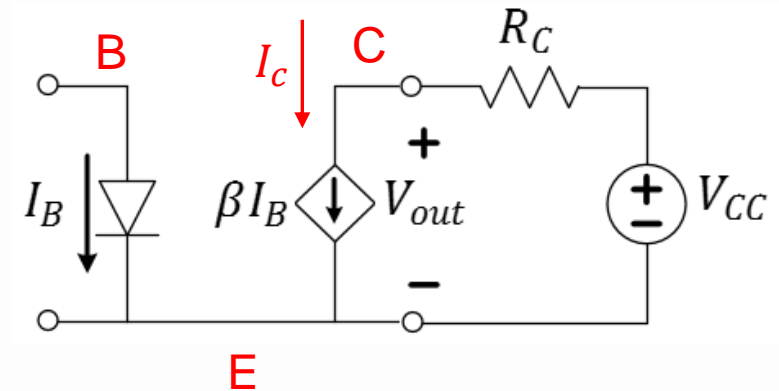

MORE


SUMMARY of technical terminology

$$I_c = \frac{V_{CC} - V_{CE}}{R_C}$$

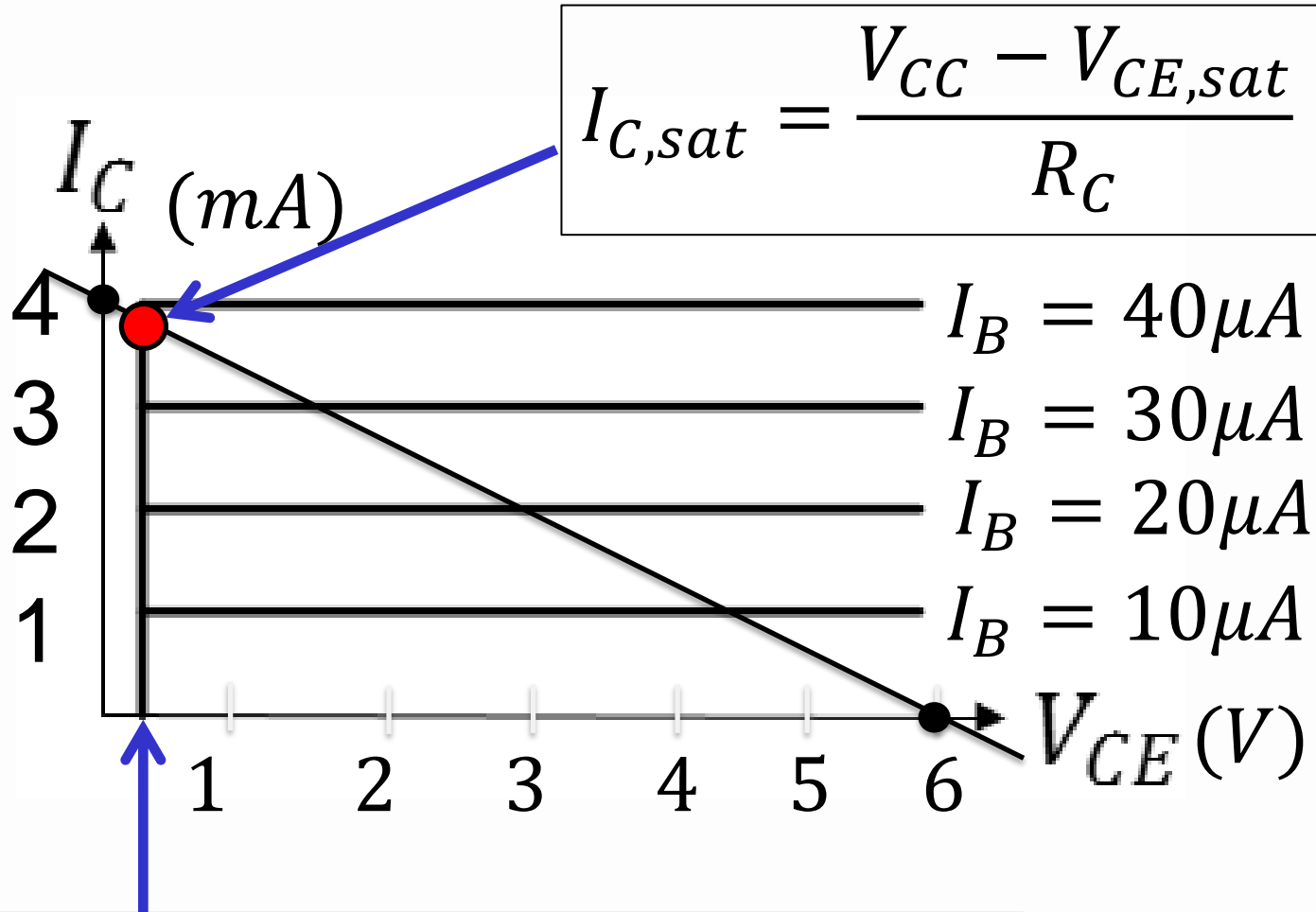

$V_{CE,sat} \approx$ typically 0.2V to 0.3V

$$I_C = \min\{\beta I_B, I_{C,sat}\}$$

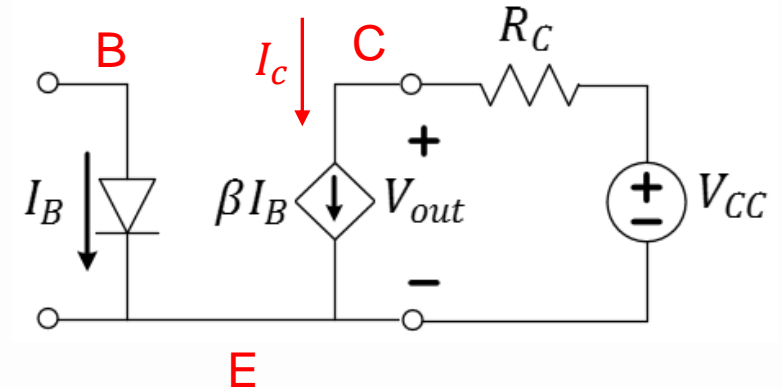

$$I_{max} = I_{C,sat}$$

$$V_{min} = V_{CE,sat}$$

MORE


SUMMARY of technical terminology

- In **saturation** the collector current cannot grow any longer if the base current is increased. Therefore:

$$I_C = I_{C,sat} < \beta I_B$$

- At the same time, the voltage between collector and emitter (V_{CE}) reaches its lowest possible level ($V_{CE,sat}$)

Two Loops Coupled by Current Equation

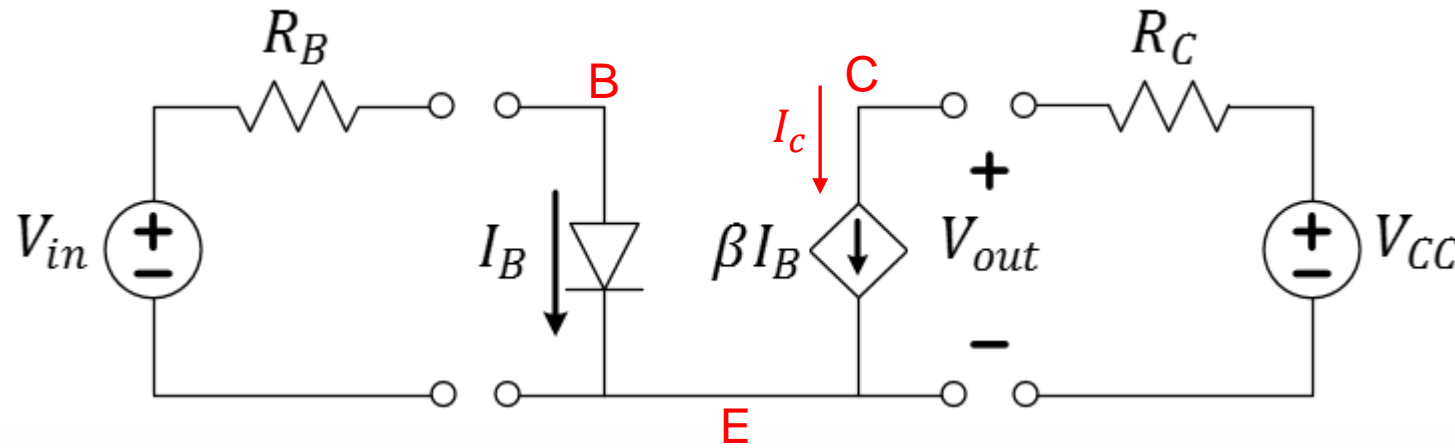


L19Q2: Right-side KVL: Find an equation relating I_{max} to V_{min} .

L19Q3: Left-side KVL: Find the smallest V_{in} such that $I_B > 0$ (if $V_{on} = 0.7\text{ V}$)?

L19Q4: What is I_B if $V_{in} = 3\text{ V}$ and $R_B = 4.6\text{ k}\Omega$?

L19Q5: Let $V_{CC} = 6\text{ V}$, $R_C = 580\text{ }\Omega$, $V_{min} = 0.2\text{ V}$, $\beta = 100$. What is I_C under the same input settings as the previous question?

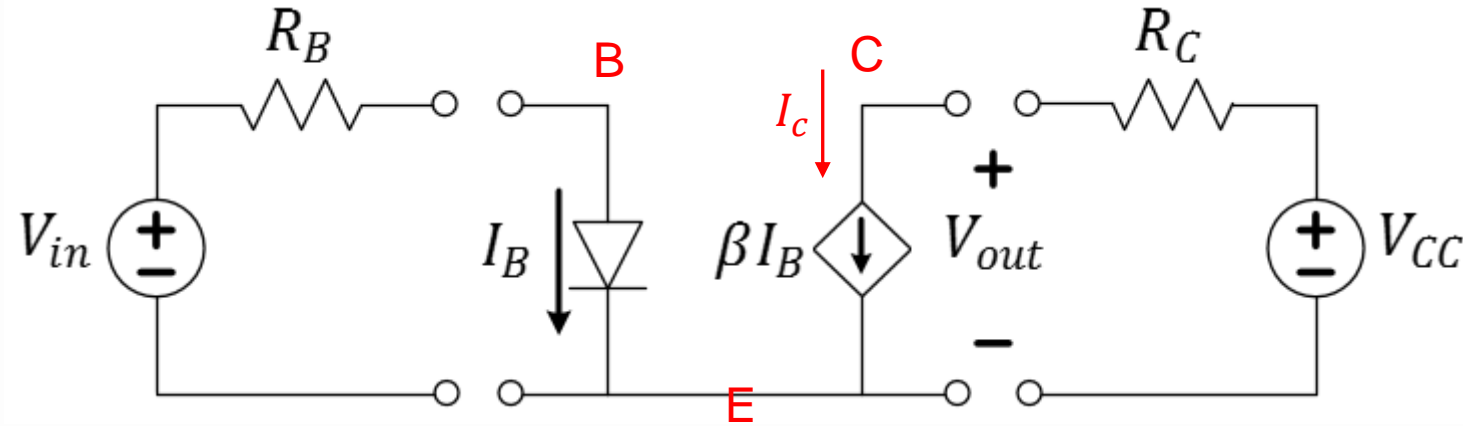L19Q2: Right-side KVL: Find an equation relating I_{max} to V_{min} .




$$I_{max} = I_{C,sat}$$
$$V_{min} = V_{CE,sat}$$

$$I_{max} = I_{C,sat} = \frac{V_{CC} - V_{min}}{R_C} = \frac{V_{CC} - V_{CE,sat}}{R_C}$$

L19Q3: Left-side KVL: Find the smallest V_{in} such that $I_B > 0$ (if $V_{on} = 0.7 V$)?

$$V_{in} > V_{on} = 0.7V \quad \Rightarrow \quad I_B > 0$$

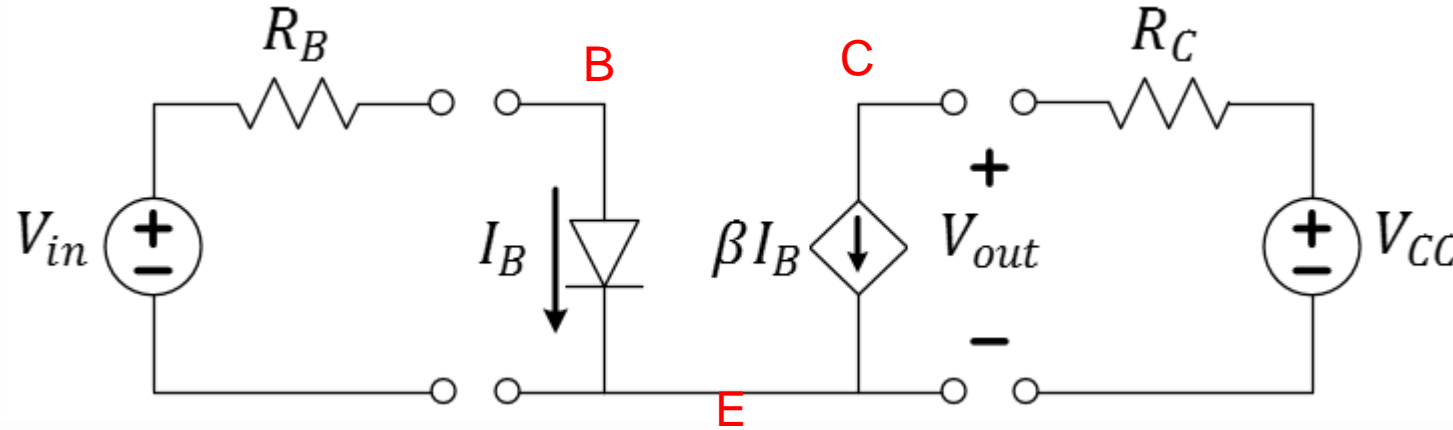L19Q4 -What is I_B if $V_{in} = 3\text{ V}$ and $R_B = 4.6\text{ k}\Omega$?




- By Ohm's Law (Nodal method)

$$I_B = \frac{3 - 0.7}{4.6k} = 0.5\text{ mA}$$

$$I_B = \frac{V_{in} - V_{on}}{R_B}$$

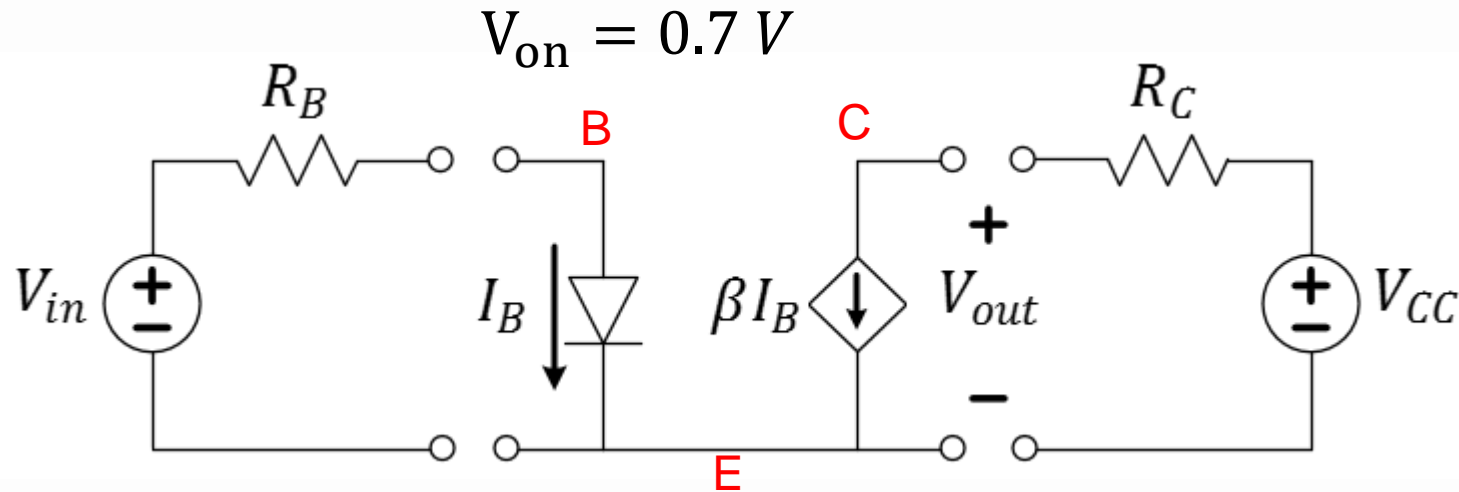L19Q5 - Let $V_{CC} = 6\text{ V}$, $R_C = 580\ \Omega$, $V_{min} = 0.2\text{ V}$, $\beta = 100$. What is I_C with the previous input settings ($V_{in} = 3\text{ V}$ and $R_B = 4.6\text{ k}\Omega$)



$$I_C = 100I_B = 50\text{ mA}.$$

We need to verify that $I_C < I_{C,sat}$ Working in active regime

$$\text{Since: } I_{C,sat} = \frac{V_{CC} - V_{min}}{R_C} = \frac{5.8}{580} = 100\text{ mA} > 50\text{ mA}$$

$\Rightarrow 50\text{ mA}$ looks OK

BJT Datasheet Parameters

2N5192G

ELECTRICAL CHARACTERISTICS* ($T_C = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS (Note 1)				
DC Current Gain ($I_C = 1.5 \text{ Adc}$, $V_{CE} = 2.0 \text{ Vdc}$) 2N5190G/2N5191G 2N5192G ($I_C = 4.0 \text{ Adc}$, $V_{CE} = 2.0 \text{ Vdc}$) 2N5190G/2N5191G 2N5192G	h_{FE}	25 20 10 7.0	100 80 – –	–
Collector-Emitter Saturation Voltage ($I_C = 1.5 \text{ Adc}$, $I_B = 0.15 \text{ Adc}$) ($I_C = 4.0 \text{ Adc}$, $I_B = 1.0 \text{ Adc}$)	$V_{CE(sat)}$	– –	0.6 1.4	Vdc
Base-Emitter On Voltage ($I_C = 1.5 \text{ Adc}$, $V_{CE} = 2.0 \text{ Vdc}$)	$V_{BE(on)}$	–	1.2	Vdc

 $\approx \beta$
 $V_{CE,sat}$
 $V_{BE,on} \leq$

L19Q6: Approximate the values of β , V_{BEon} , and $V_{CE,sat}$ from the datasheet.

BJT Datasheet Parameters

2N5192G

h_{FE} = small signal gain
 β = d.c. gain (a.k.a. H_{FE})
 $\beta \approx h_{FE}$

ELECTRICAL CHARACTERISTICS* ($T_C = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS (Note 1)				
DC Current Gain ($I_C = 1.5 \text{ Adc}$, $V_{CE} = 2.0 \text{ Vdc}$) 2N5190G/2N5191G 2N5192G	h_{FE}	25 20	100 80	-
($I_C = 4.0 \text{ Adc}$, $V_{CE} = 2.0 \text{ Vdc}$) 2N5190G/2N5191G 2N5192G		10 7.0	- -	
Collector-Emitter Saturation Voltage ($I_C = 1.5 \text{ Adc}$, $I_B = 0.15 \text{ Adc}$) ($I_C = 4.0 \text{ Adc}$, $I_B = 1.0 \text{ Adc}$)	$V_{CE(sat)}$	- -	0.6 1.4	Vdc
Base-Emitter On Voltage ($I_C = 1.5 \text{ Adc}$, $V_{CE} = 2.0 \text{ Vdc}$)	$V_{BE(on)}$	-	1.2	Vdc

$\approx \beta$

$V_{CE,sat}$
 $V_{BE,on} \leq$

L19Q6: Approximate the values of β , V_{BEon} , and $V_{CE,sat}$ from the datasheet.

$\beta \approx 20 \text{ to } 50$, $V_{BEon} \approx 0.6 \text{ to } 1 \text{ V}$, $V_{CEsat} \approx 0.6 \text{ to } 1.2 \text{ V}$


BJT in Active Region

BJT datasheet parameters:

- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$

L19Q7: Find I_B .

L19Q8: Find I_C .

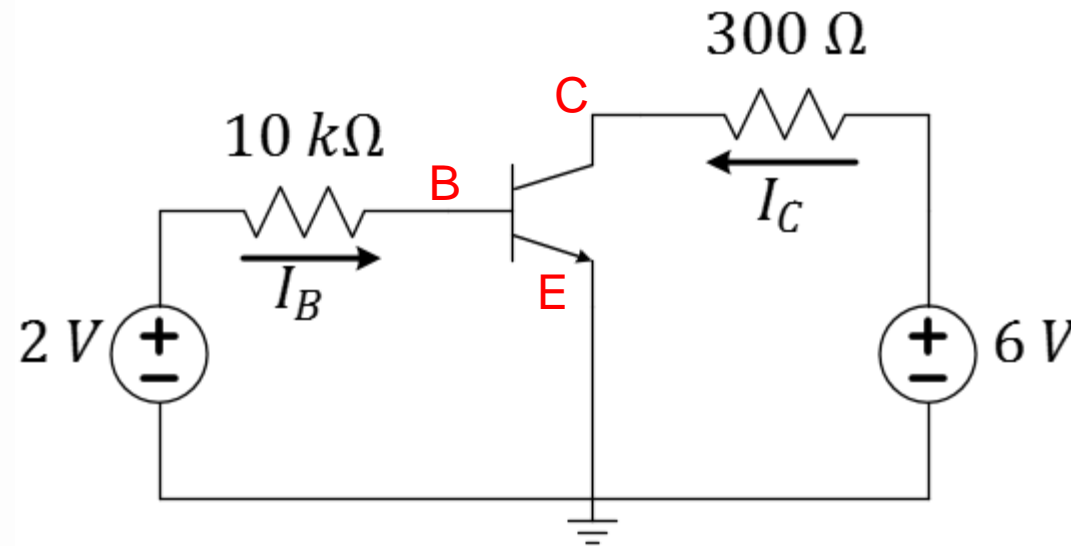


Q7:

- A. $I_B = 0\text{ }\mu\text{A}$
- B. $I_B = 1\text{ }\mu\text{A}$
- C. $I_B = 2\text{ }\mu\text{A}$
- D. $I_B = 10\text{ }\mu\text{A}$
- E. $I_B = 100\text{ }\mu\text{A}$

BJT in Active Region – L19Q7: Find I_B

BJT datasheet parameters:

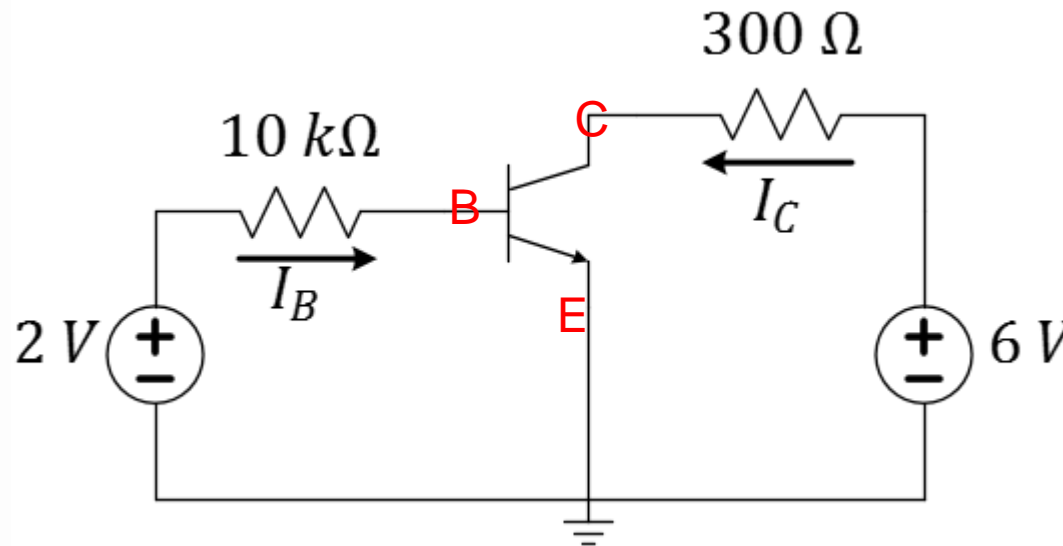- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$



Q7:


- A. $I_B = 0\text{ }\mu\text{A}$
- B. $I_B = 1\text{ }\mu\text{A}$
- C. $I_B = 2\text{ }\mu\text{A}$
- D. $I_B = 10\text{ }\mu\text{A}$
- E. $I_B = 100\text{ }\mu\text{A}$

$$I_B = \frac{V_{in} - V_{BE,on}}{10k} = \frac{2 - 1}{10k} = 0.1\text{mA} = 100\mu\text{A}$$

BJT in Active Region – L19Q8: Find I_C

BJT datasheet parameters:

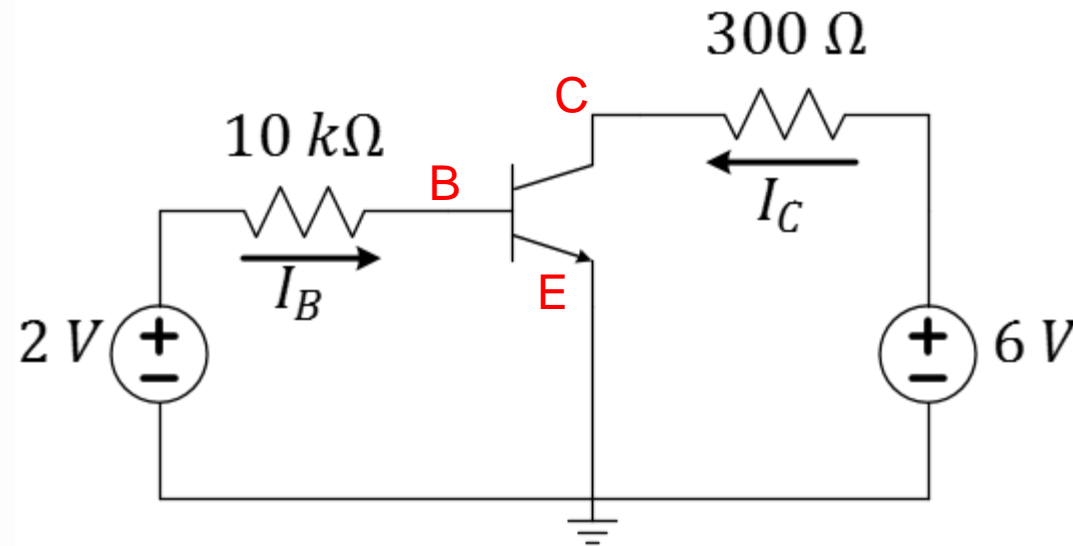- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$



$$I_C = \beta I_B = 10\text{mA}$$

$$I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{300} = \frac{6 - 0.2}{300} = 19.3\text{mA}$$


BJT in Cutoff

BJT datasheet parameters:

- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$

L19Q9: Find I_B .

L19Q10: Find I_C .

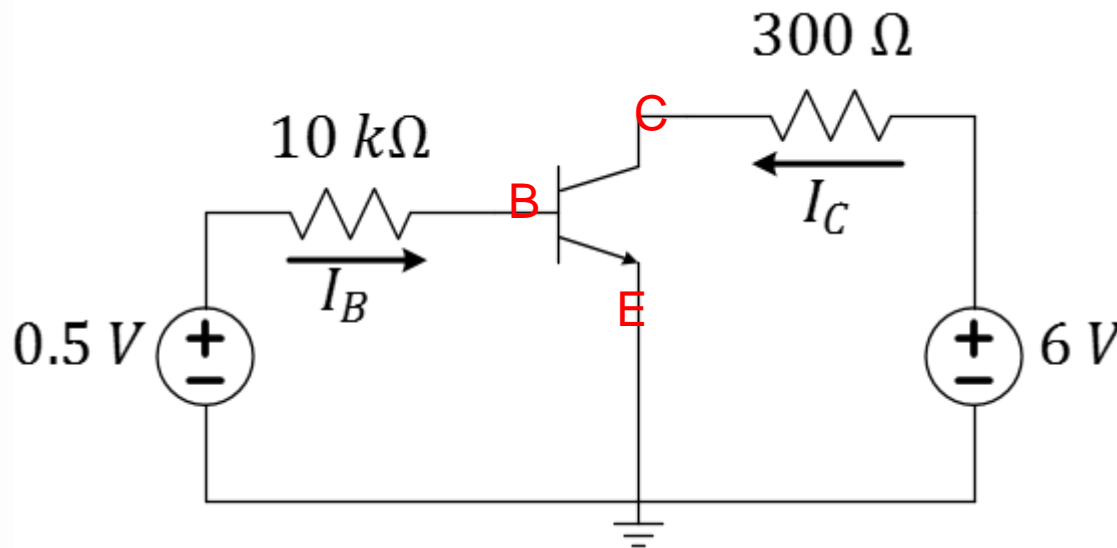

$$V_{in} = 0.5\text{ V} < V_{BE,on}$$

$$I_B \approx 0 \quad \& \quad I_C \approx 0$$


BJT in Saturation

BJT datasheet parameters:

- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$

L19Q11: Find I_B .


L19Q12: Find I_C .

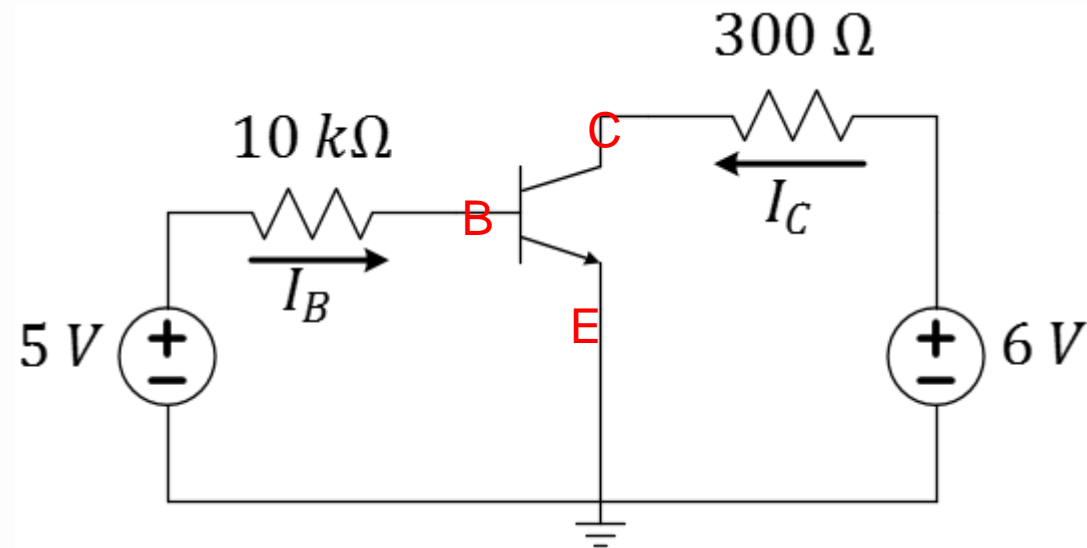

BJT in Saturation

BJT datasheet parameters:

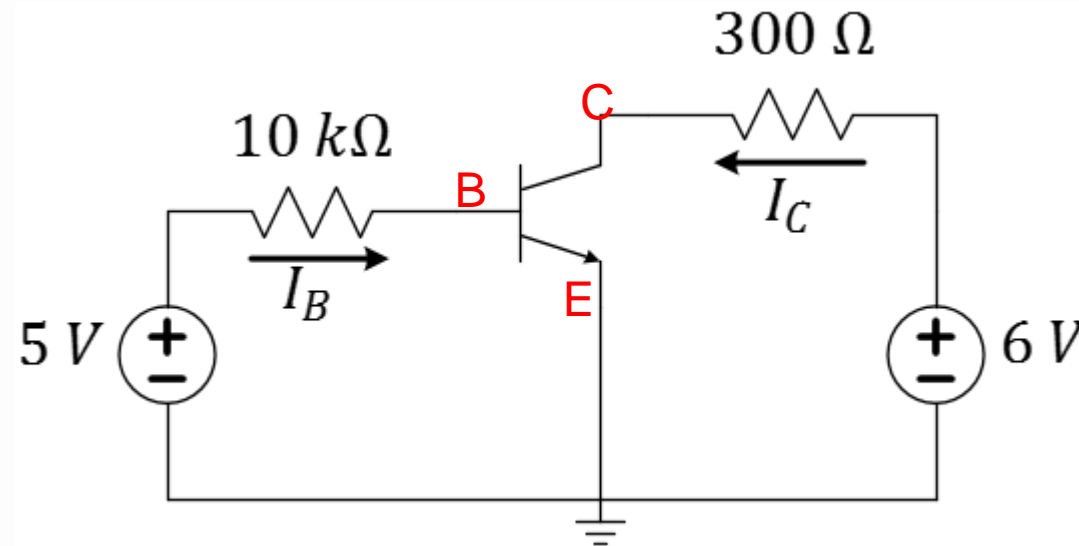- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$



$$I_B = \frac{V_{in} - V_{BE,on}}{10k} = \frac{5 - 1}{10k} = 0.4\text{mA} = 400\mu\text{A}$$


$$I_C = \beta I_B = 40\text{mA} > I_{C,sat} = 19.3\text{mA} \quad (\text{cannot be supplied})$$

$$I_C = I_{C,sat} = 19.3\text{ mA}$$

BJT Exercise

BJT datasheet parameters:

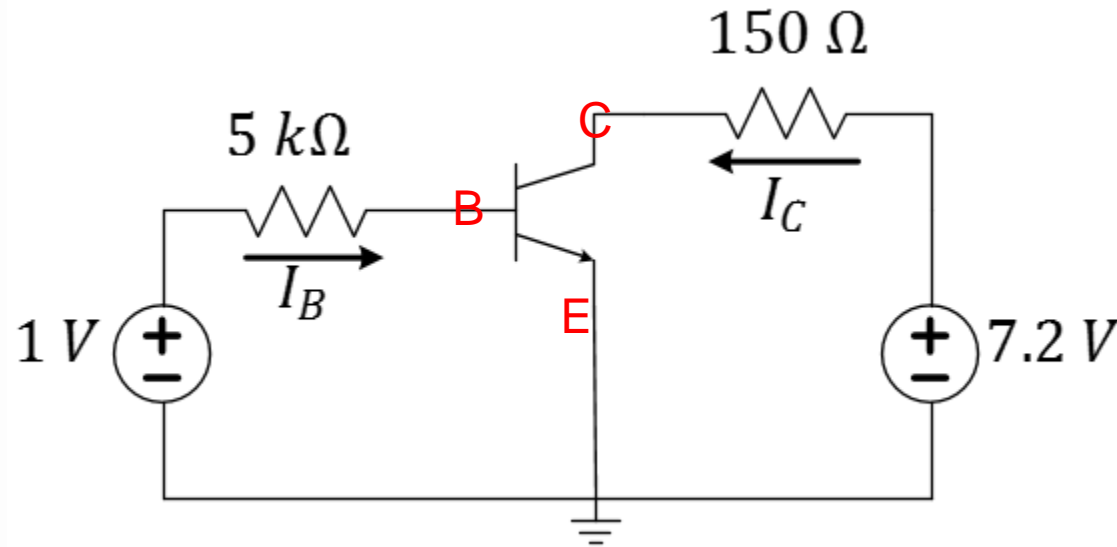- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$




L19Q13: Find I_C and identify in which regime the transistor is operating.

L19Q13: Find I_C and identify in which regime the transistor is operating.

BJT datasheet parameters:

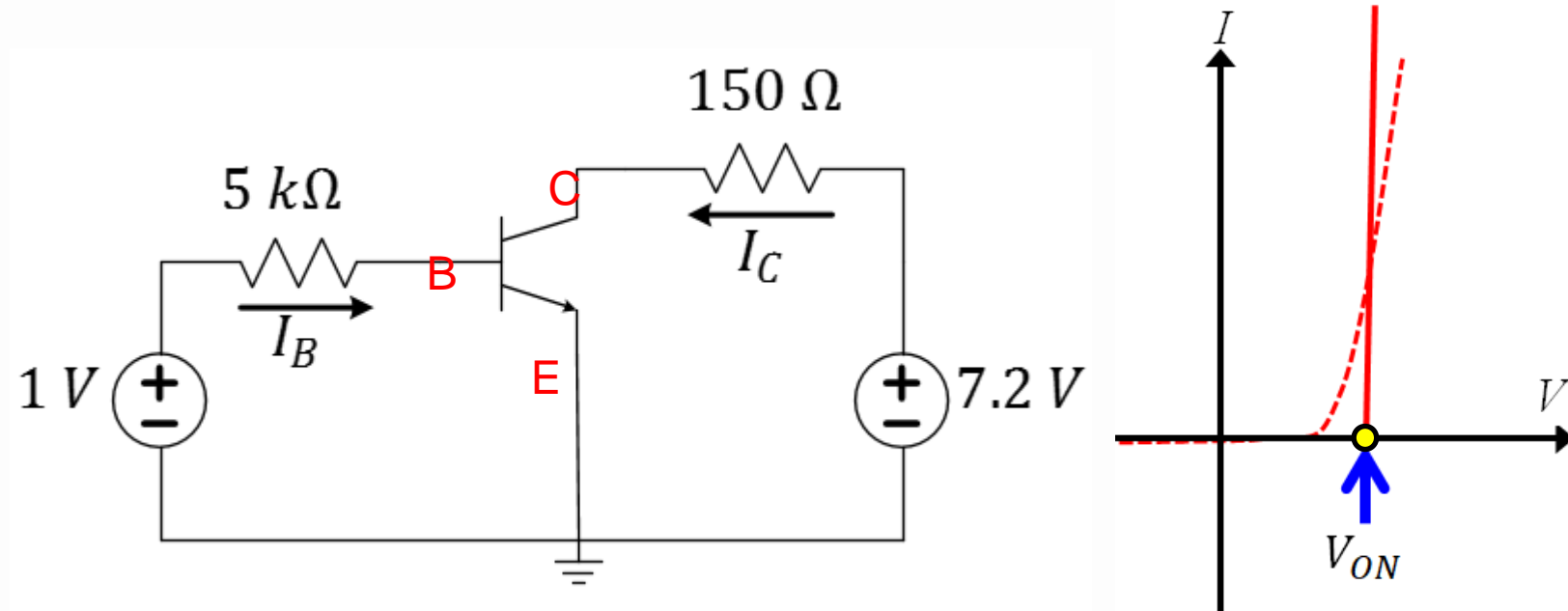- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$



$$I_B = \frac{V_{in} - V_{BE,on}}{10k} = \frac{1 - 1}{10k} = 0\text{ A}$$


$$I_C = 0$$

Right at the boundary between “cutoff” and “active” regime (corner point)

BJT Exercise

BJT datasheet parameters:

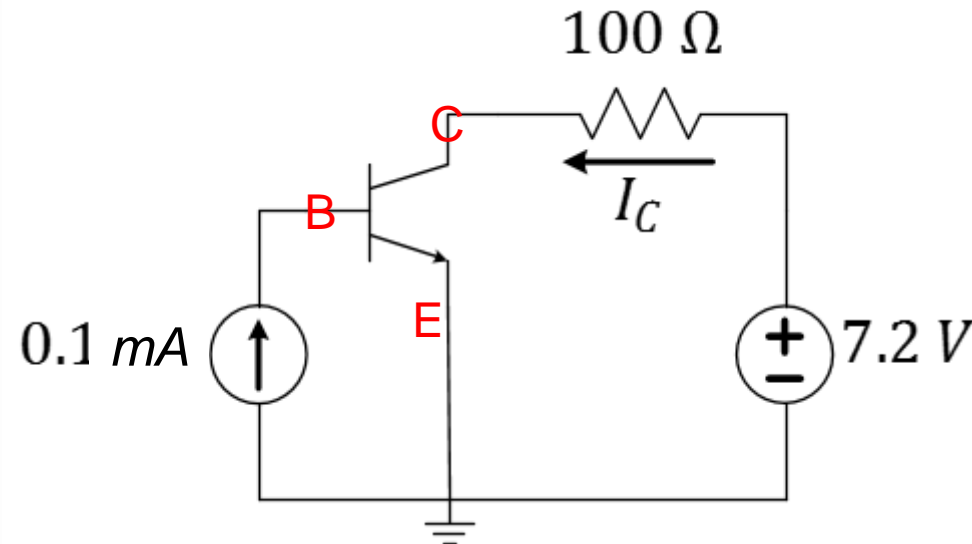- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$



L19Q14: Find I_C and identify in which regime the transistor is operating.


L19Q15: Determine the power consumed by the transistor.

L19Q14: Find I_C and identify in which regime the transistor is operating

L19Q15: Determine the power consumed by the transistor

BJT datasheet
parameters:

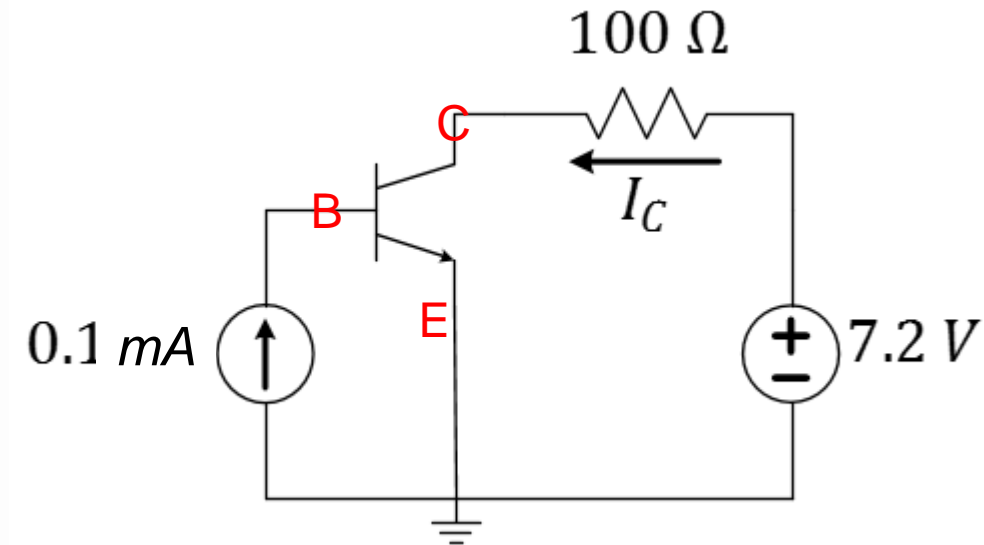- $\beta = 100$
- $V_{BE,on} = 1\text{ V}$
- $V_{CE,sat} = 0.2\text{ V}$






$$I_C = \beta I_B = 10\text{mA} \quad \left(I_{C,sat} = \frac{7.2 - 0.2}{100} = 70\text{mA} \right) \quad \begin{matrix} I_C < I_{C,sat} \\ \text{Active regime} \end{matrix}$$

$$\begin{aligned} P &= V_{BE,on} I_B + V_{CE} I_C = 1 \times 0.1\text{m} + (7.2 - 100 \times 10\text{m}) \times 10\text{m} \\ &= 0.1\text{mW} + 62\text{mW} = 62.1\text{mW} \end{aligned}$$

MORE

Summary n-p-n BJT regimes

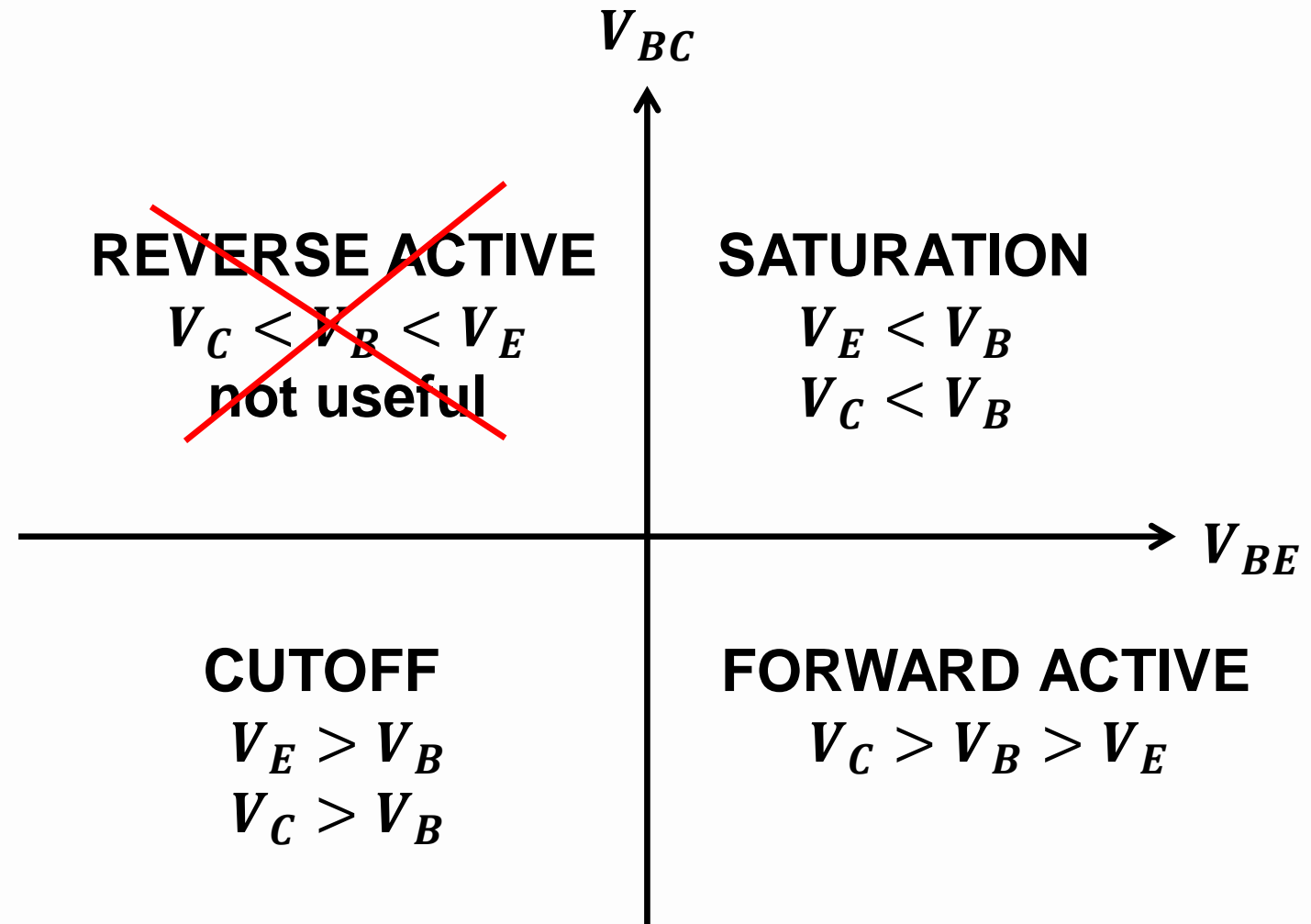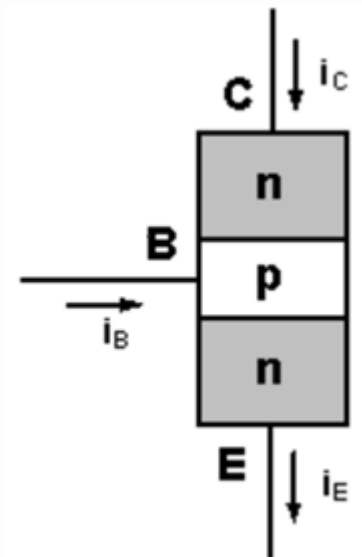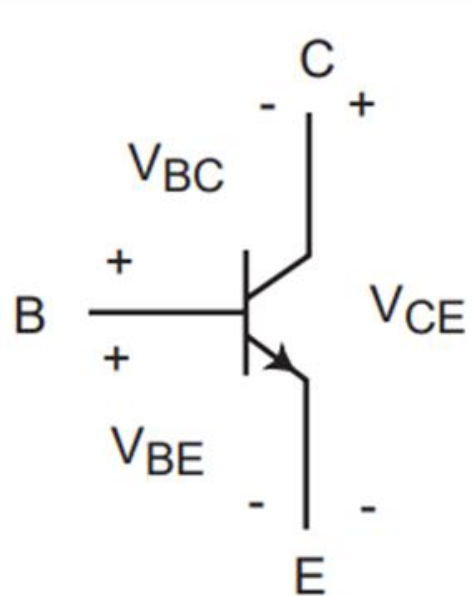

L19 Learning Objectives

- a. Identify B, E, C terminals on an npn-BJT symbol
- b. Explain BJT's three regimes of operation
- c. Calculate active-regime I_C using V_{BEon} in the BE loop
- d. Calculate maximum I_C based on $V_{CE,sat}$ and CE loop
- e. Calculate I_C given complete biasing conditions and transistor parameters, no matter which regime
- f. Calculate the power dissipated by a transistor