
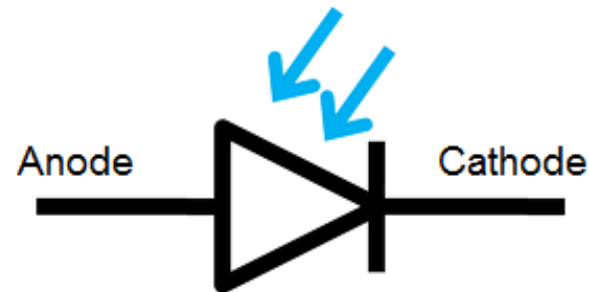



Lecture 16: Introduction to Diodes

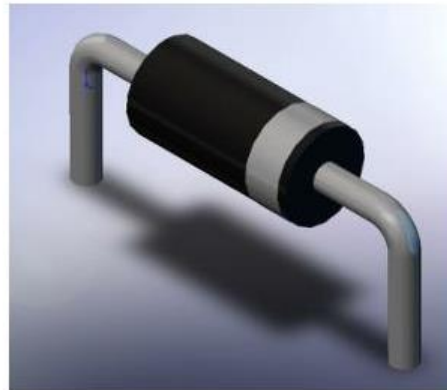- Diode IV characteristics
- Connecting diode to a linear circuit
- Piecewise linear models of diodes



Recommended: <https://learn.sparkfun.com/tutorials/diodes>


■ IV characteristics

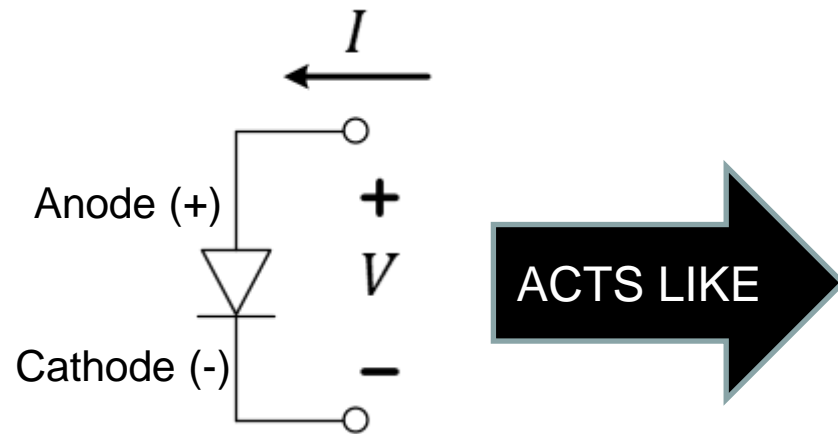


Mathematical expression

$$I \approx I_S (e^{V/nV_{therm}} - 1)$$

$$V_{therm} = k_B T / q$$

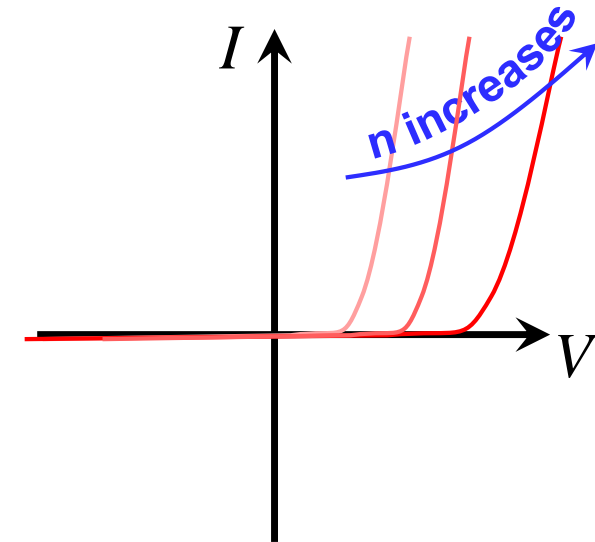

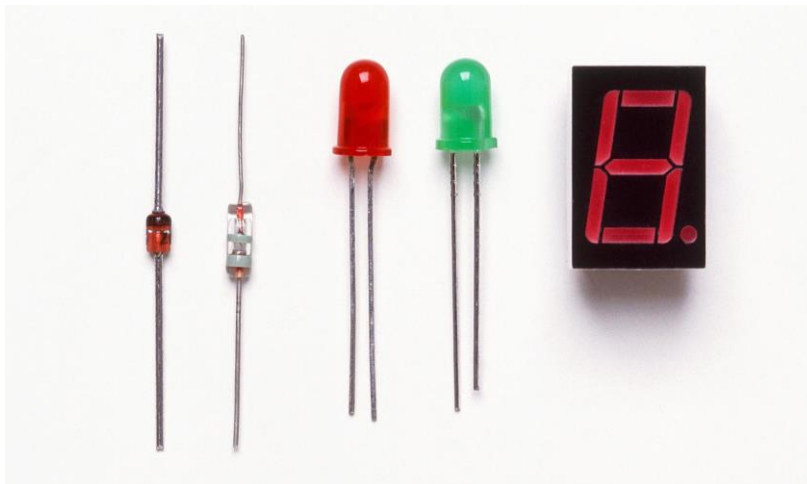■ Major applications: lighting, electronics



Made of *semiconductor* materials like Si, Ge, GaN with some additives called *dopants*.

■ Date sheet

$$I \approx I_S (e^{V/nV_{therm}} - 1)$$

$$V_{therm} = \frac{k_B T}{q} \text{ (thermal voltage)}$$


$$\frac{k_B}{q} = 8.617 \times 10^{-5} eV \cdot K^{-1} \text{ (Boltzmann's constant)}$$

T = temperature (Kelvin)



$$\frac{k_B T}{q} = 25.85 mV \text{ at } 300K$$

n = ideal factor
(depends on device fabrication parameters)


■ Circuit model

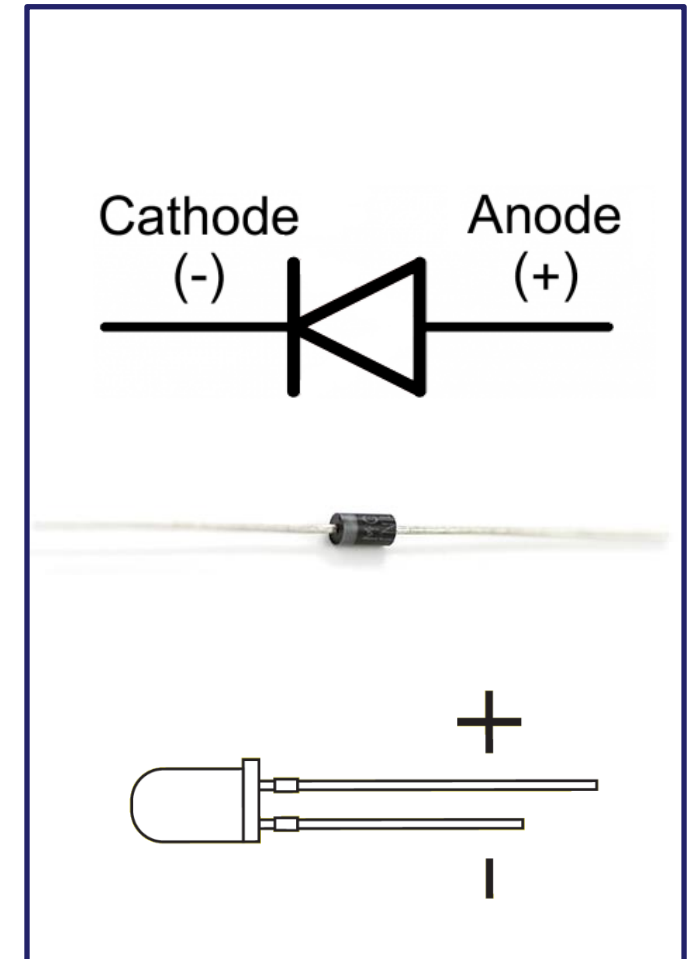


Working principle – Supplementary Note

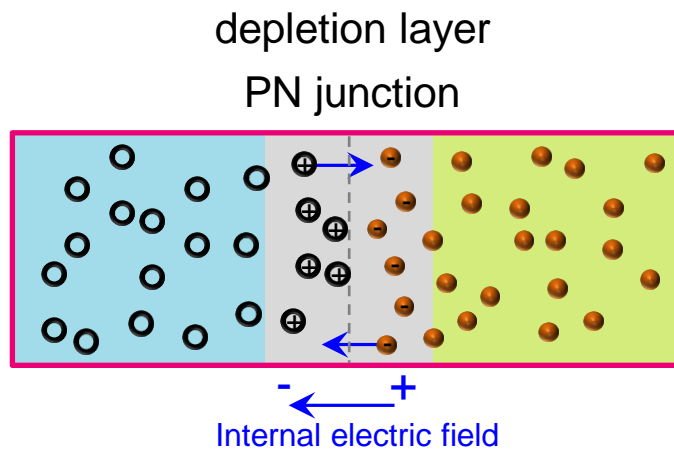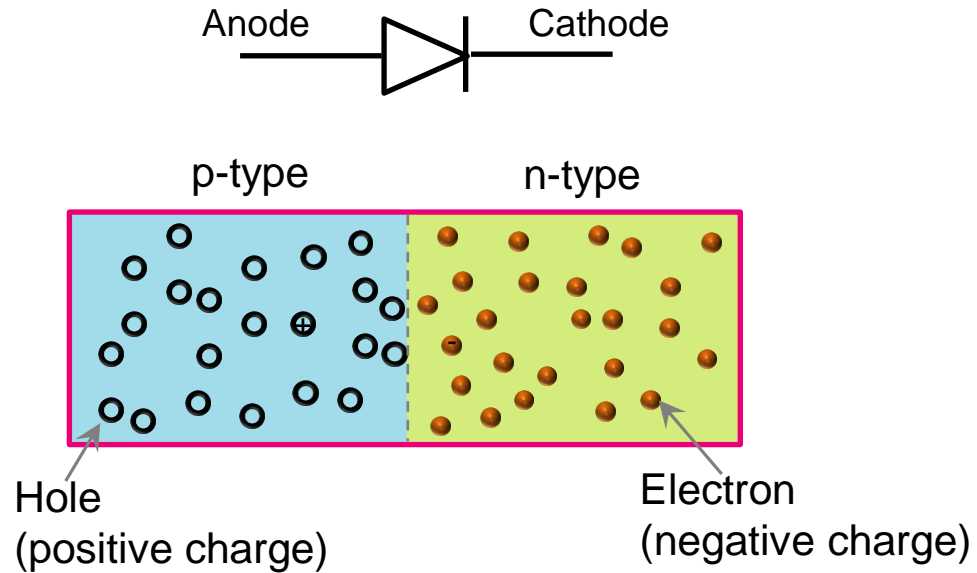



Case 1: forward bias (conductive)

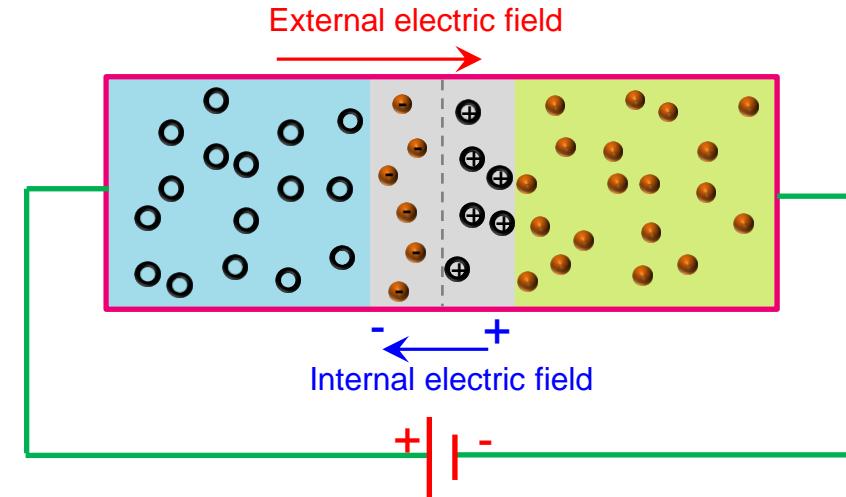

Case 2: reverse bias (cut-off)

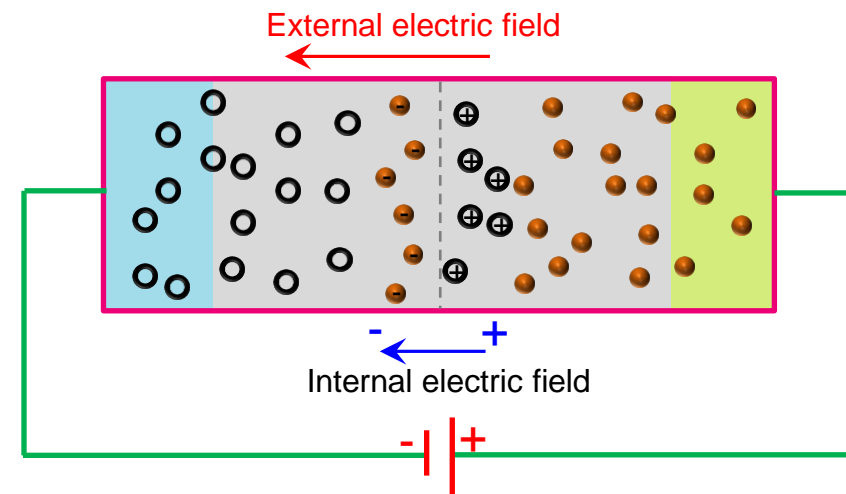

L16Q1: Based on the exponential equation for IV, can the diode supply power?

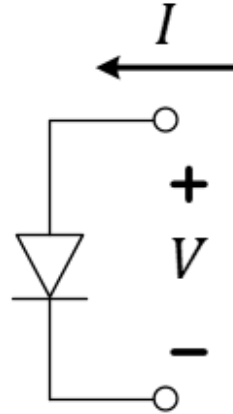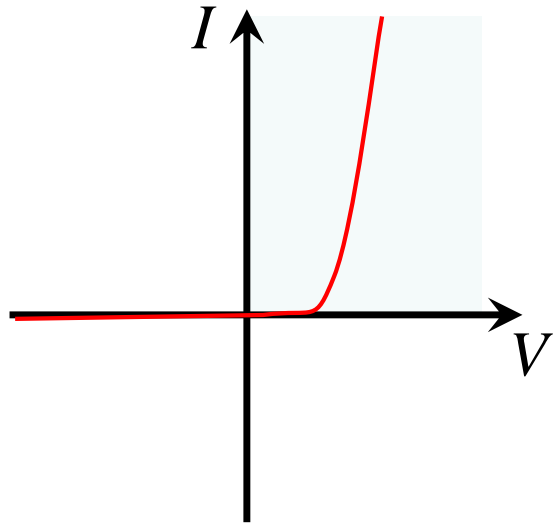


Case 1: **forward bias** ($V > 0$)

$$e^{V/nV_{therm}} > 1$$

$$I \approx I_S (e^{V/nV_{therm}} - 1) > 0$$

$$\underline{P = IV > 0}$$

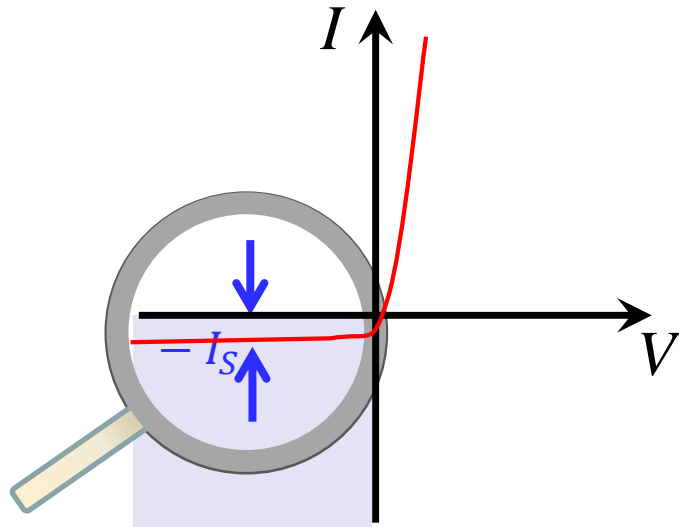

Case 2: **reverse bias** ($V < 0$)

$$e^{V/nV_{therm}} < 1$$


$$I \approx I_S (e^{V/nV_{therm}} - 1) < 0$$

$$I \approx -I_S \text{ (for large enough } |V| \text{)}$$

$$\underline{P = IV > 0}$$

No, the curve exists only in two quadrants where the “signed” P is > 0 .

Connecting diode to a linear circuit

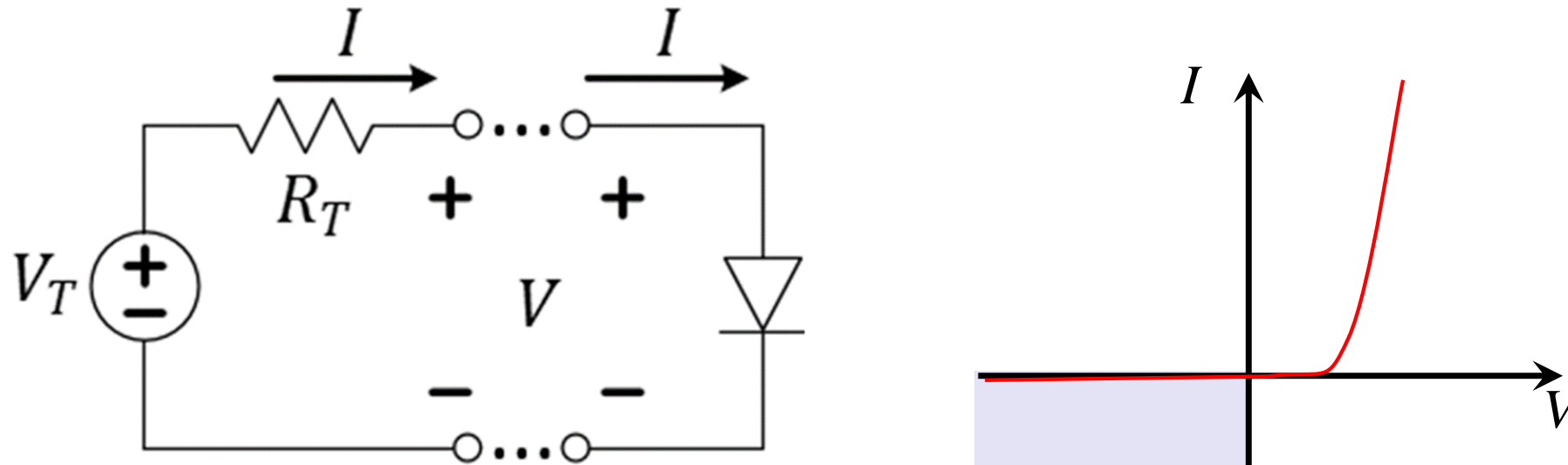

We can solve graphically for an operating point.
For an LED more current means more light.

Working at reverse bias



L16Q2: What is the current flowing through the diode if $V_T < 0$?

small and negative...nearly 0

Instead of looking for graphical solutions, we can approximate the diode with two linear segments, corresponding to diode's regimes of operation.




Case 1: forward bias ($V > V_{ON}$)

$$I > 0$$

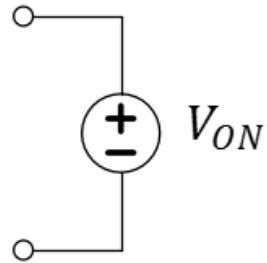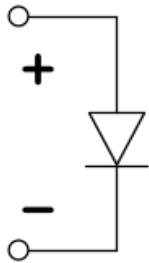


Case 2: reverse bias ($V < V_{ON}$)

$$I = 0$$

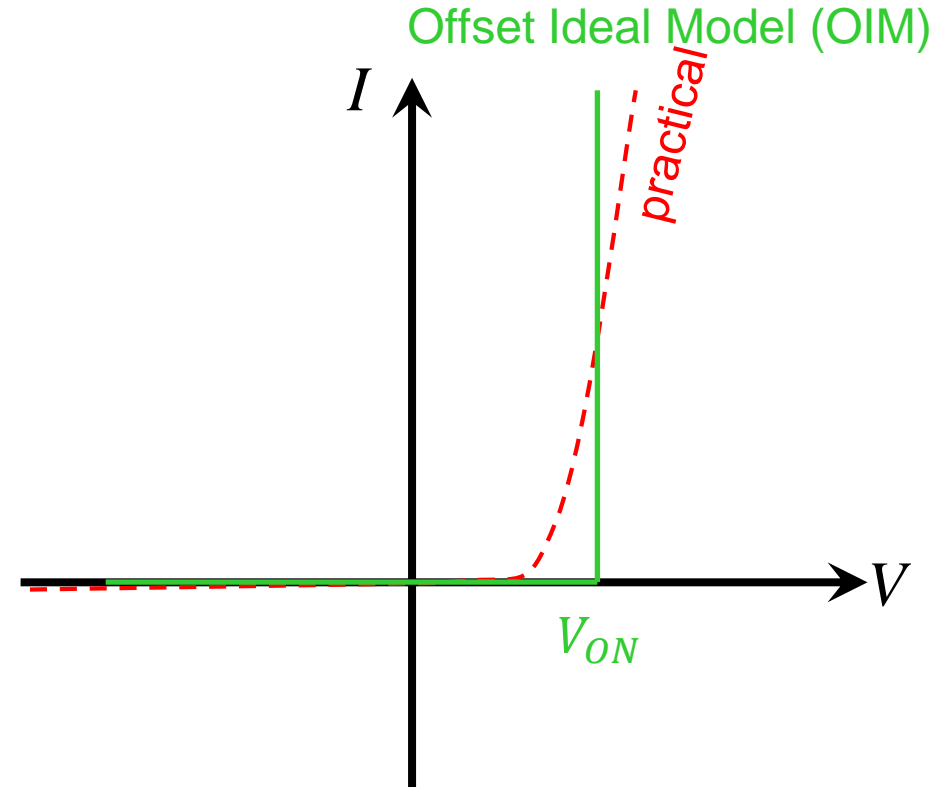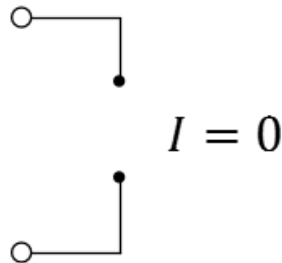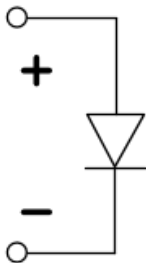


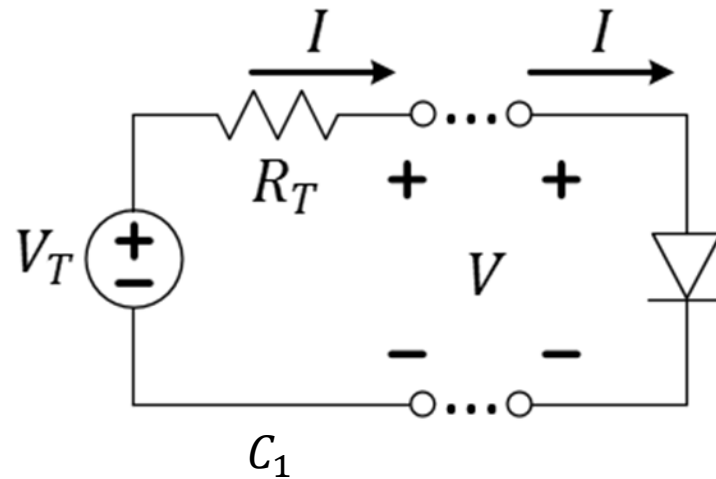L16Q3: What is the minimum V_T of the connected linear circuit which causes current to flow through the diode if the piecewise linear model above is used?



For the resistor R_T , the IV characteristic is,
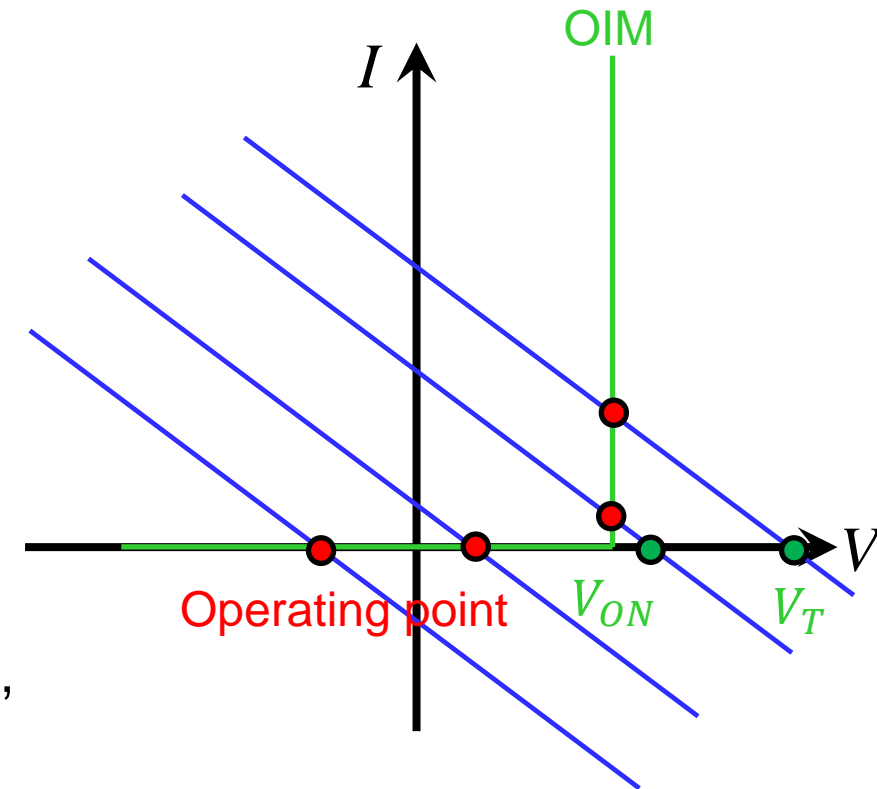
$$I = \frac{V_T - V}{R_T} = \frac{V_T}{R_T} - \frac{V}{R_T}$$



$$I > 0 \Rightarrow V_T > V_{on}$$

Different diode types have different V_{ON}


Diode Type	$V_{ON}(V)$	Applications
Silicon	0.6-0.7	General; integrated circuits; switching, circuit protection, logic, rectification, etc.
Germanium	~0.3	Low-power, RF signal detectors
Schottky	0.15-0.4	Power-sensitive, high-speed switching, RF
Red LED (GaAs)	~2	Indicators, signs, color-changing lighting
Blue LED (GaN)	~3	Lighting, flashlights, indicators
“Ideal”	0	Can neglect V_{ON} for high voltage applications

L16Q4: What is the power dissipated by a Ge diode if 30 mA is flowing through it?

Germanium:

$$V_{on} \sim 0.3V$$
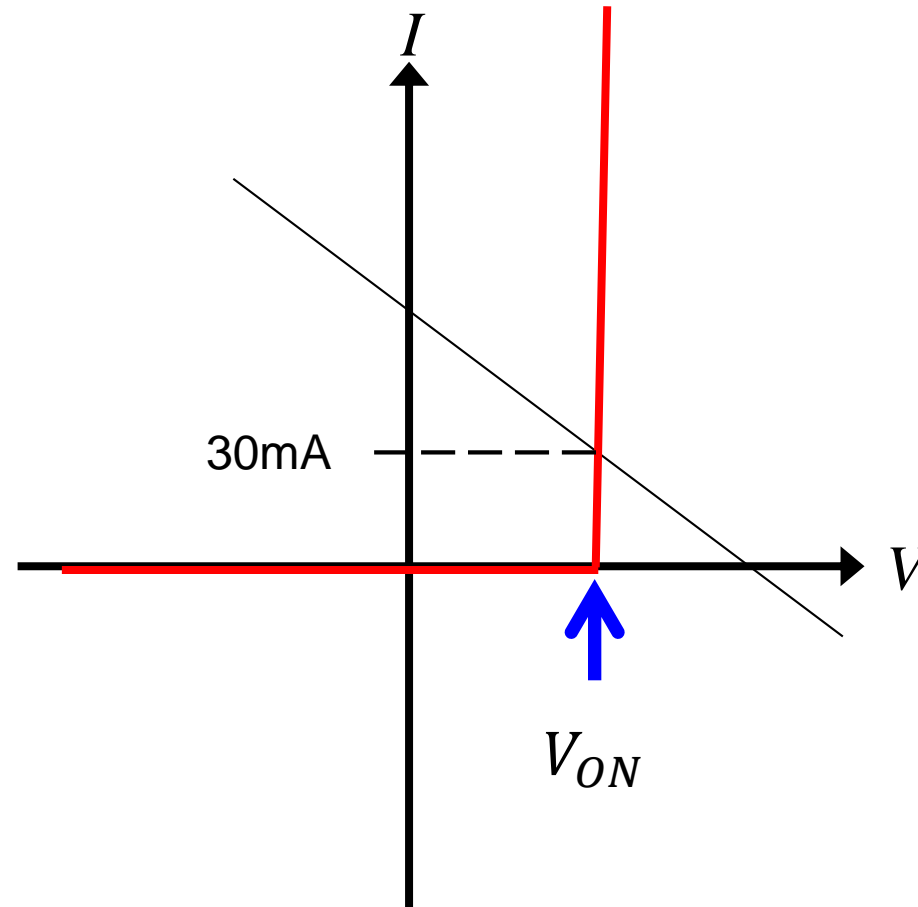
$$\begin{aligned} P &= V_{on} \times I \\ &= 0.3 \times 30mA \\ &= 9mW \end{aligned}$$



Q4:

A. 3 mW


B. 9 mW

C. 30 mW

D. 90 mW

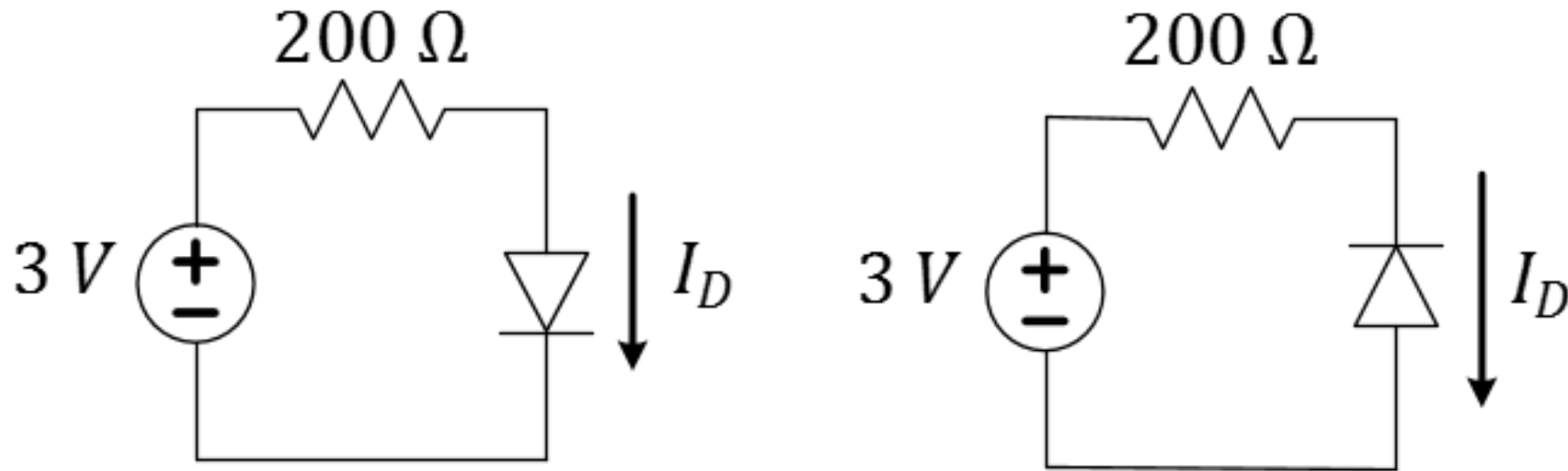E. 900 mW

Diode circuit examples (offset ideal model)




Assume offset-ideal model with $V_{ON} = 0.7$ (common Si diodes)

L16Q5: What is the current through the diode in the top left circuit?

L16Q6: What is the current through the diode in the top right circuit?


L16Q5: What is the current through the diode?

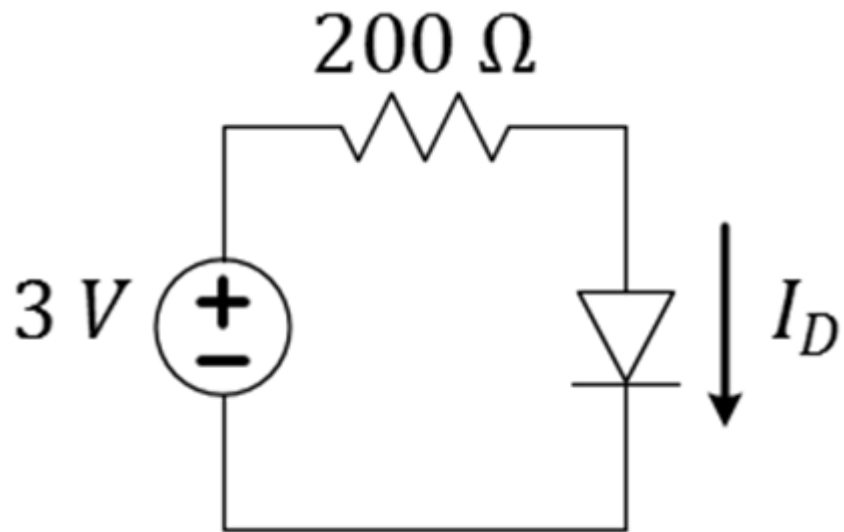Assume offset-ideal model with $V_{ON} = 0.7$ (common Si diodes)




FORWARD BIAS
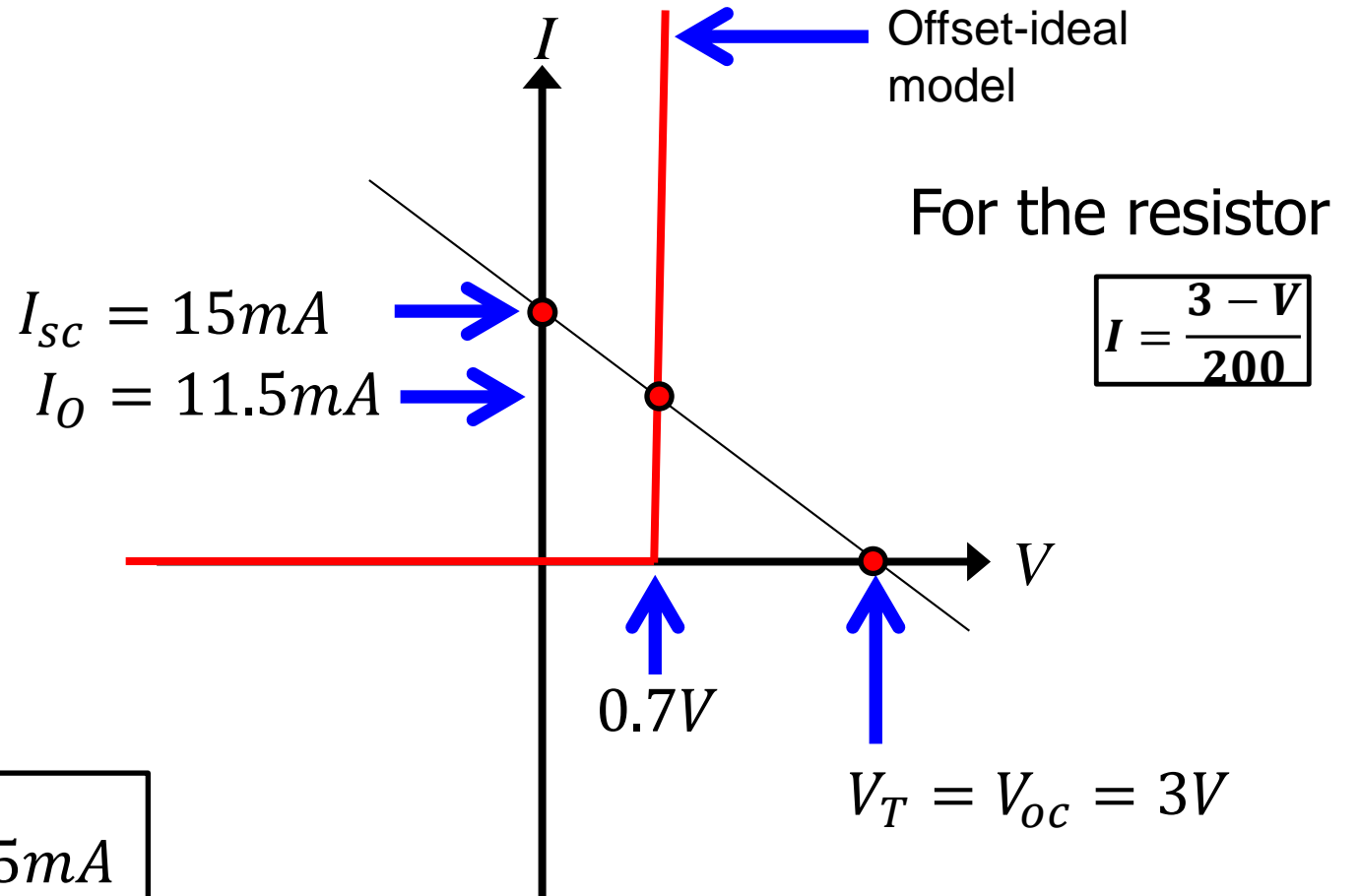
$$I_O = I_{sc} - \frac{V_{ON}}{R} = 0.015 - \frac{0.7}{200} = 11.5mA$$




L16Q6: What is the current through the diode?

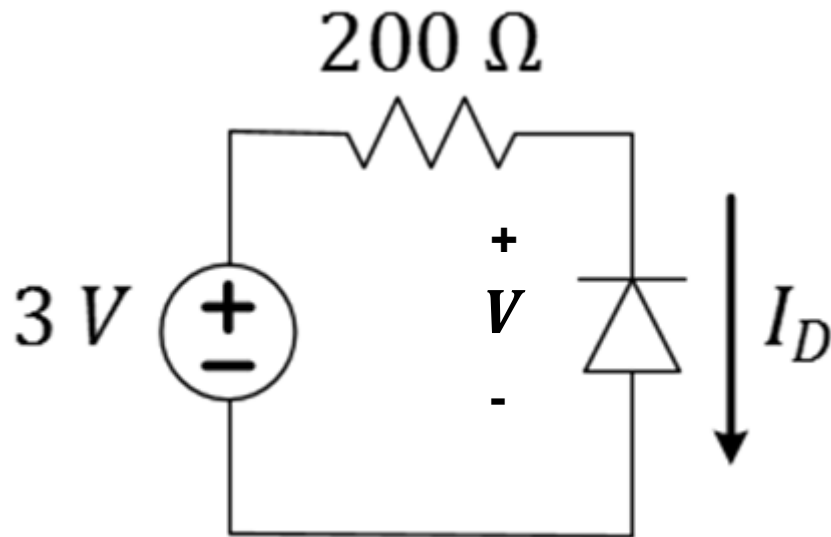Assume offset-ideal model with $V_{ON} = 0.7$ (common Si diodes)




REVERSE BIAS

$$I_D = \frac{3 - V}{200}$$

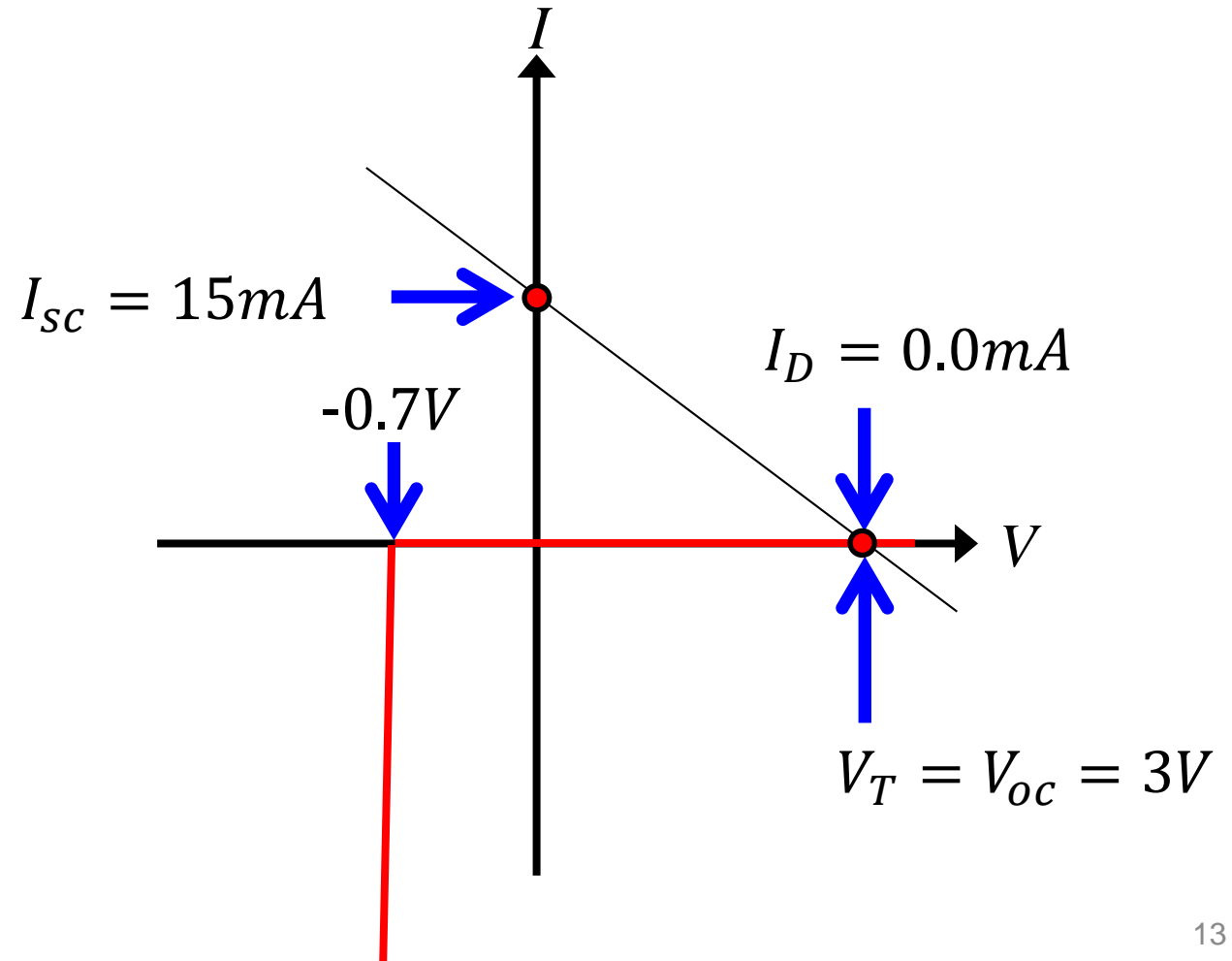


L16Q6: What is the current through the diode?

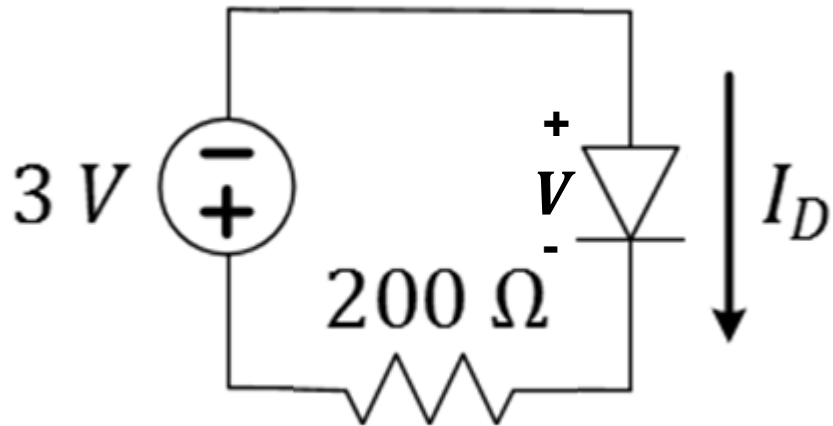Assume offset-ideal model with $V_{ON} = 0.7$ (common Si diodes)




REVERSE BIAS

$$I_D = \frac{-3 - V}{200}$$

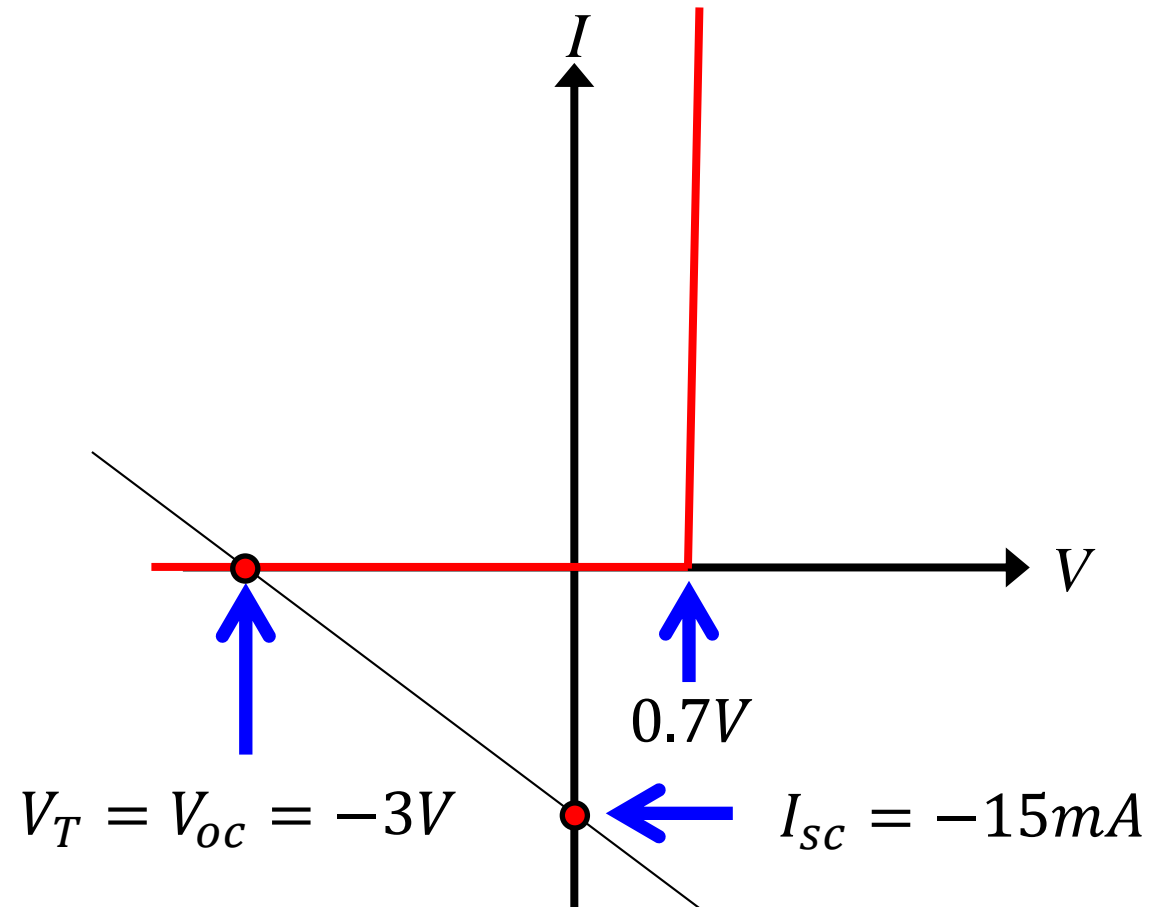

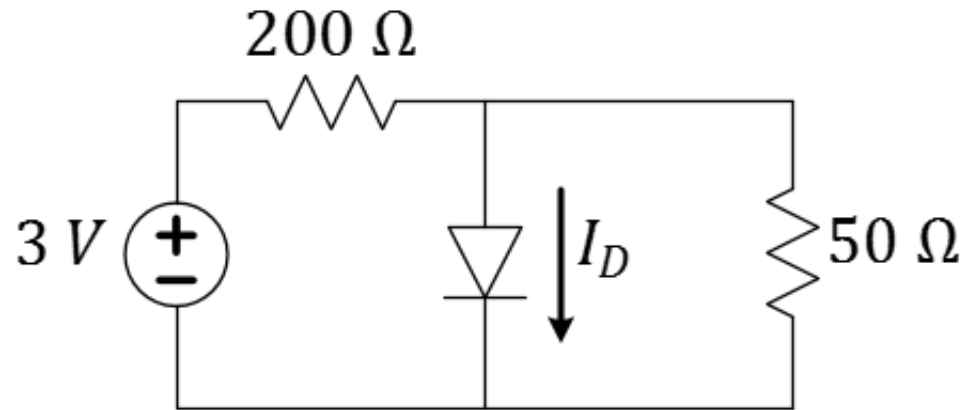Diode circuit examples (offset ideal model)



Assume offset-ideal model with $V_{ON} = 0.7V$ (common Si diodes)

L16Q7: What is the current through the diode in the circuit?

$I_D =$


A. -11.5 mA

B. -2.5 mA

C. 0 mA

D. $+2.5\text{ mA}$

E. $+11.5\text{ mA}$

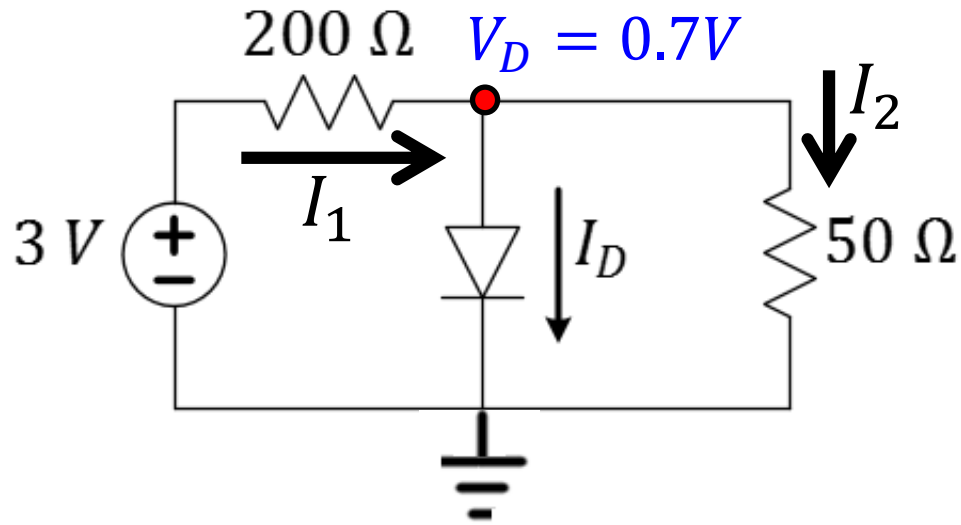L16Q7: What is the current through the diode in the circuit?

Assume offset-ideal model with $V_{ON} = 0.7V$

Assume diode is conducting:


$$I_1 = \frac{(3 - 0.7)}{200} = \frac{2.3}{200} = 11.5mA$$

$$I_2 = \frac{0.7}{50} = 14mA$$

From KCL

$$I_D = I_1 - I_2 = -2.5mA$$

NOT PHYSICAL → diode does not conduct

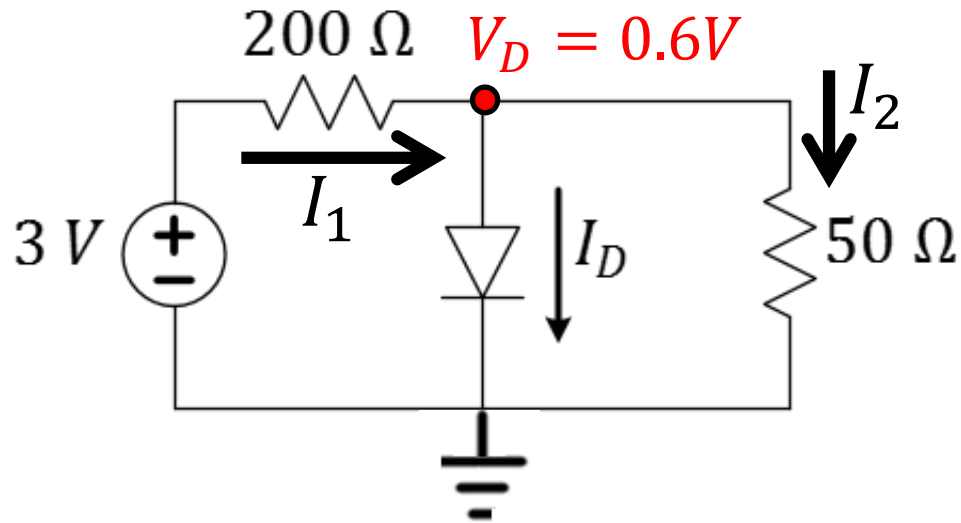L16Q7: What is the current through the diode in the circuit?

Assume offset-ideal model with $V_{ON} = 0.7V$

Assume diode is reverse biased:

$$I_D = 0A$$

$$I_1 = I_2 = \frac{3}{250} = 12mA$$

$$V_D = I_2 \times 50 = 0.6V$$

I-V operating point of the diode is (0A,0.6V)

$I_D =$

A. $-11.5 mA$


B. $-2.5 mA$

C. $0 mA$

D. $+2.5 mA$

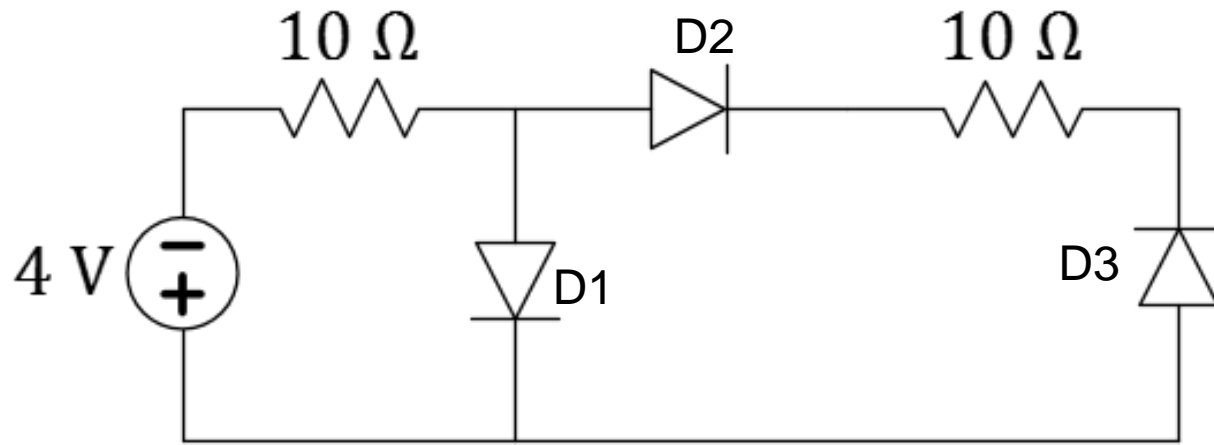E. $+11.5 mA$


Back-to-back diodes in series are modeled by OIM as an open circuit



L16Q8: Assume OIM with $V_{ON} = 0.7$ V (Si)
What is the current through the left-most diode?

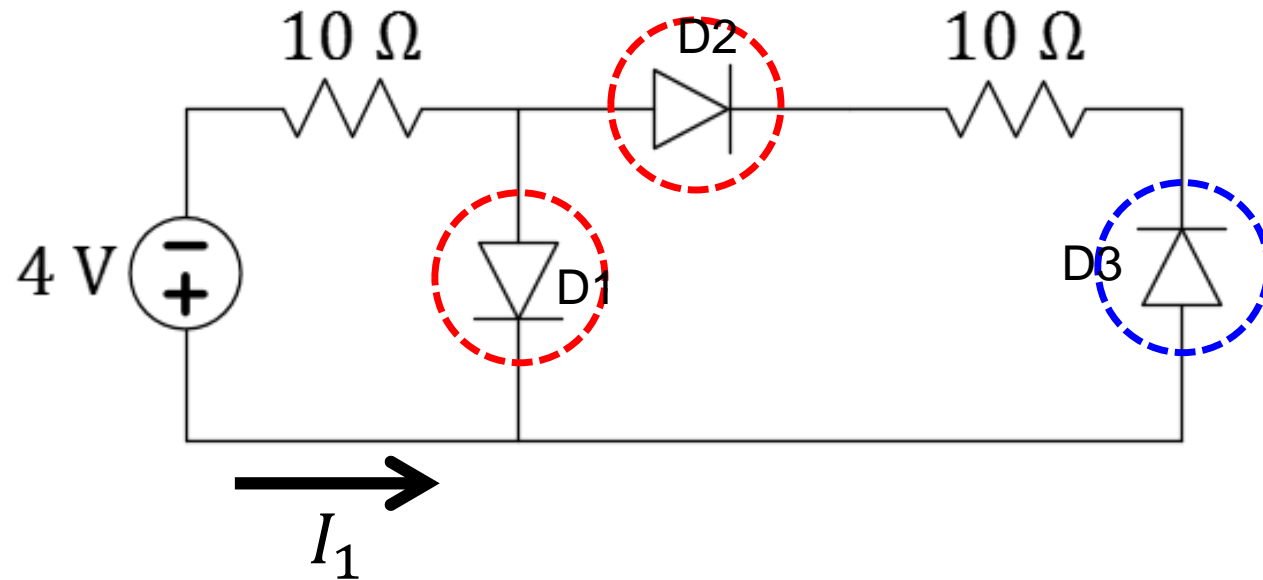- A. 0 Amps*
- B. 0.2 Amps*
- C. 0.33 Amps*
- D. 0.4 Amps*
- E. 3.3 Amps*

**L16Q8: Assume OIM with $V_{ON} = 0.7 \text{ V}$ (Si)
What is the current through the left-most diode?**




- A. 0 Amps*
- B. 0.2 Amps*
- C. 0.33 Amps*
- D. 0.4 Amps*
- E. 3.3 Amps*

☐ FORWARD BIAS

☐ REVERSE BIAS

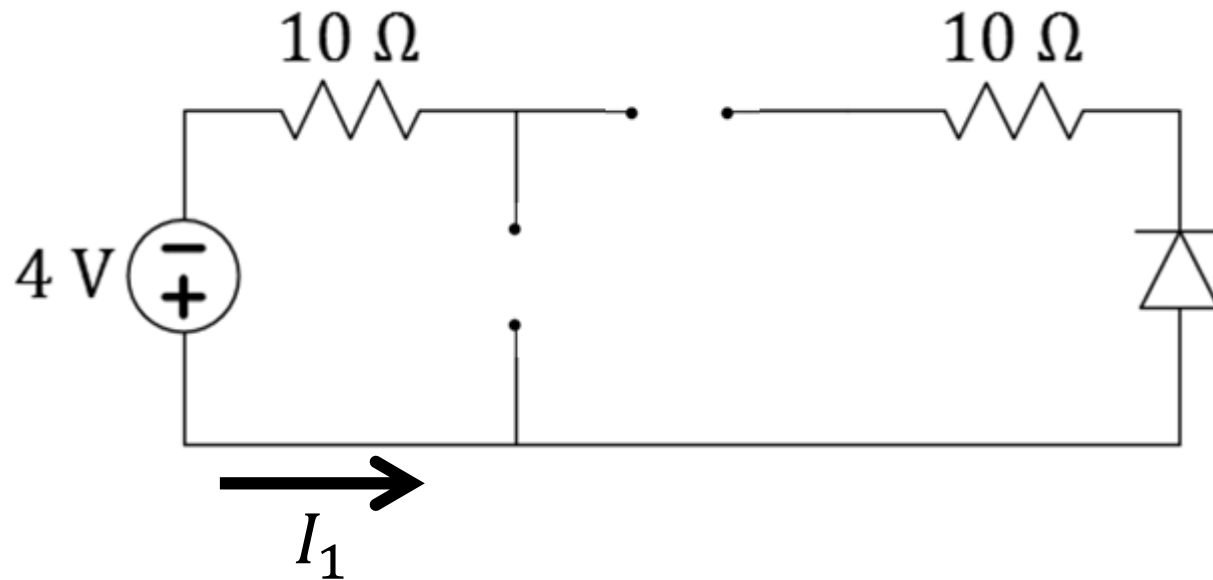**L13Q8: Assume OIM with $V_{ON} = 0.7 \text{ V}$ (Si)
What is the current through the left-most diode?**



- A. 0 Amps**
- B. 0.2 Amps
- C. 0.33 Amps
- D. 0.4 Amps
- E. 3.3 Amps



L16 Learning Objectives

- a. Draw a “typical” diode IV curve and describe its shape
- b. Explain how to use graphical analysis to find the operating point of a diode connected to a linear circuit
- c. Describe the offset ideal diode model (open, V-source)
- d. Solve simple circuit problems with one diode, given V_{ON}