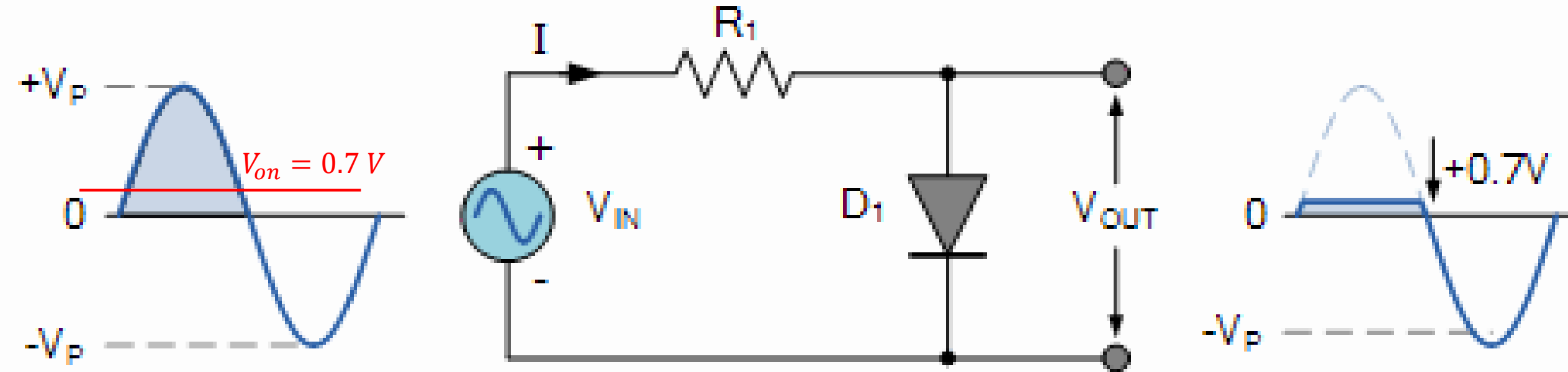


EXPLORE MORE

DIODE CLIPPING CIRCUITS for Alternating Voltage

Assume:
Silicon diodes with $V_{ON} = 0.7V$


Positive Diode Clipping Circuit



Case 1: when V_{in} is larger than V_{on} , the diode is turned on, $V_{out} = 0.7\text{ V}$

Case 2: when V_{in} is smaller than V_{on} , the diode is turned off, $V_{out} = V_{in}$


Negative Diode Clipping Circuit

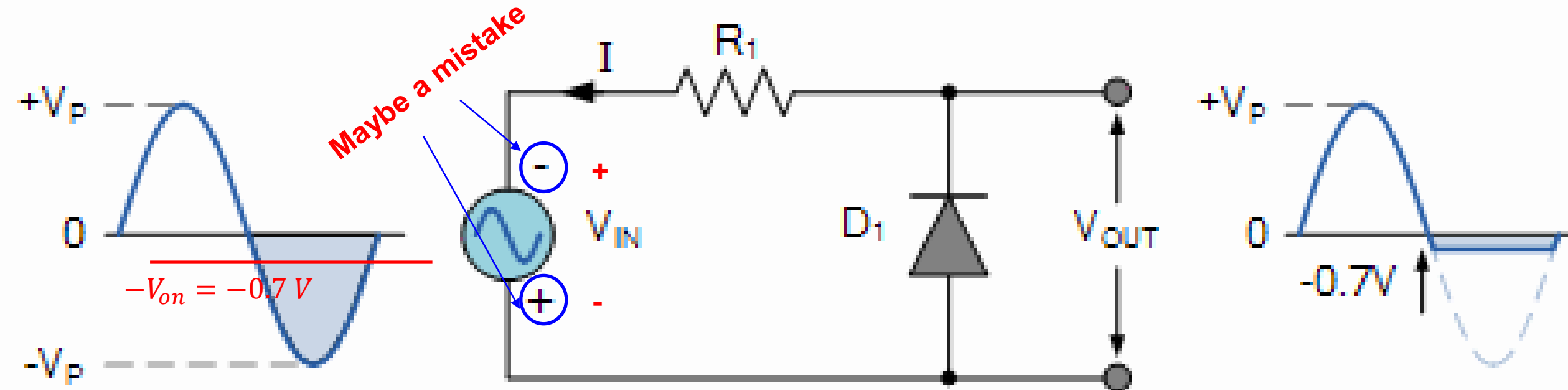

Case 1: when V_{in} is larger than $-V_{on}$, the diode is turned off, $V_{out} = V_{in}$

Case 2: when V_{in} is smaller than $-V_{on}$, the diode is turned on, $V_{out} = -0.7\text{ V}$

Clipping Both Half Cycles

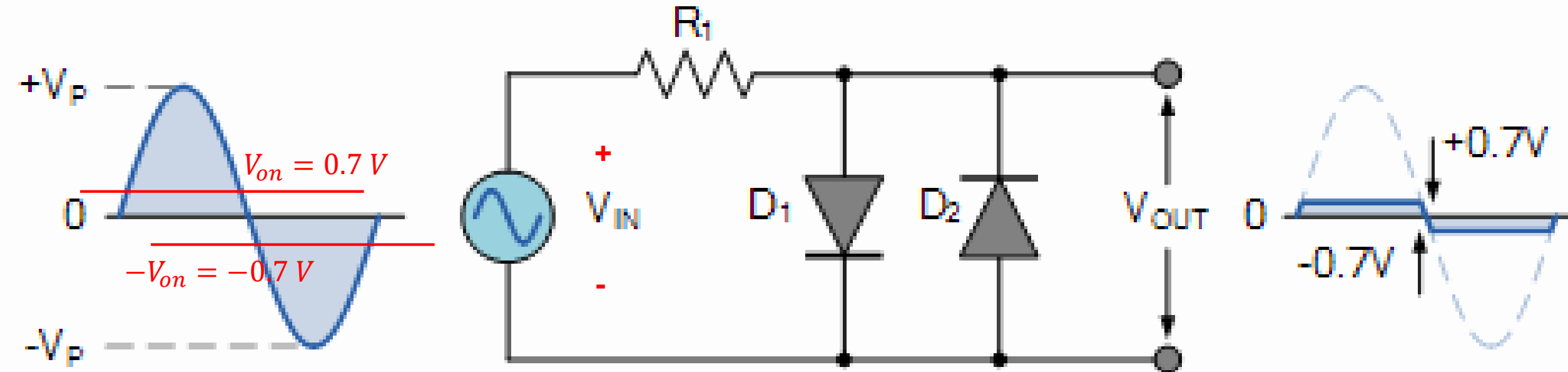


Case 1: when V_{in} is larger than V_{on} , diode D_1 is turned on, $V_{out} = 0.7\text{ V}$

Case 2: when V_{in} is smaller than $-V_{on}$, diode D_2 is turned on, $V_{out} = -0.7\text{ V}$

Case 3: when V_{in} is within $-V_{on}$ and V_{on} , both diodes are turned off, $V_{out} = V_{in}$


Positive Bias Diode Clipping

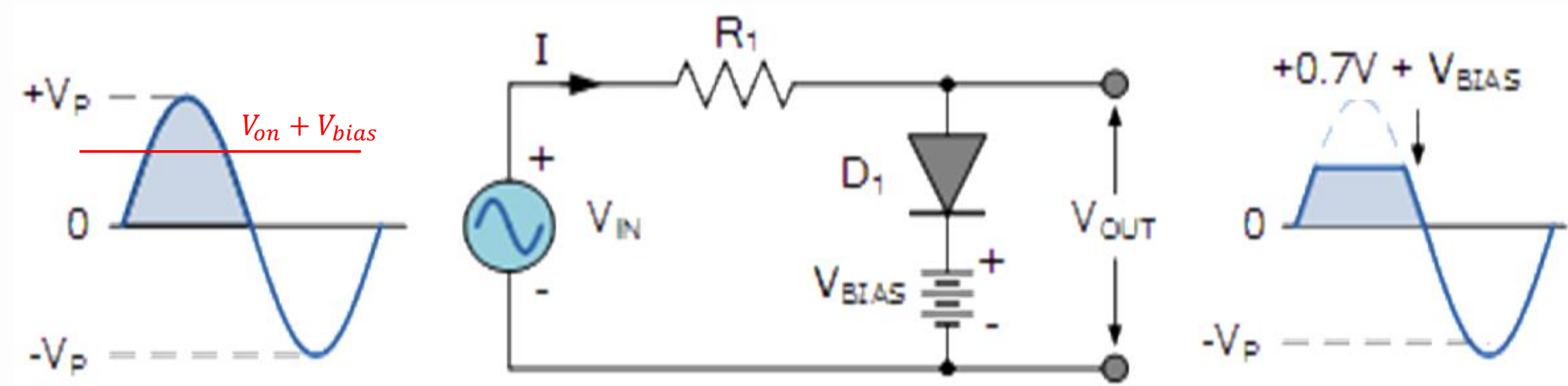

Case 1: When $V_{in} > V_{on} + V_{bias}$, the diode is on, so $V_{out} = V_{on} + V_{bias}$

Case 2: Otherwise, $V_{out} = V_{in}$


Negative Bias Diode Clipping

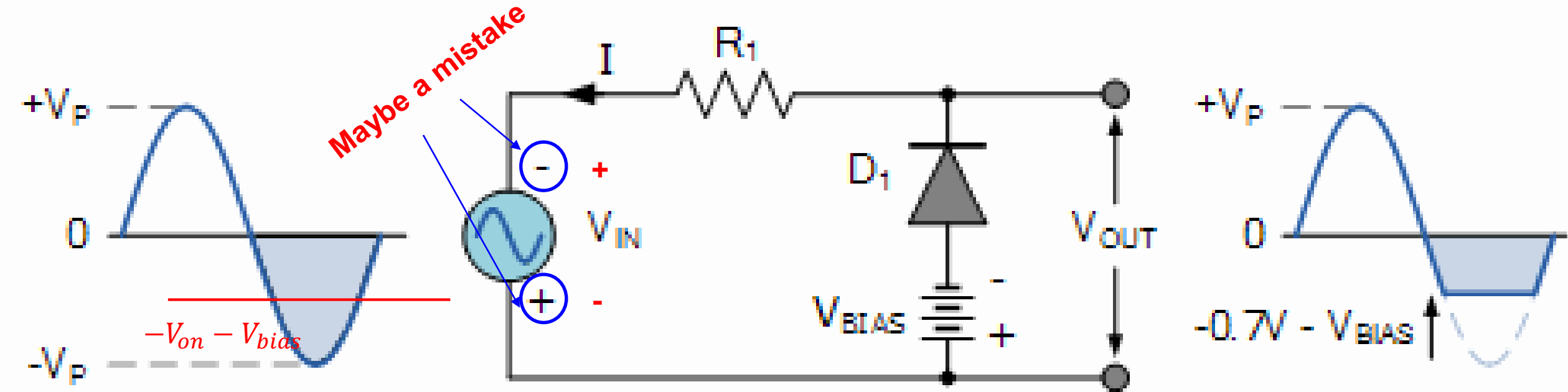

Case 1: When $V_{in} < -V_{on} - V_{bias}$, the diode is on, so $V_{out} = -V_{on} - V_{bias}$

Case 2: Otherwise, $V_{out} = V_{in}$

Diode Clipping – Different Bias Level

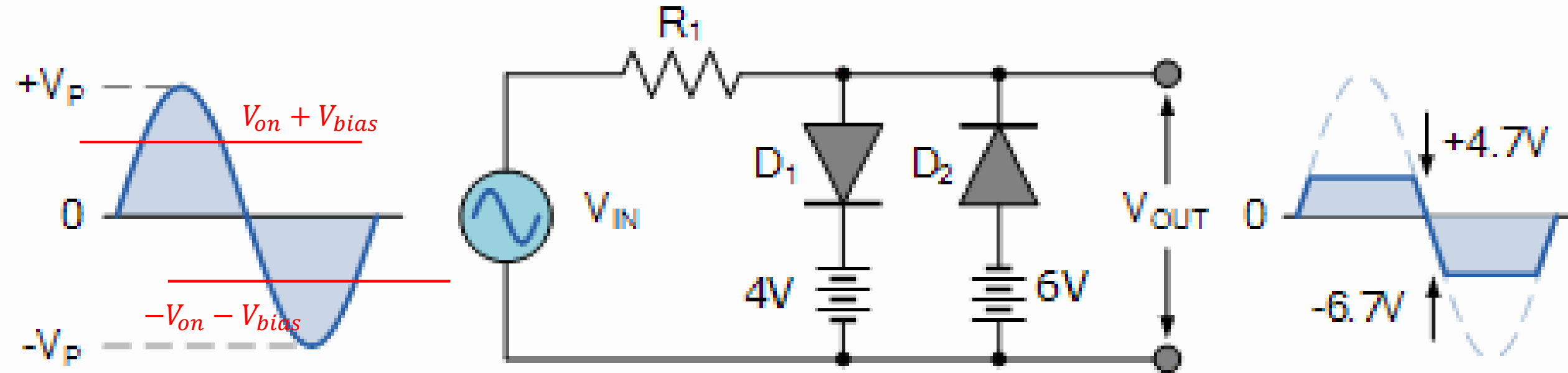


Case 1: When $V_{in} > V_{on} + 4$, diode D_1 is on, so $V_{out} = V_{on} + 4$

Case 2: When $V_{in} < -V_{on} - 6$, diode D_2 is on, so $V_{out} = -V_{on} - 6$

Case 3: Otherwise, $V_{out} = V_{in}$

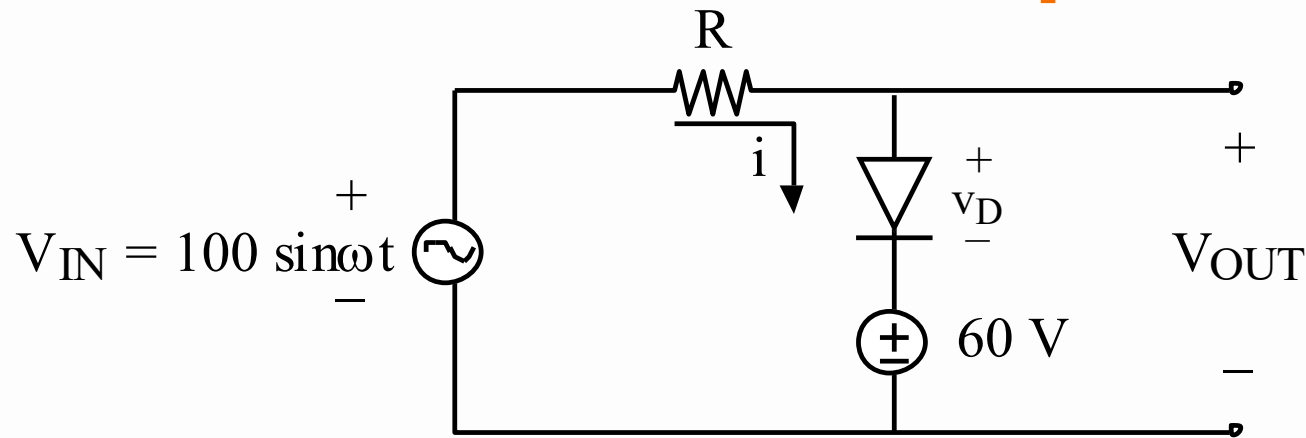
A voltage-clipping circuit sets maximum or minimum output voltage



Kirchhoff voltage law


KVL:

$$V_{OUT} = 60 + v_D$$

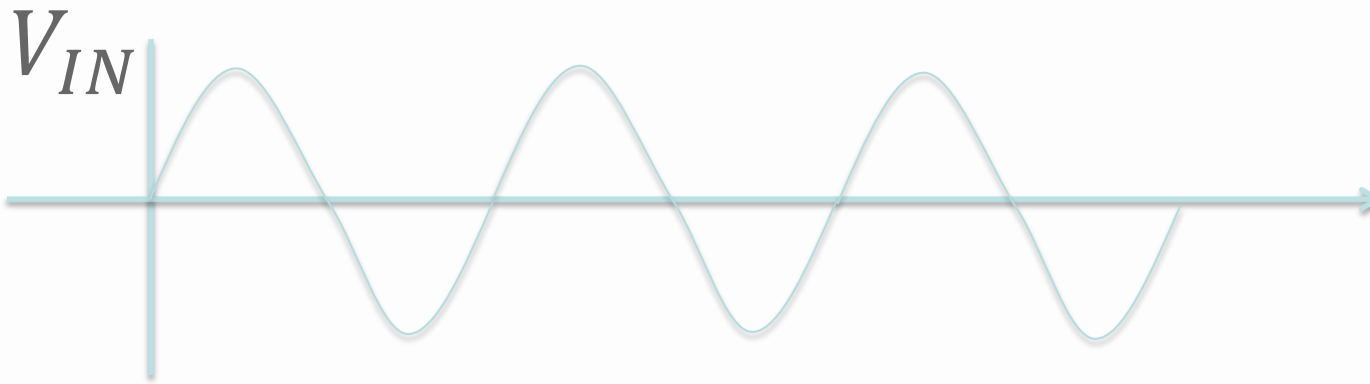


L18Q9: If the input voltage waveform is shown, what is the output waveform, assuming an ideal diode model ($V_{ON} = 0\text{ V}$)?

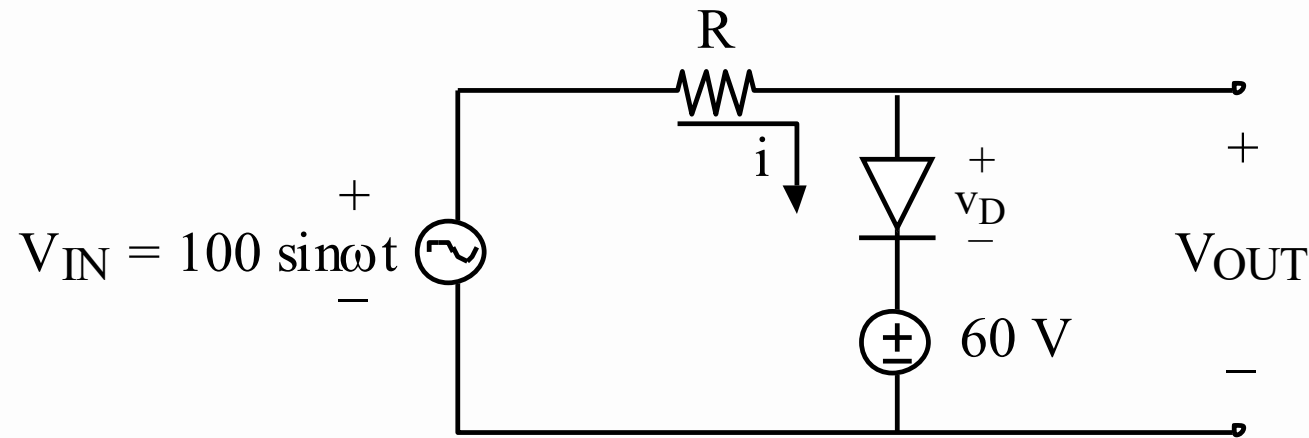L18Q9: If the input voltage waveform is shown, what is the output waveform, assuming an ideal diode model ($V_{ON} = 0$ V)?



KVL:


$$V_{OUT} = 60 + v_D$$

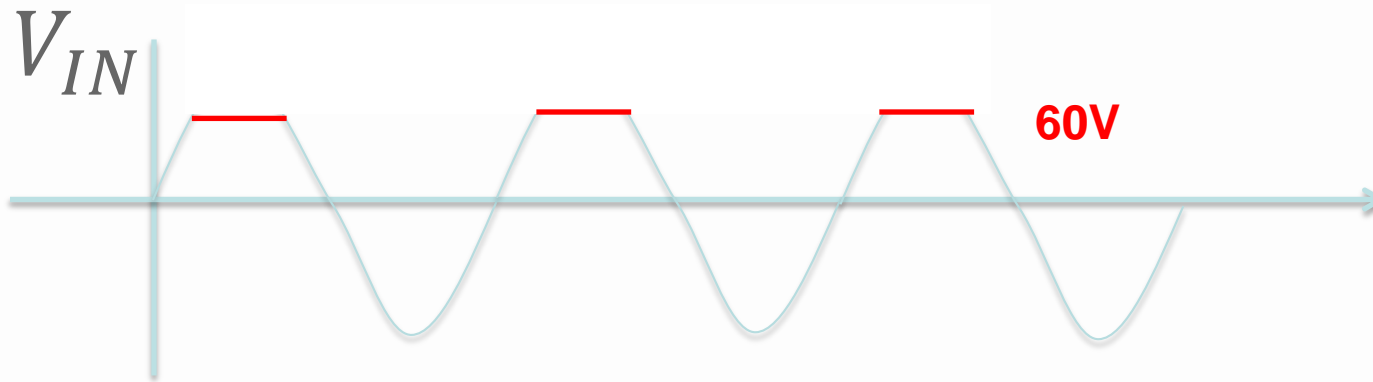

EXPLORE MORE

Voltage Rectification with diode circuits


Half-Wave Rectifier Circuit

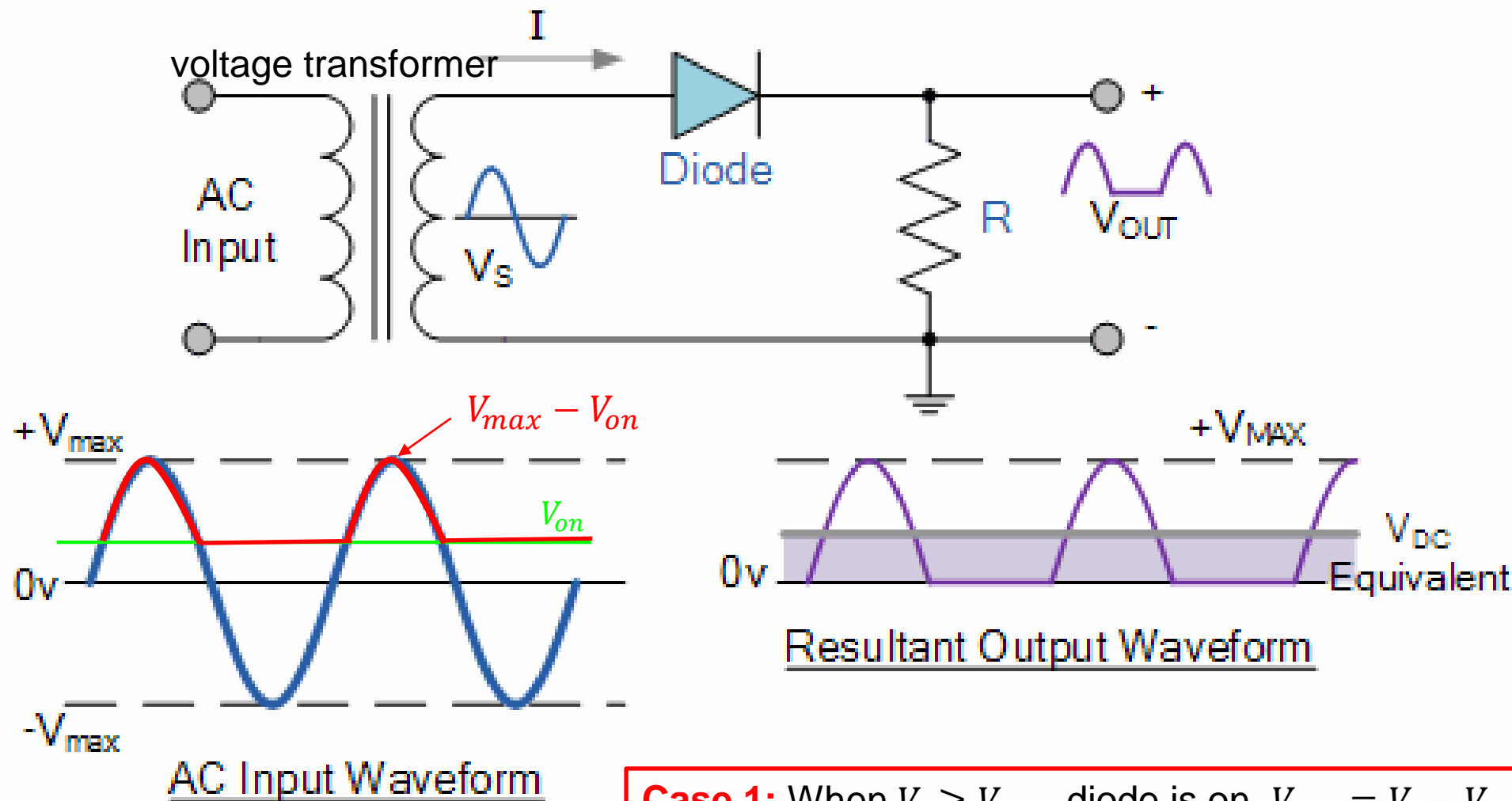

Case 1: When $V_s \geq V_{on}$, diode is on, $V_{out} = V_s - V_{on}$




Case 2: When $V_s < V_{on}$, diode is off, $I = 0$, $V_{out} = I \times R = 0$

Half-Wave Rectifier-Smoothing Capacitor

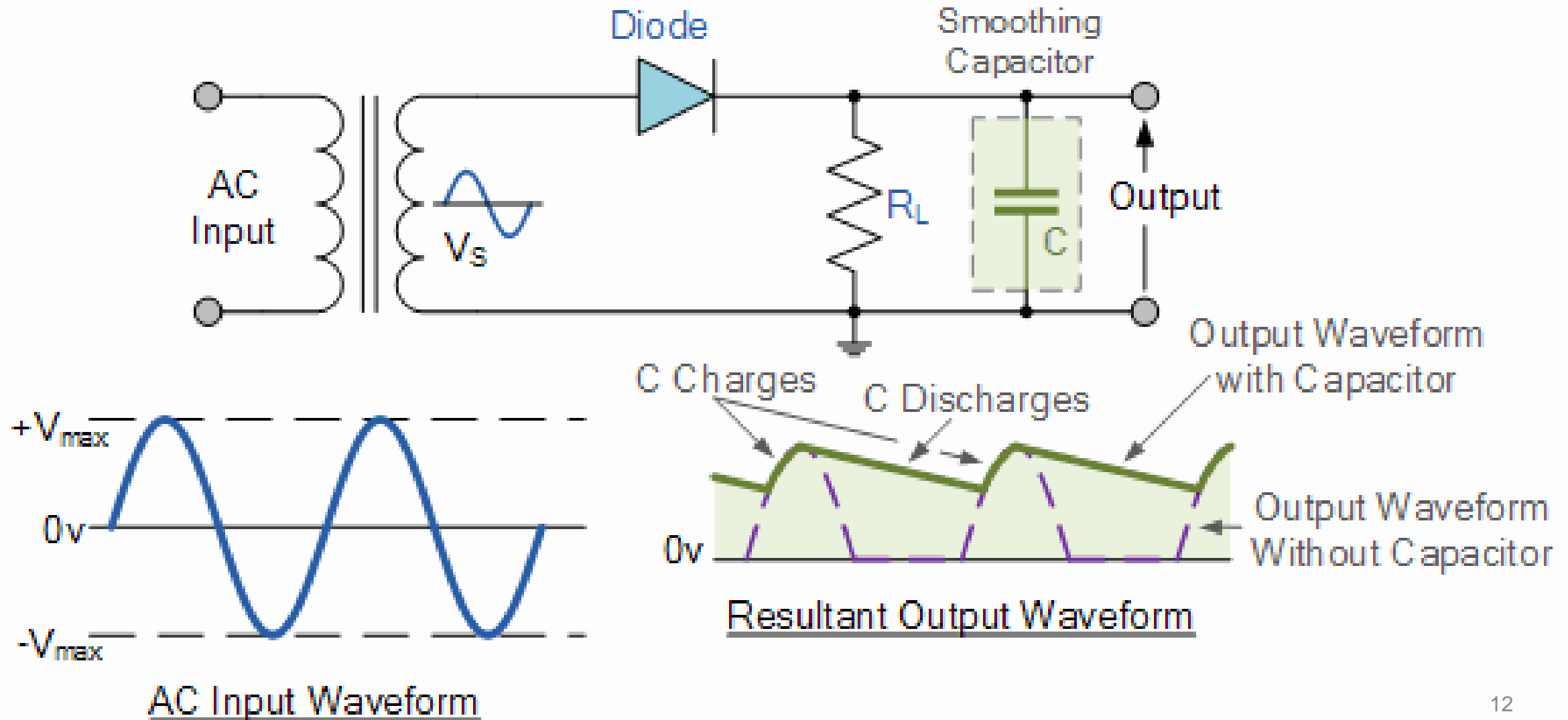

Supplementary Note for capacitor

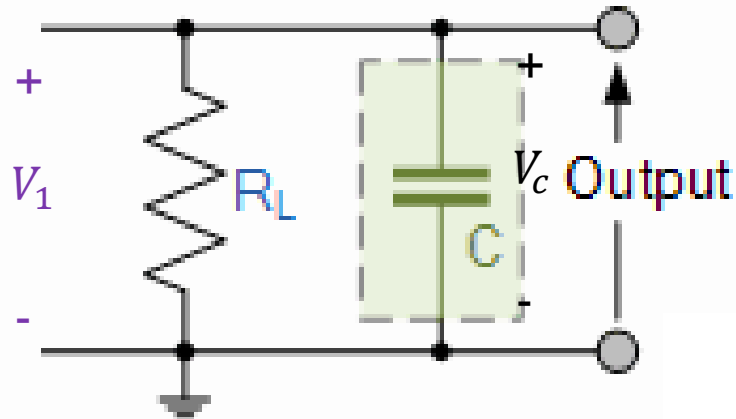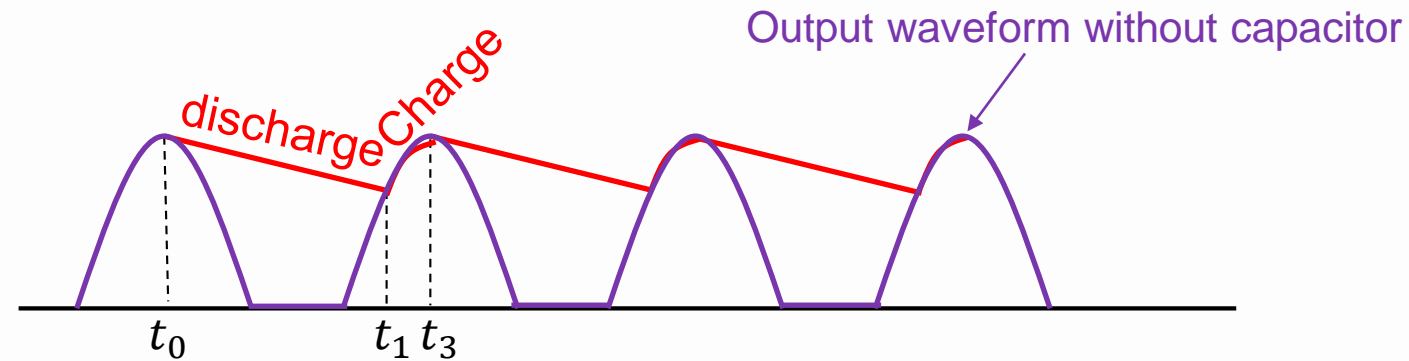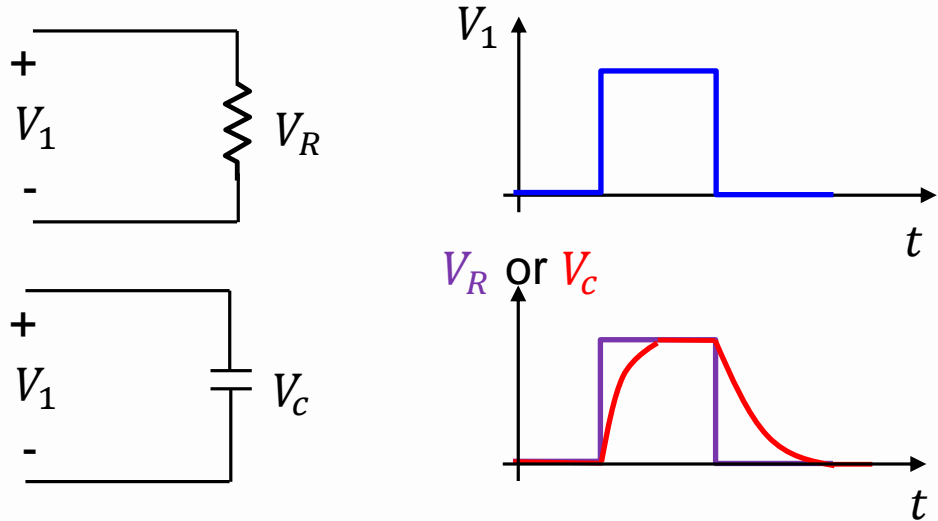
Capacitor is different from resistor. Modifying the well-established state needs some time delay



1. At $t = t_0$, $V_1 = V_c$, the circuit reaches a balance
2. After $t = t_0$, $V_1 < V_c$, so the capacitor discharges, This discharge **needs some time delay**.
3. At $t = t_1$, $V_1 = V_c$, the circuit reaches a balance
4. After $t = t_1$, $V_1 > V_c$, so the capacitor charges (actually also needs time delay, here UIUC ignores)

Full-Wave Rectifier Circuit



Case 1: when $V_s \geq V_{on}$, D_1 is on, $V_{out} = V_s - V_{on}$

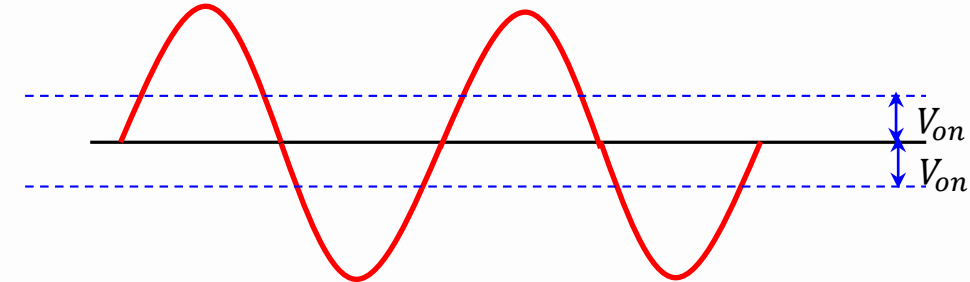


Case 2: when $V_s \leq -V_{on}$, D_2 is on, $V_{out} = |V_s| - V_{on}$

Case 3: otherwise, D_1 & D_2 are off, $V_{out} = 0$


Output voltage

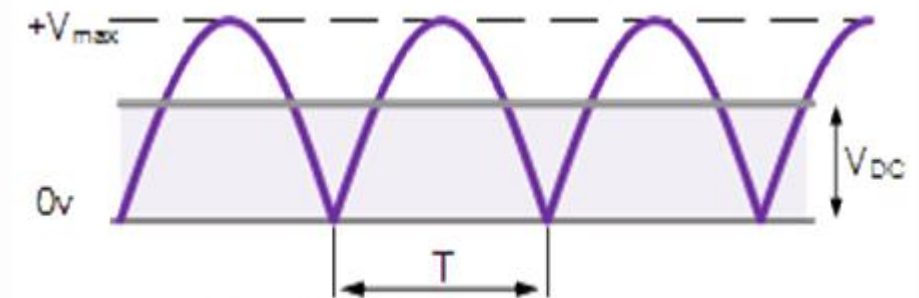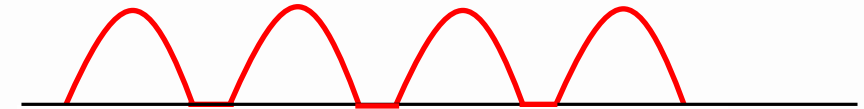


Resultant Output Waveform

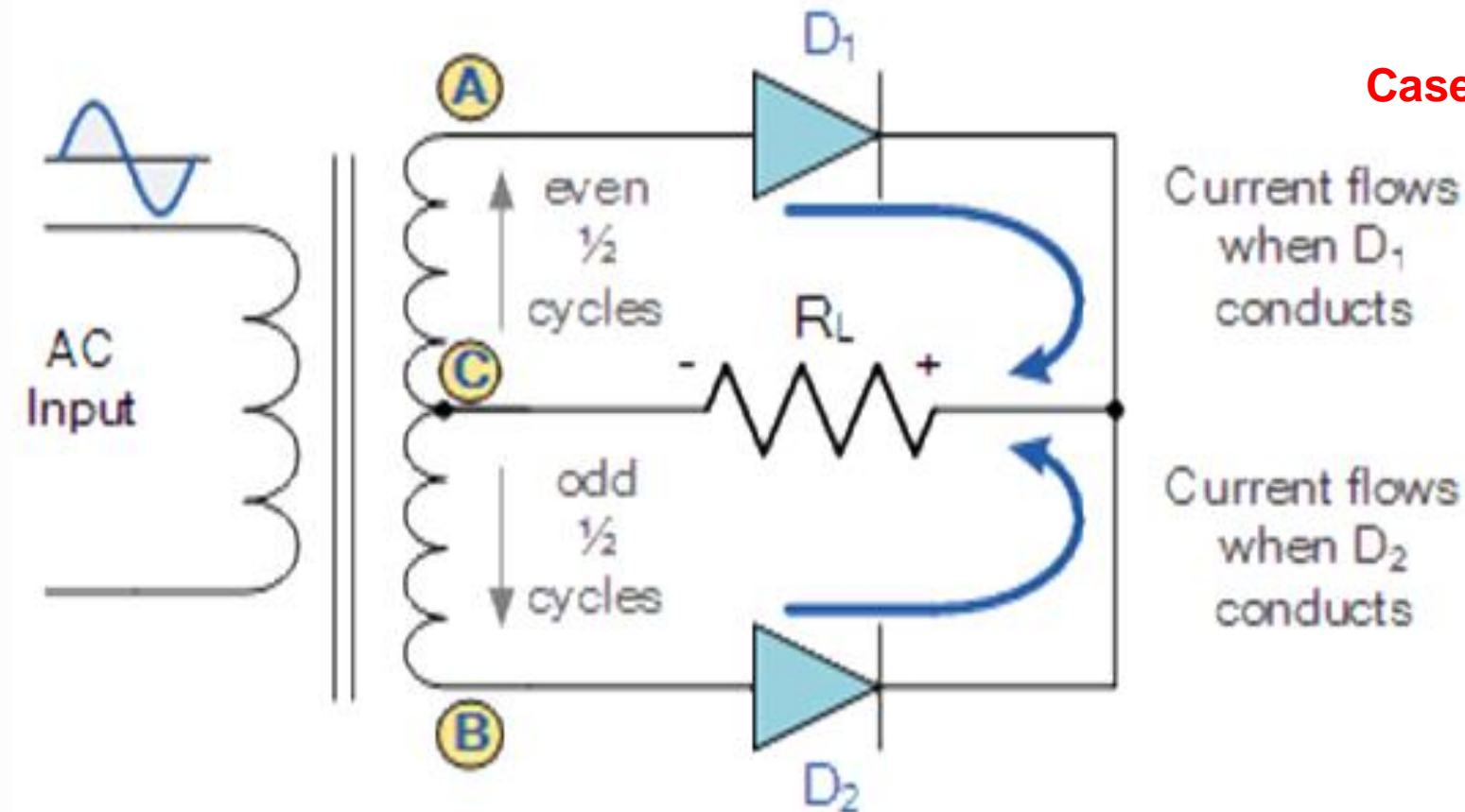

Full-Wave Diode Bridge Rectifier

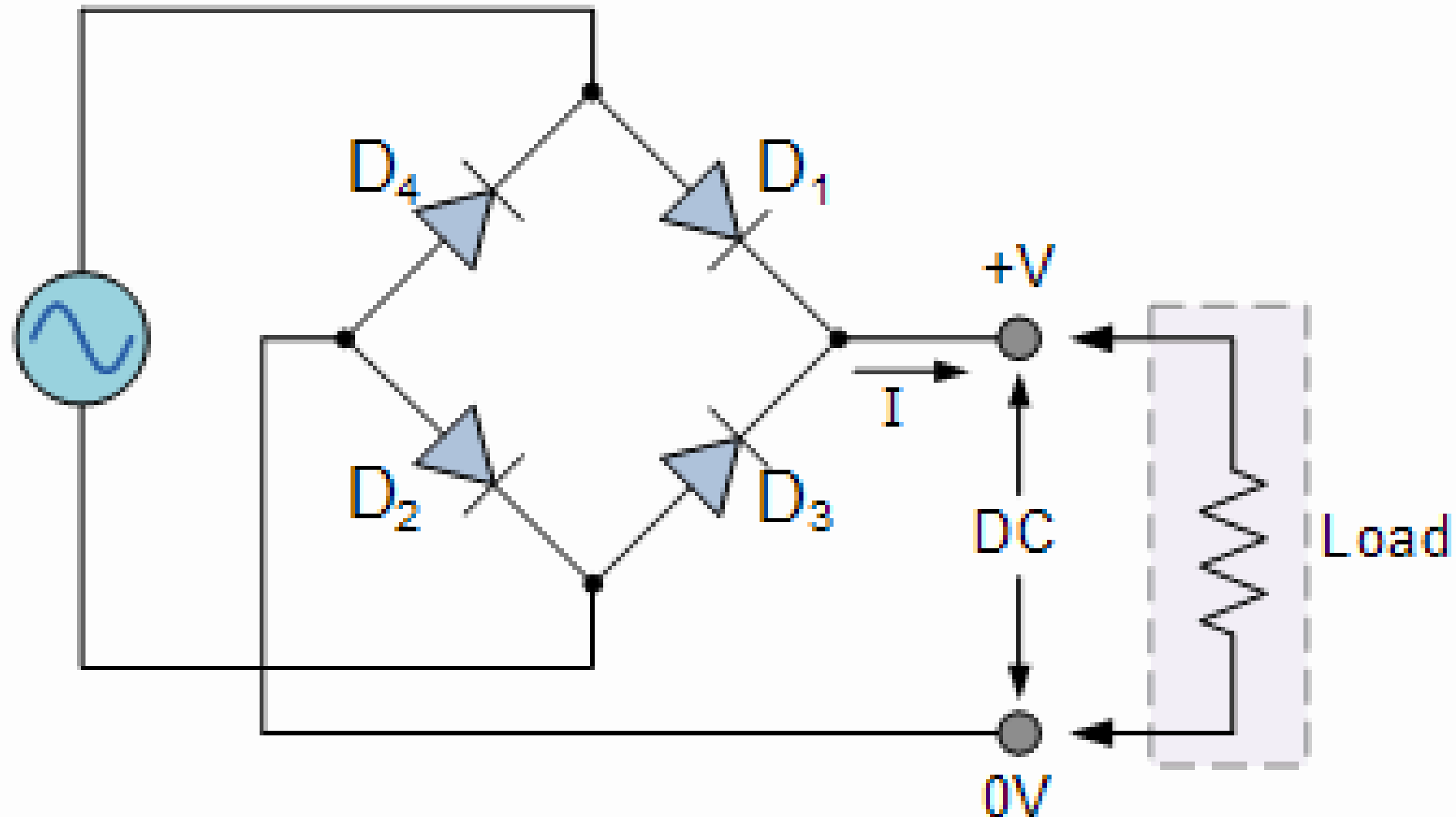


Diode Bridge – Positive Half-cycle

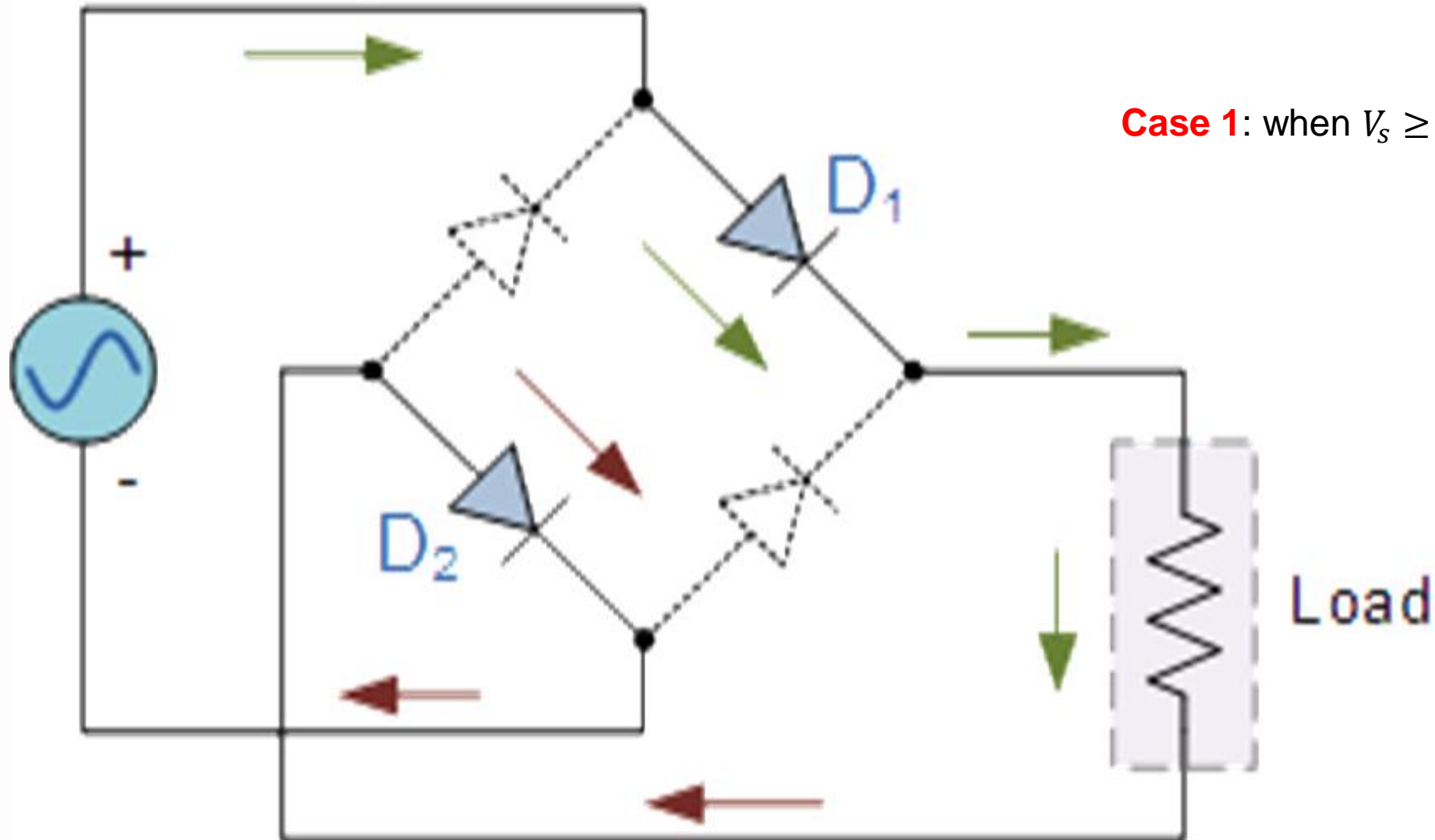


Case 1: when $V_s \geq 2 \times V_{on}$, $V_{out} = V_s - 2 \times V_{on}$

Diode Bridge – Negative Half-cycle

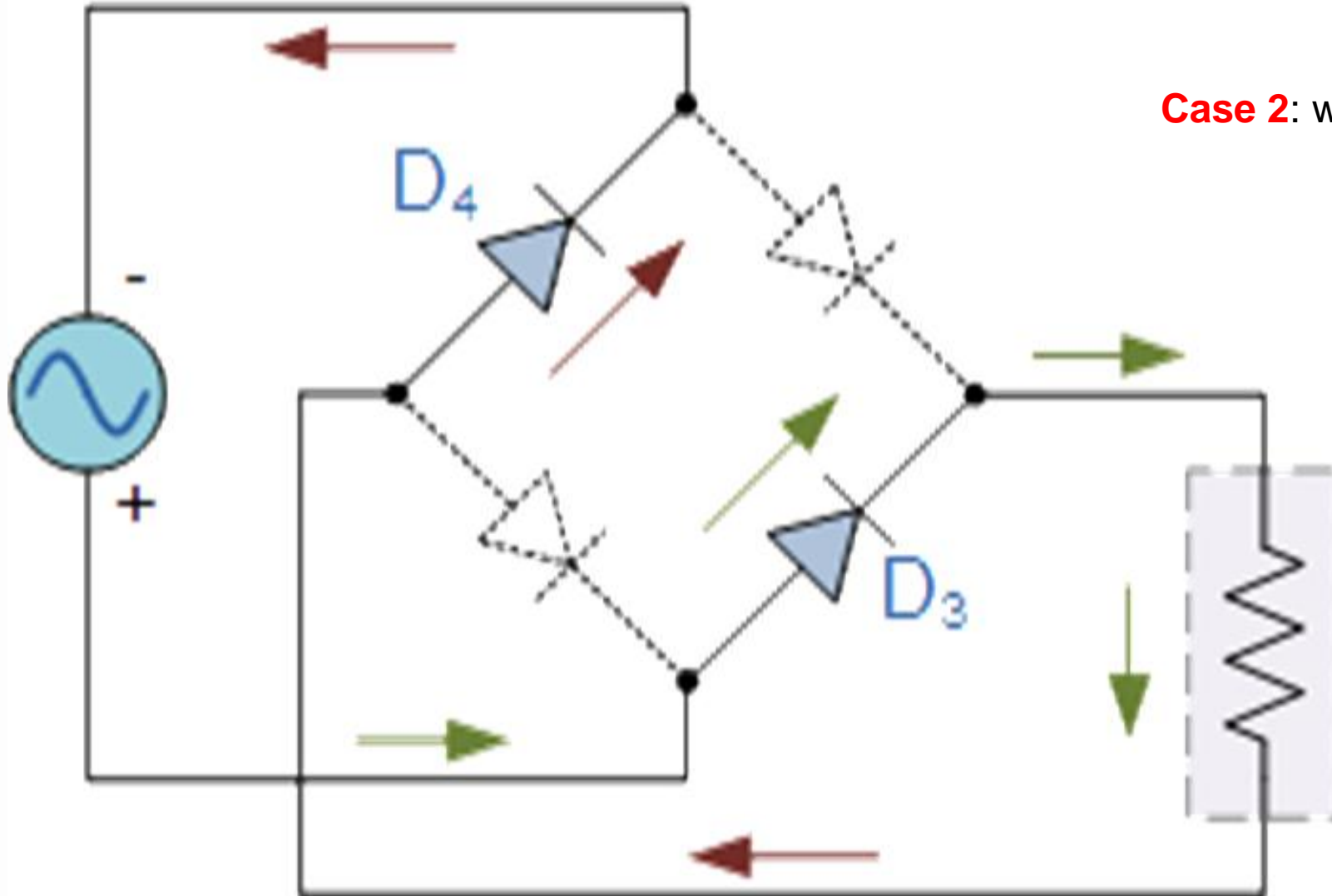


Case 2: when $V_s \leq -2 \times V_{on}$, $V_{out} = |V_s| - 2 \times V_{on}$

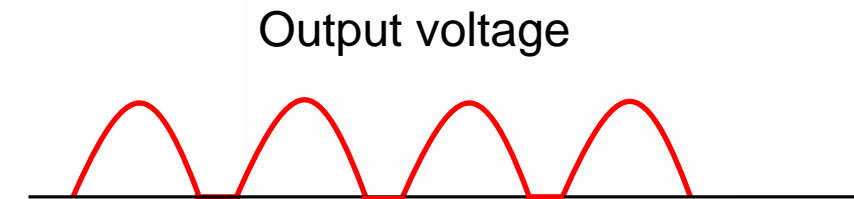


Load

Diode Bridge with Smoothing Capacitor

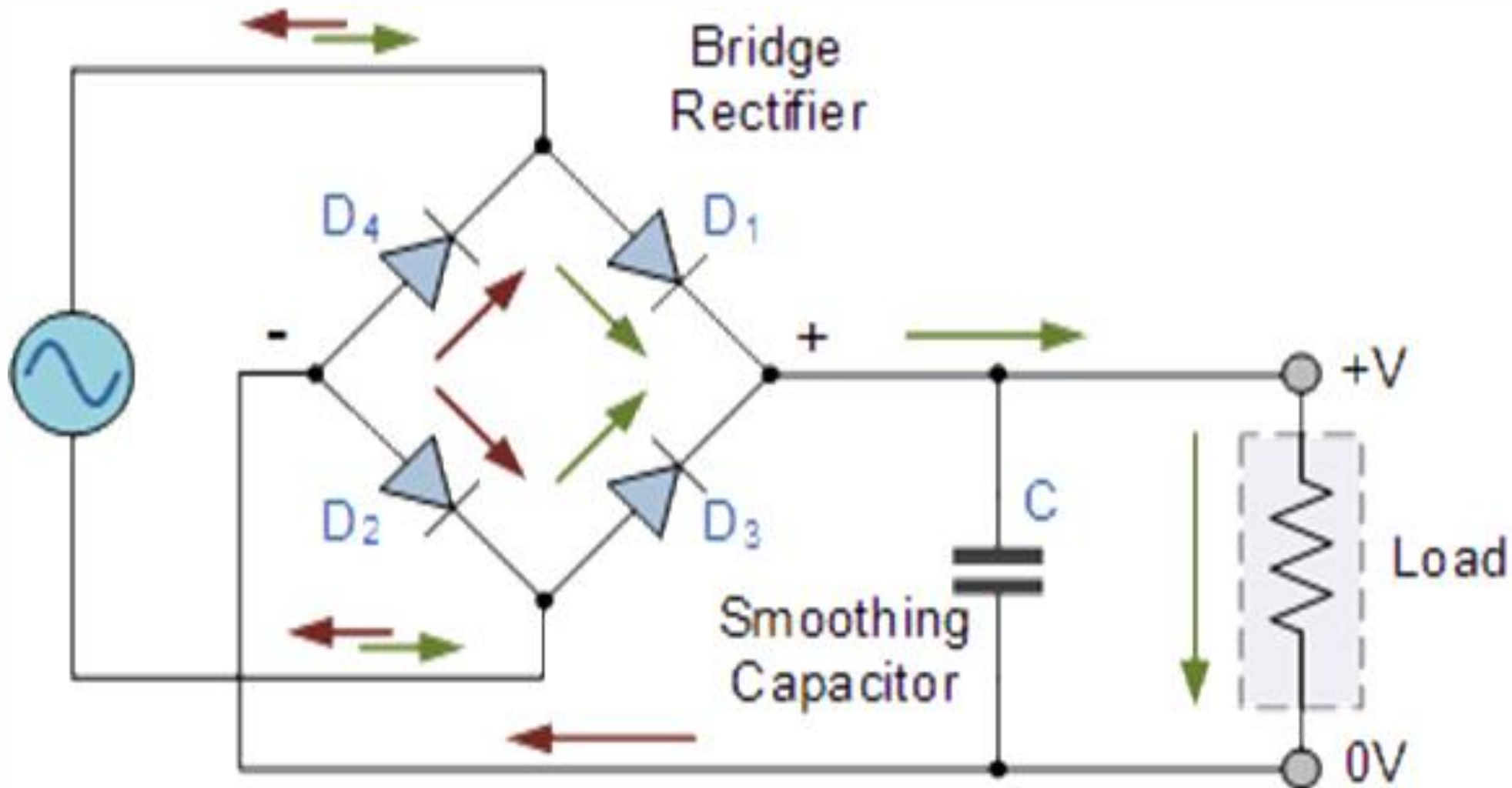


Waveform

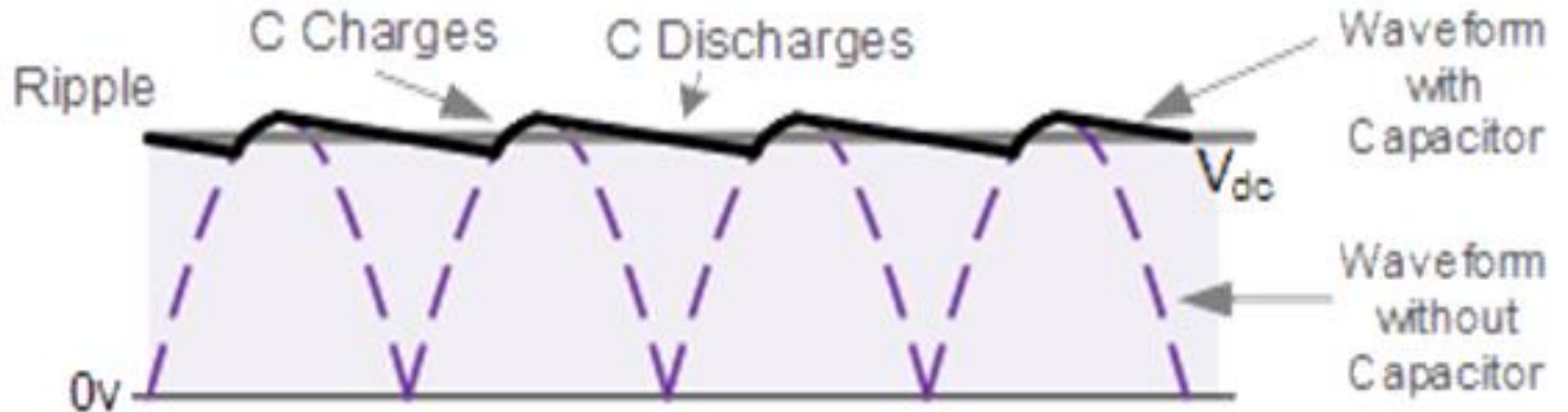

Resultant Output Waveform

EXPLORE MORE

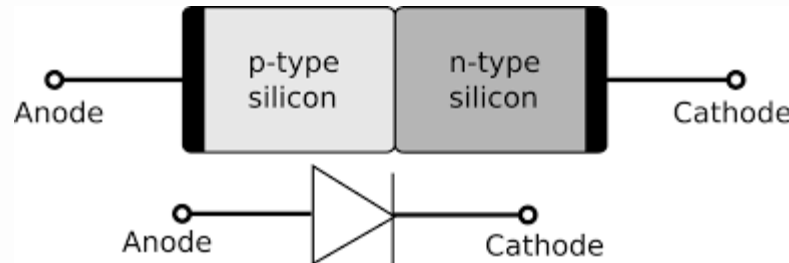Physical considerations on semiconductor diodes



L18 Learning Objectives

- a. Solve circuit analysis problems involving sources, resistances, and diodes
- b. Estimate power dissipation in diode circuits
- c. Select appropriate current-limiting resistors
- d. Determine voltage limits and waveforms at outputs of diode voltage-clipping circuits

Lecture 19: Exercises, Start Lecture 20!

- We will use this lecture to catch up, if needed
- We will do multiple exercises
- Slides may be distributed in lecture