




Lecture 12: IV Characteristics, Part II

- Measuring I-V Characteristics of Circuits
- Calculating I-V Characteristics of Linear Circuits
- Operating (I,V) point when Sub-circuits are Connected
- Power and the I-V Characteristics

$I = mV + b$. Why do we care?

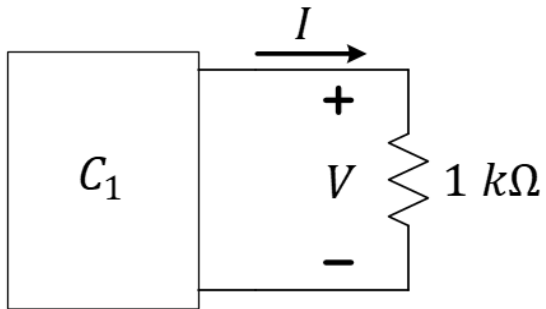
Linear IV models allow prediction of operating points before two circuits are joined...




$$C_1: I = 3m - \frac{1}{2k}V; C_2: I = \frac{1}{2k}V$$

$$V_{op} = 2V, I_{op} = 2mA$$

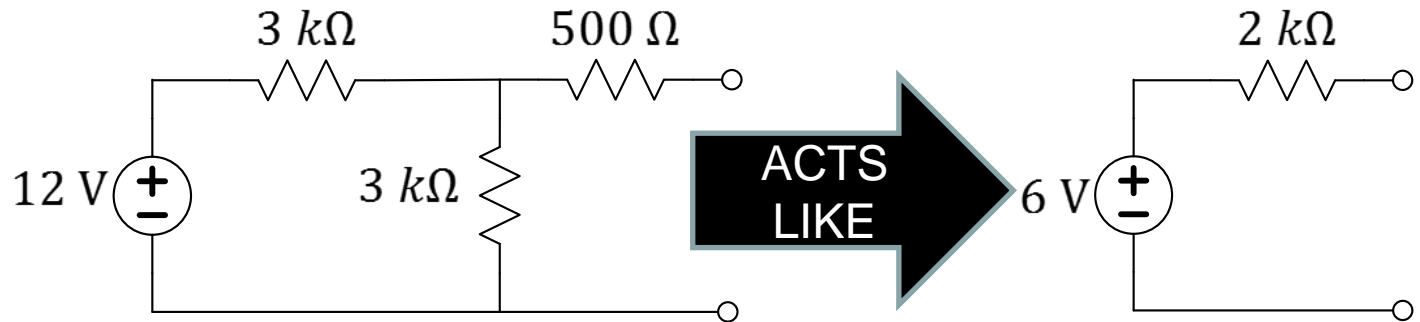Creates simpler models based on behavior...





Creates simpler models of nonlinear devices...

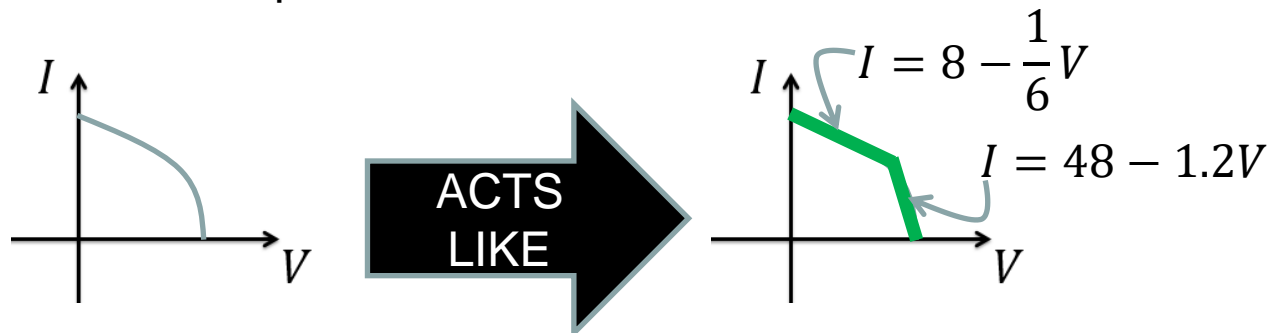


Linear I-Vs of source-resistor circuits

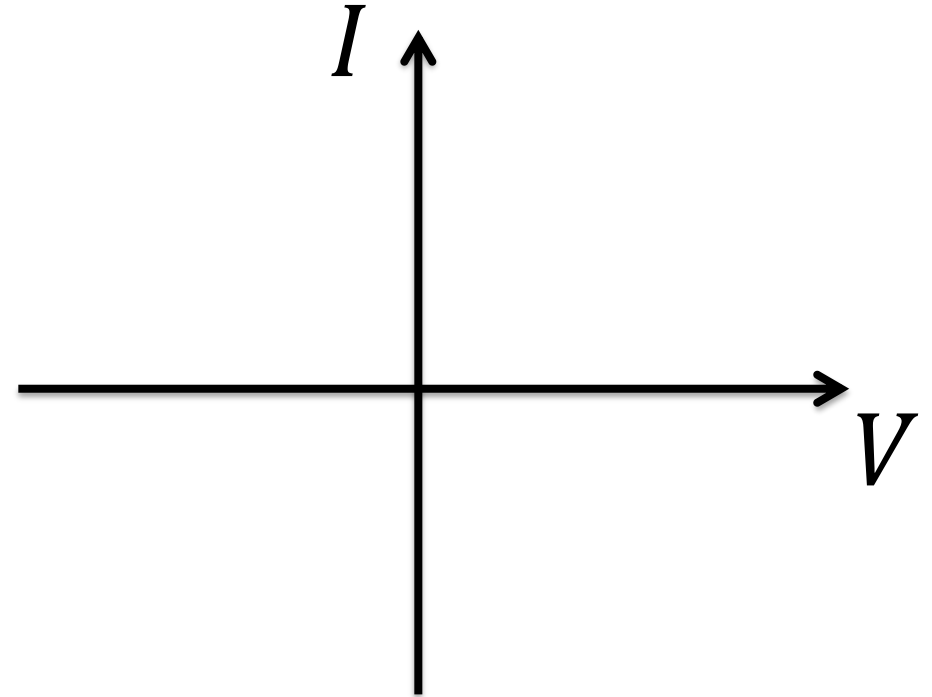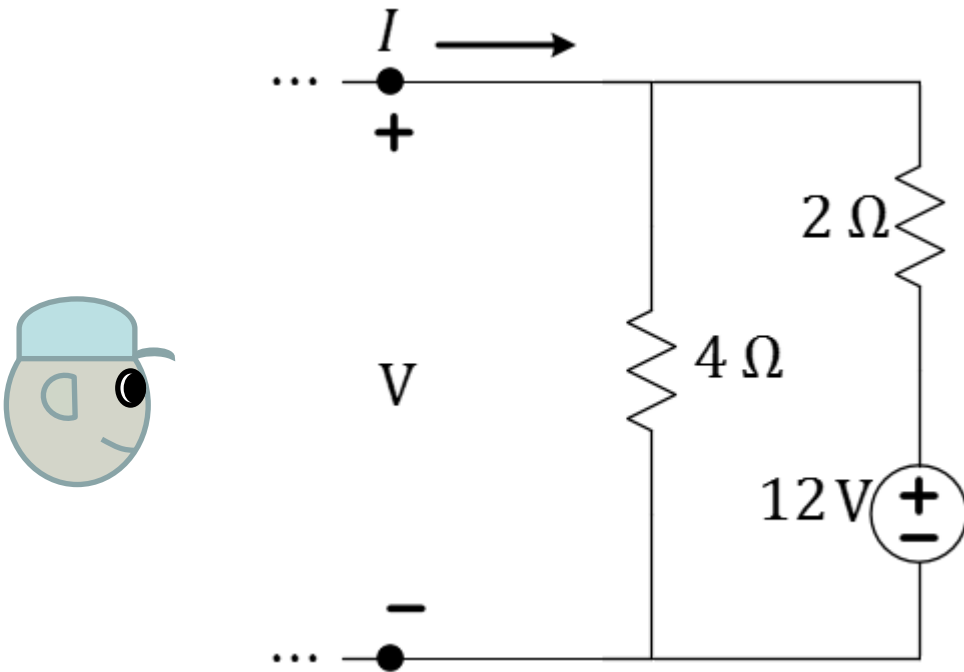Any combination of current or voltage sources with resistor networks has a linear I-V (between any two nodes).




Q: What are the current values of I when V is equal to 0V , 2V , and 4V ?

Connecting two sub-circuits

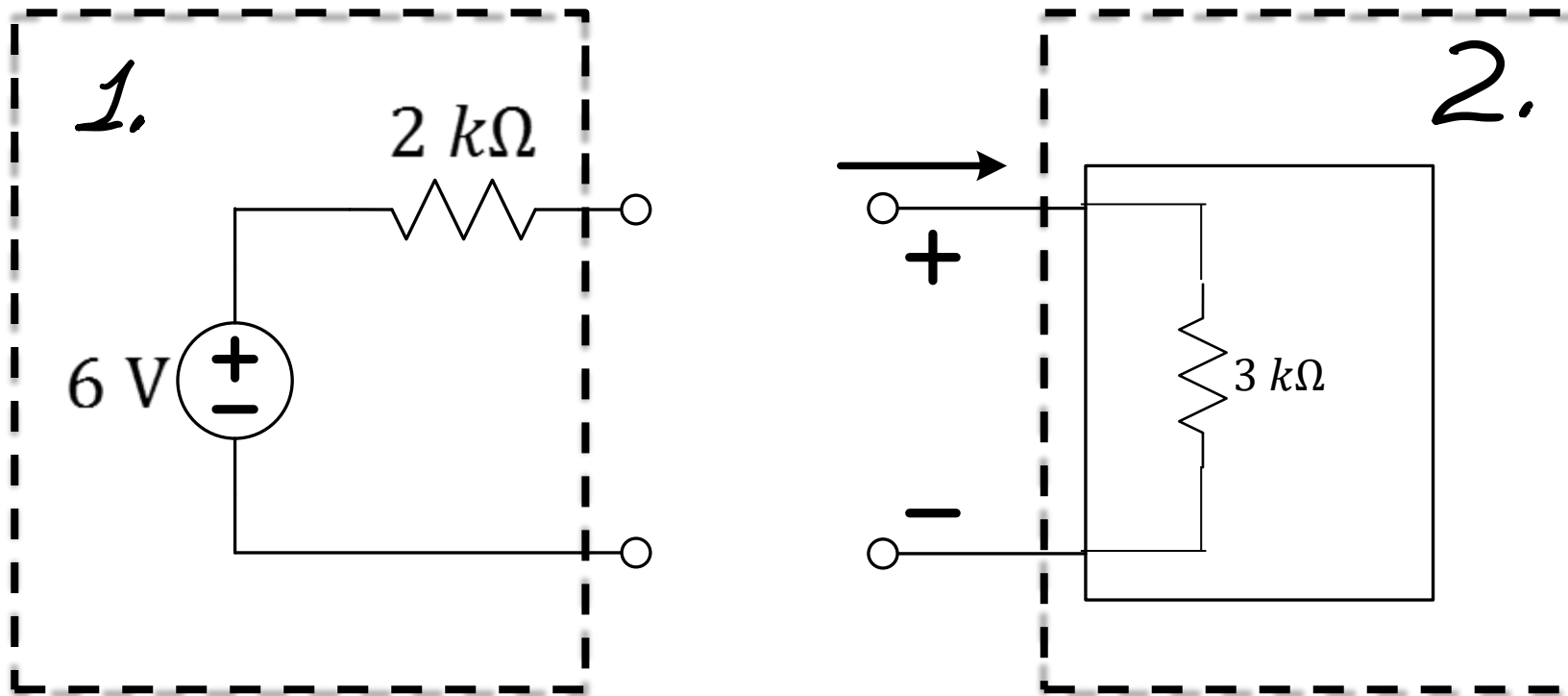


Q: What are the IV characteristics of a $3\text{ k}\Omega$ resistor?

Connecting two sub-circuits

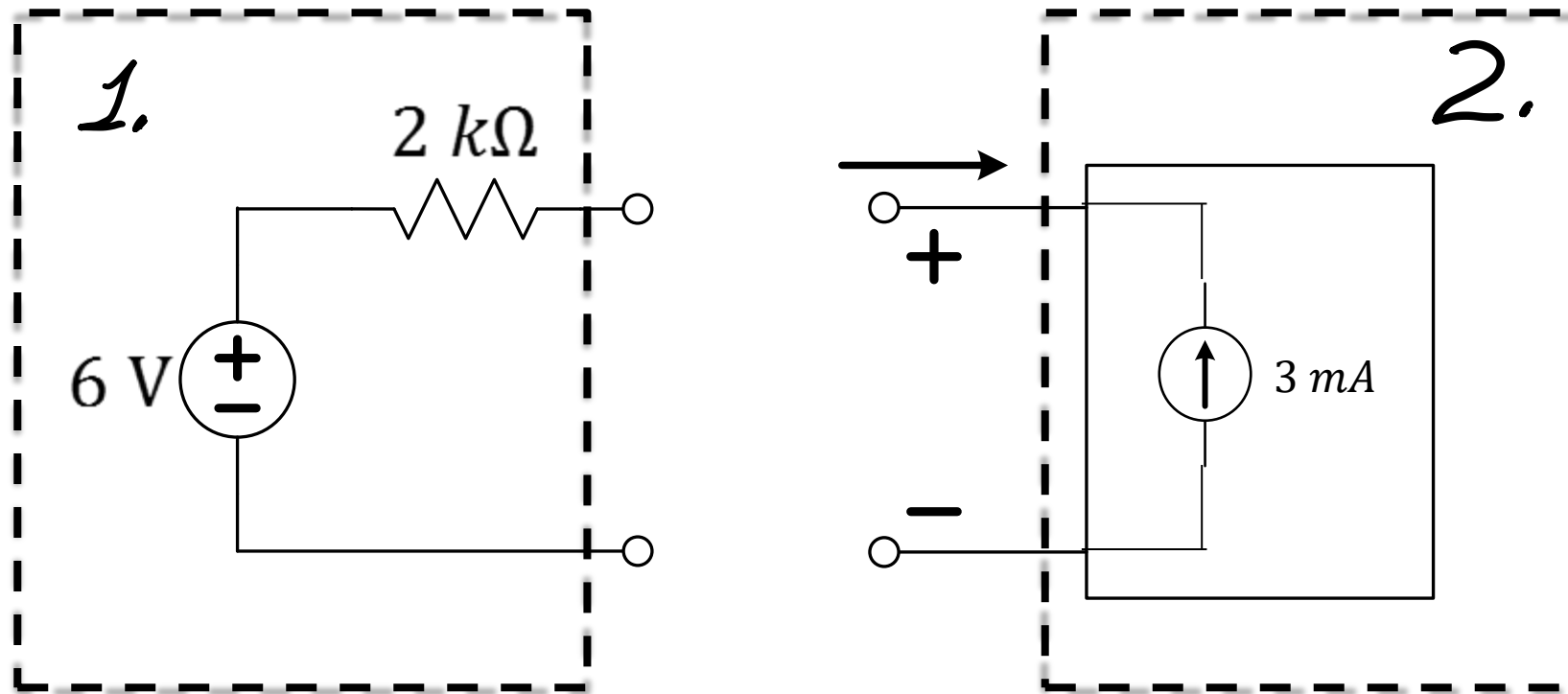


Q: What are the IV characteristics of a 3 mA current source?

Connecting two sub-circuits

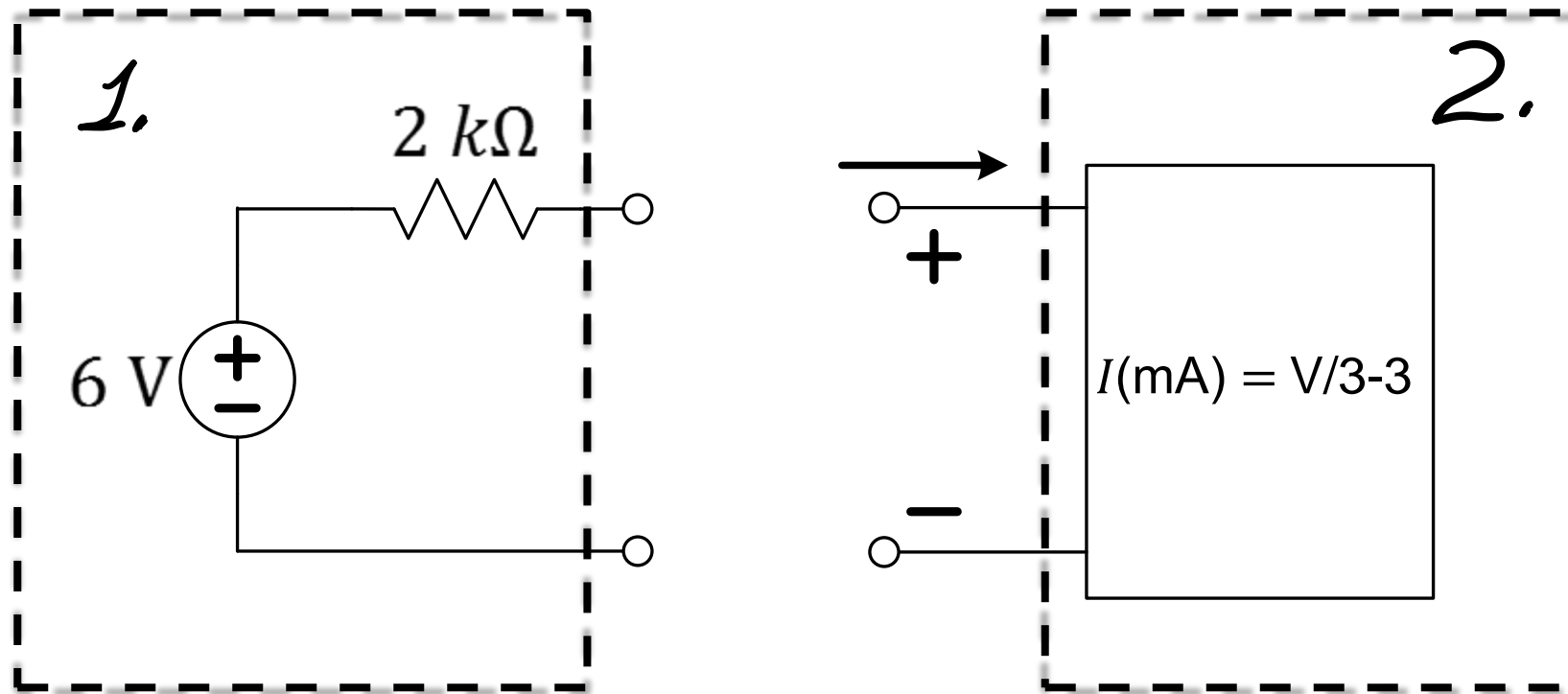


Q: Given the IV characteristic equation, what will be the operating point when C_1 is joined to C_2 ?

Connecting two sub-circuits (cont'd)

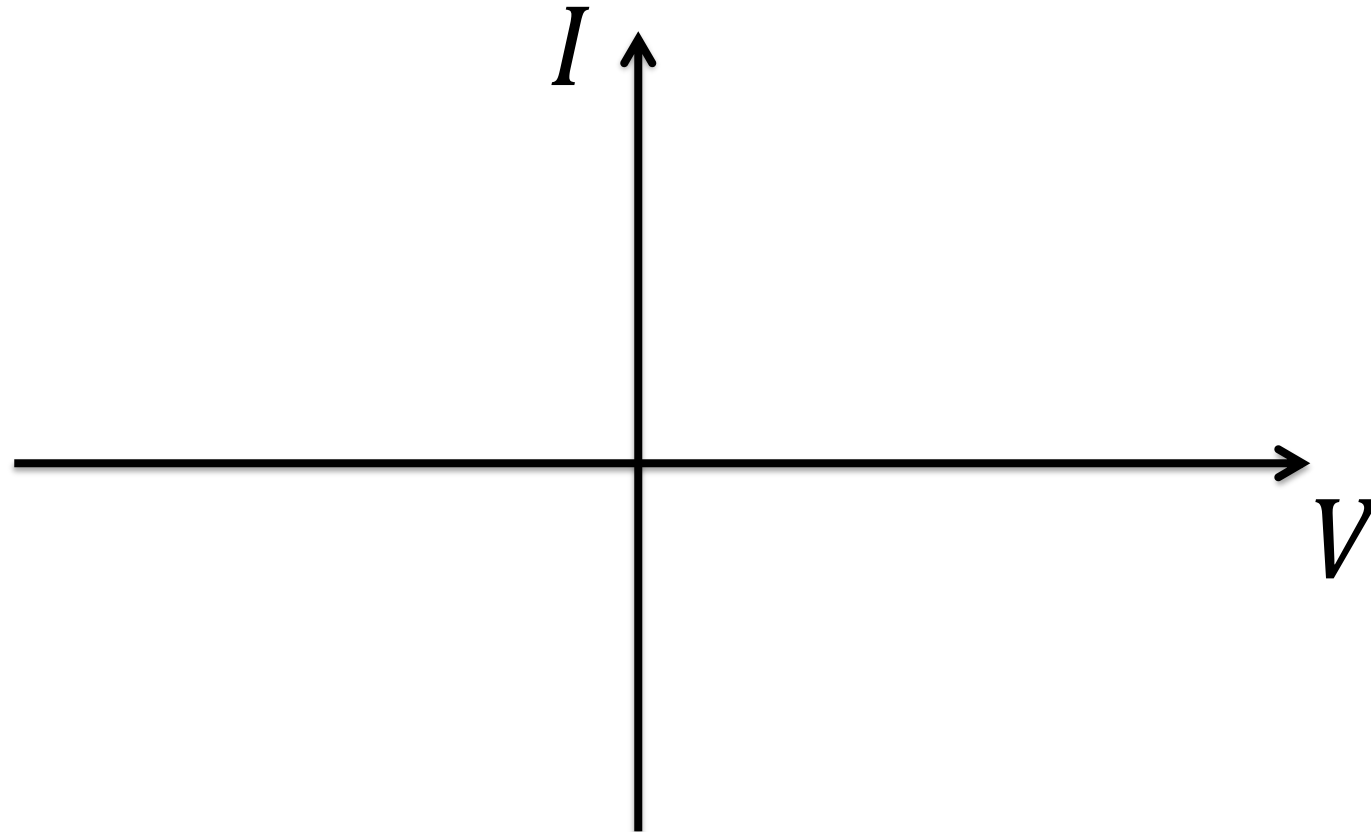

Q: Considering the three choices for circuit #2, what is the operating point when the two sub-circuits are connected? In each case, which sub-circuit supplies the power?


Either or Both Sources Can Supply Power

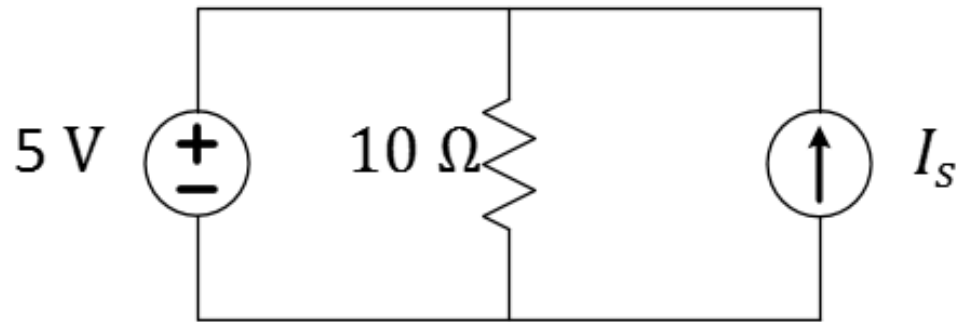

Q: For what values of I_S does the voltage source supply power?

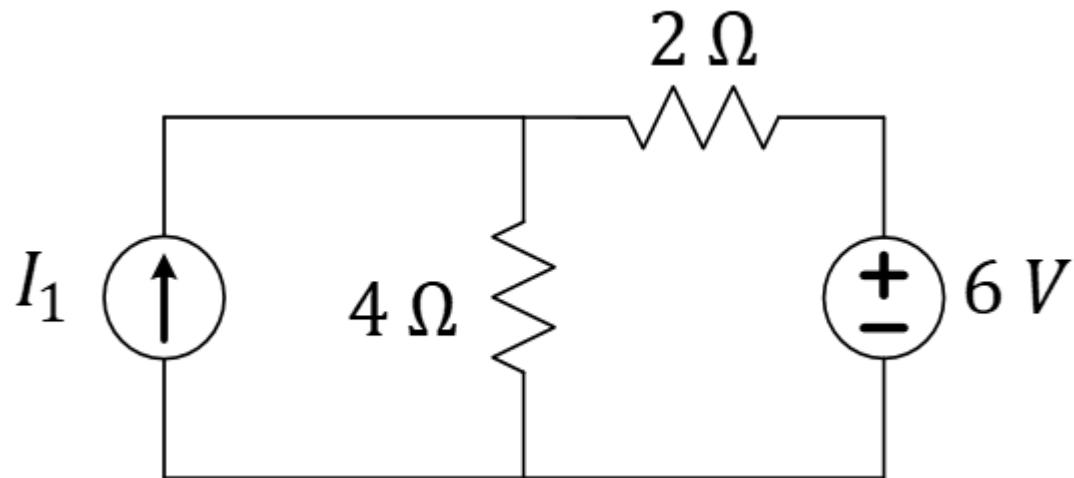Exercise

Q: What is the maximum value of I_1 for which the voltage source supplies power?



- A. -3 A
- B. -1.5 A
- C. 0 A
- D. 1.5 A
- E. 3 A



L12 Learning Objectives

- a. Find (V, I) operating points of connected sub-circuits
- b. Calculate power flow between connected sub-circuits