




Lecture 7: Circuit Tools

- Equivalent Resistance Defined
- Voltage Divider
- Current Divider
- Power Dissipation in Series and Parallel Resistive Loads
- Example Problems and Practice

Series Connection

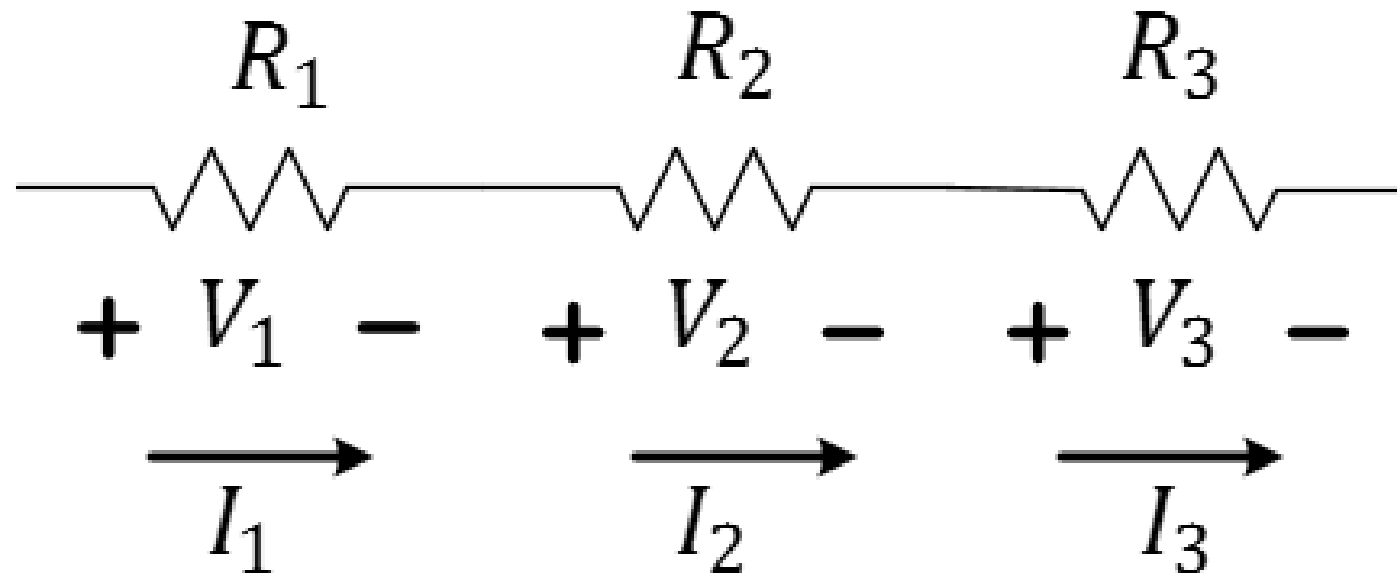
Series connections share the same current



$$I_1 = I_2 = I_3 \text{ because of KCL}$$


Equivalent Resistance

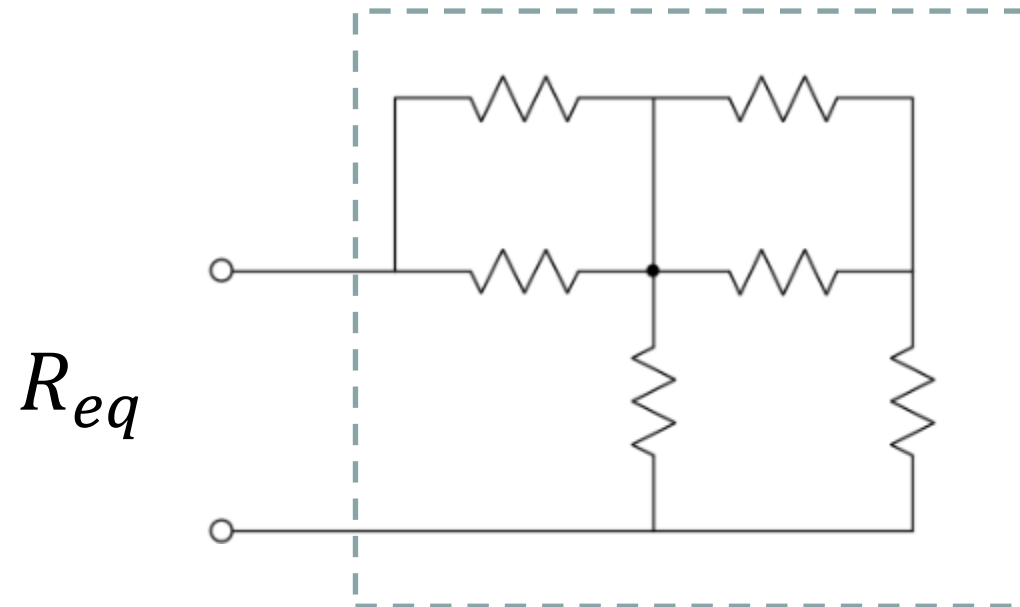Equivalent Resistance is the resistance value you get when you place an entire resistive network into a (virtual) box and characterize it as an Ohmic device (a new resistor).



Equivalent Resistance of Series Resistors

Resistances in series add up

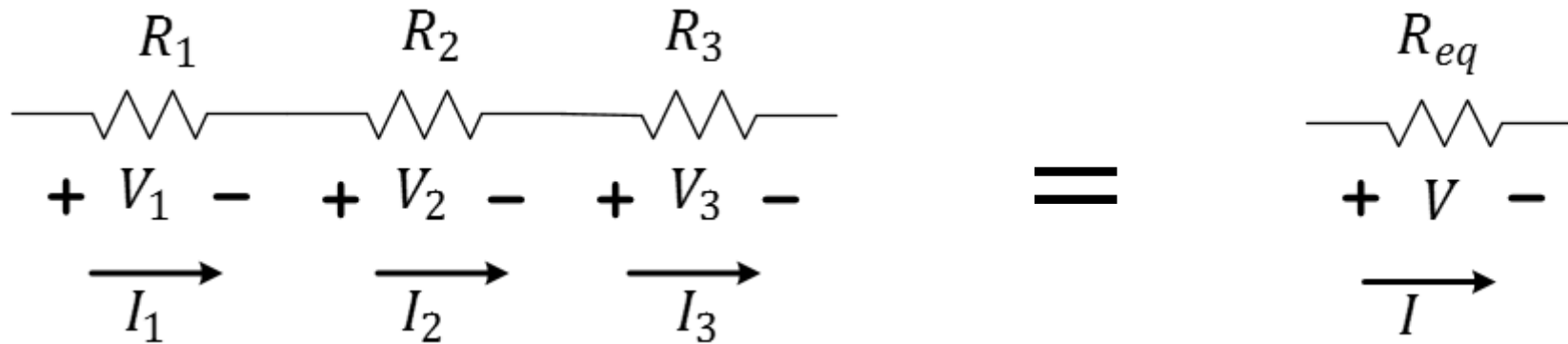



$$R_{eq} = R_1 + R_2 + \cdots + R_N$$

This can be intuitive: think of telegraphy wires in series.


Voltage Divider Rule (VDR)

When a voltage divides across resistors in series, more voltage drop appears across the largest resistor.

$$V_k = \frac{R_k}{R_{eq}} \cdot V_T$$

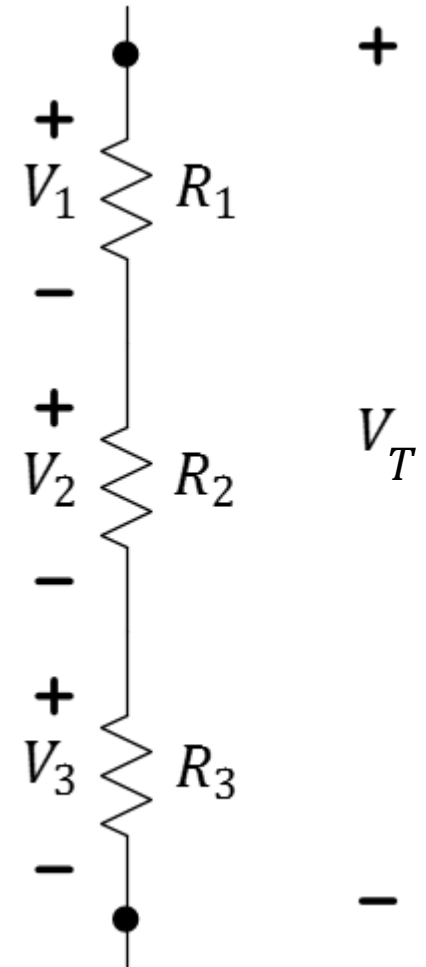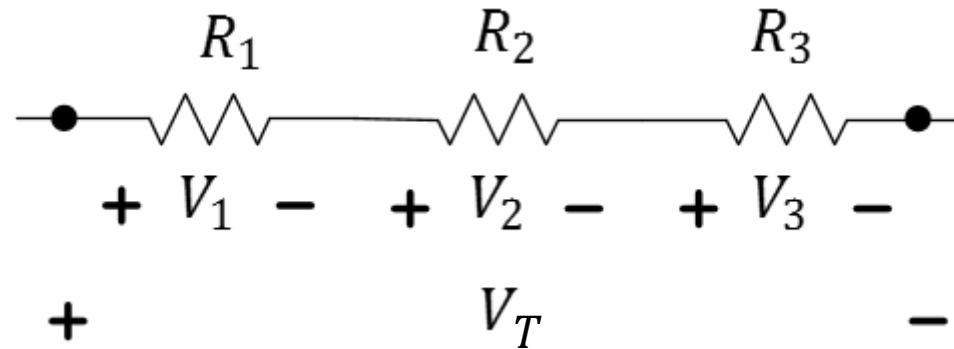


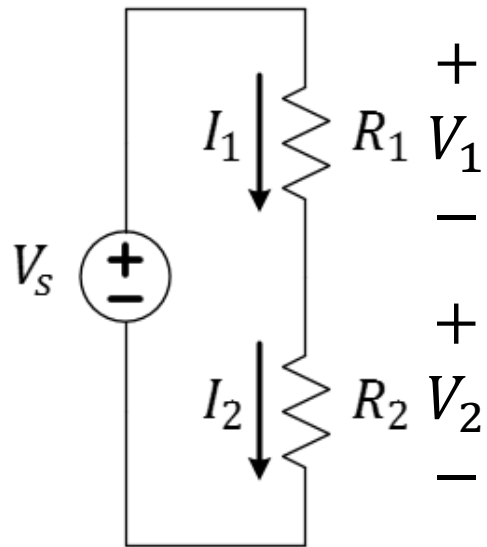Q: If $R_1 < R_2$, which of the following is true?




- A. $V_1 < V_2$ and $I_1 < I_2$
- B. $V_1 < V_2$ and $I_1 = I_2$
- C. $V_1 = V_2$ and $I_1 = I_2$
- D. $V_1 > V_2$ and $I_1 = I_2$
- E. $V_1 > V_2$ and $I_1 > I_2$

Q: Use VDR to find V_1 .

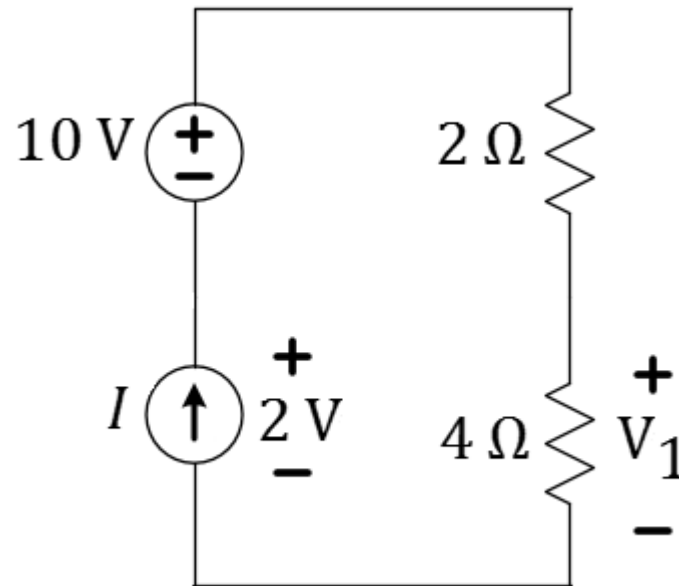

- A. $V_1 \leq -6V$
- B. $-6 < V_1 \leq -2V$
- C. $-2 < V_1 \leq 2V$
- D. $2 < V_1 \leq 6V$
- E. $6V < V_1$

VDR Derivation

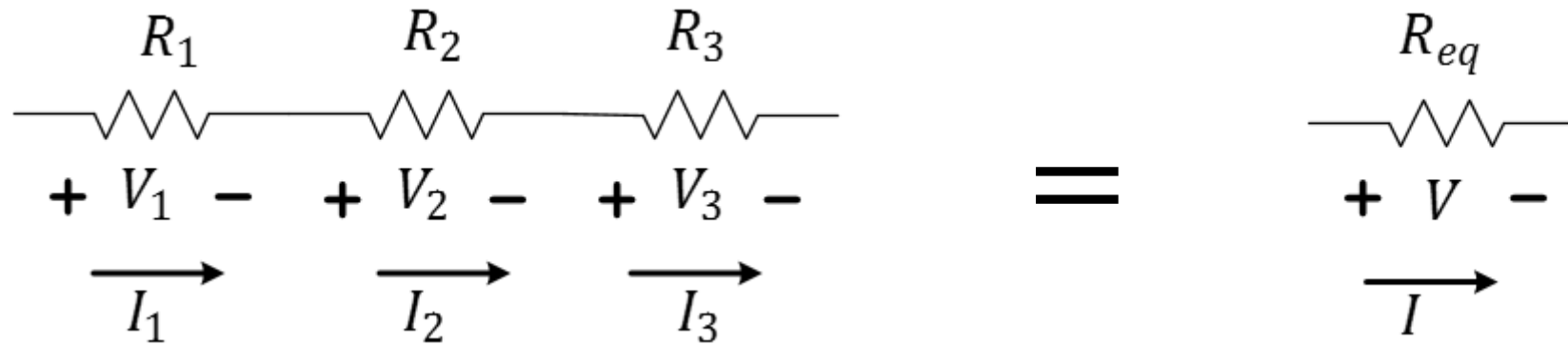


Since $I = I_k$, $\frac{V}{R_{eq}} = \frac{V_k}{R_k}$ by Ohm's Law. So, $V_k = \frac{R_k}{R_{eq}} \cdot V$



- Compares the input voltage to known voltages.
- Uses “voltage dividers” and “comparators”
- This is stuff we will understand through ECE110!

Parallel Connection

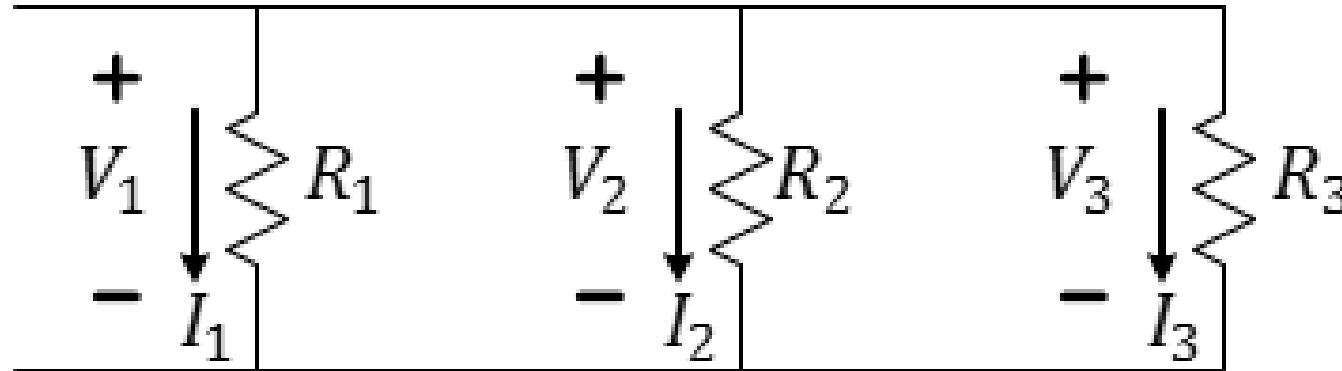Parallel connections share the same voltage potentials at two end nodes (shared by the elements)




$$V_1 = V_2 = V_3 \text{ because of KVL}$$

Q: Are appliances in your house/apartment connected in series or in parallel?

A.

B.

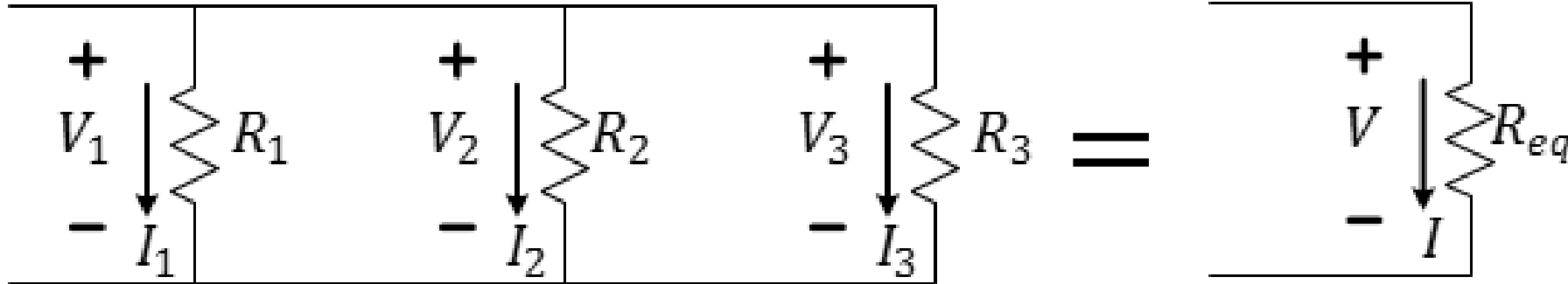Equivalent Resistance of Parallel Resistors



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

If $N = 2$,

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Q: Which statement is true in general?



A. $R_{eq} \approx R_1$

B. $R_{eq} < R_1$

C. $R_{eq} > R_1$

D. None of these is true

Resistors and Power Ratings

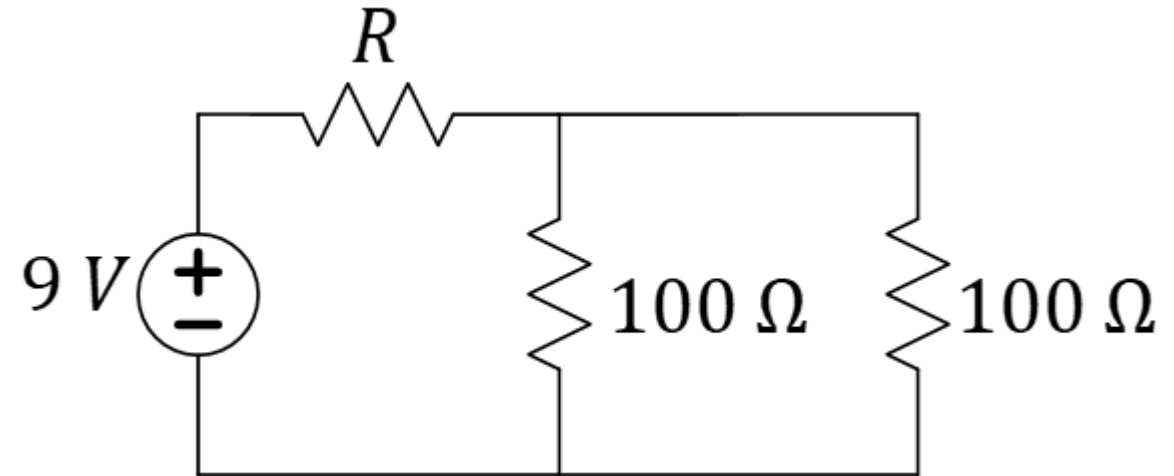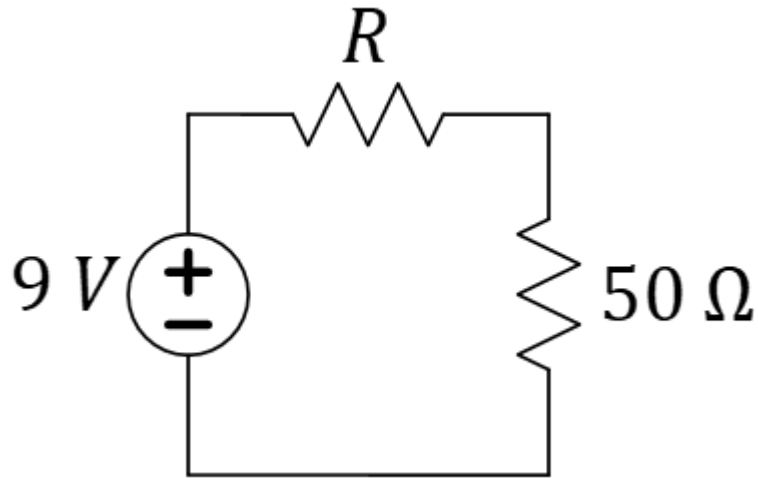


Q: Which statement is true regarding a single 50-Ohm resistor vs two 100-Ohm resistors, each of which is rated $\frac{1}{4}$ -watts, used as shown above in the same circuit?

- ☒ A. The 100-Ohm parallel combination has twice the power rating.
- B. The 100-Ohm parallel combination has a resistance of 200 Ohms.
- C. The 100-Ohm parallel combination has twice the probability of failure.
- D. None of these are true.
- E. All of these are true.

Current Divider Rule (CDR)


When a current divides into two or more paths, a greater amount of current will go down the path of lower resistance.

$$I_k = \frac{R_{eq}}{R_k} \cdot I$$

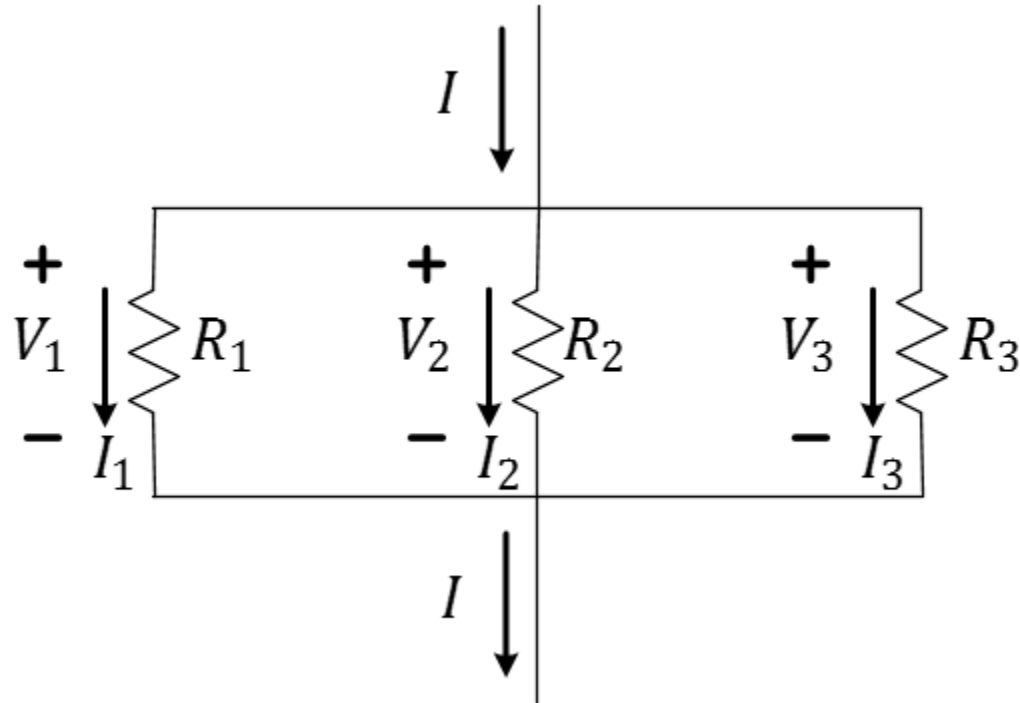

One CDR Application

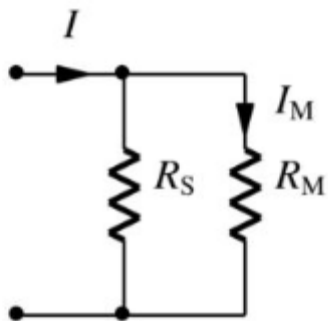- High-current Ammeter
- Use a high-power shunt resistance R_S to carry most of the current
- Measure the current through R_M (the meter resistor) using a galvanometer.




Q: Which is true in this application?

- A. $R_S \ll R_M$
- B. $R_S \gg R_M$
- C. $R_S \approx R_M$

Q: Give the formula for I (the current we want measured) in terms of I_M (the current we did measure).

$$I = \frac{R_k}{R_{eq}} I_M = \dots = \frac{R_S + R_M}{R_S} I_M$$

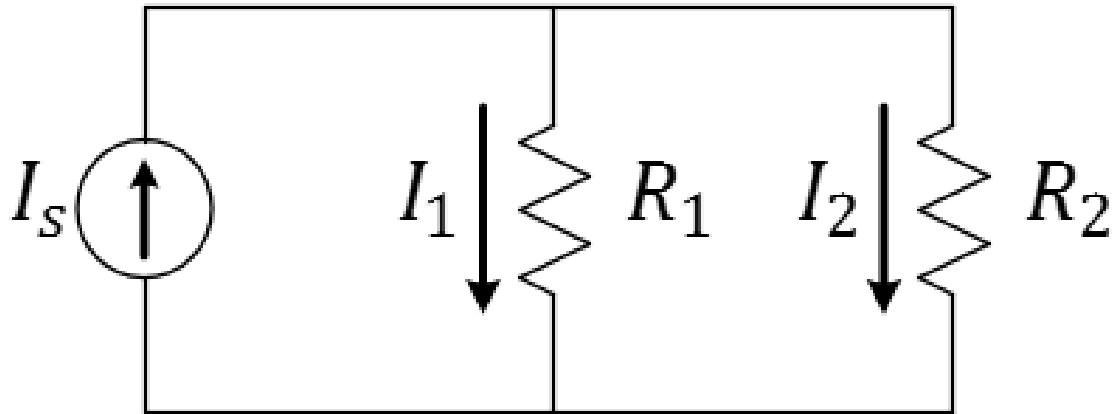Q: If $R_1 < R_2$, which of the following is true?



A. $I_1 < I_2 < I_s$

B. $I_1 < I_s < I_2$

C. $I_2 < I_1 < I_s$

D. $I_2 < I_s < I_1$

E. $I_s < I_2 < I_1$

Q: In a parallel connection, does A. a smaller or B. larger resistor absorb more power?



L7 Learning objectives

- a. Identify series and parallel connections within a circuit network
- b. Find equivalent resistance of circuit networks
- c. Compute power ratings of resistor networks
- d. Estimate resistance by considering the dominant elements
- e. Apply rules for current and voltage division to networks
- f. Apply conservation of energy to components within a circuit network